

Lab 1: Basic electrical measurements (version 1.2)

WARNING:

- *Do not make voltage measurements while the multimeter is set for current measurements as this will blow the current limiting fuse.*
- *Do not turn on the power supply until you have double-checked your circuit.*
- *Do not attempt to make a current measurement across a voltage supply as this can damage (blow fuse) in the current meter.*

Equipment:

DC Power Supply
Digital Multimeter
Circuit breadboard
Resistors & Jumper wires

Concepts:

Ohm's & Kirchhoff's Laws
Loaded Circuit: Thevenin Theorem
Voltage and Current measurements

Lab Goals

Build simple circuits. Measure voltage and current at every part of the circuit. Use Ohm's and Kirchhoff's Laws to calculate the expected voltage and current given the input voltage and measured resistors.


Key steps:

- Measure resistance of each resistor before you assemble circuit. You cannot measure the resistance of individual resistors while they are part of a circuit.
- Make an estimate of the maximum power dissipated in any resistor (you are using $\frac{1}{4}$ W resistors).
- Verify power supply voltage by measuring voltage.
- Assemble circuit on breadboard.
- Measure voltage between all points in the circuit.
- Measure current at all points in the circuit.

Elementary circuits

Select two/three different resistors with values in the range 300-3000 Ω . Resistance is read using the color band code described in the Appendix below. Always measure individual components before placing them in a circuit, or isolated (otherwise measurements will be affected by other components in the circuit). Compare them with expected values.

Construct the circuit **Circuit 1** in the breadboard using the resistors and a DV voltage supply (you can use the circuit design work station which contains fixed and variable voltage supplies and variable resistors among other elements/components). Use Ohm's and Kirchhoff's Law to calculate the current thought and voltages across each component. Compare with measurements.

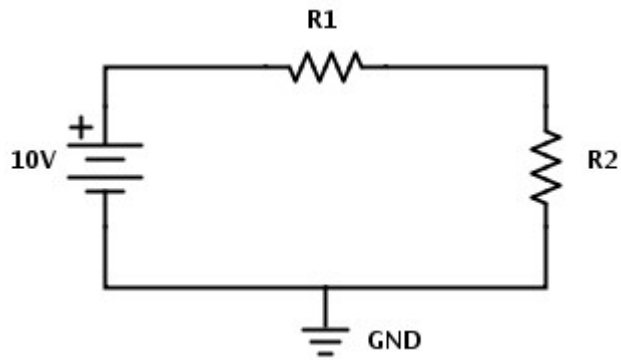

Circuit 1

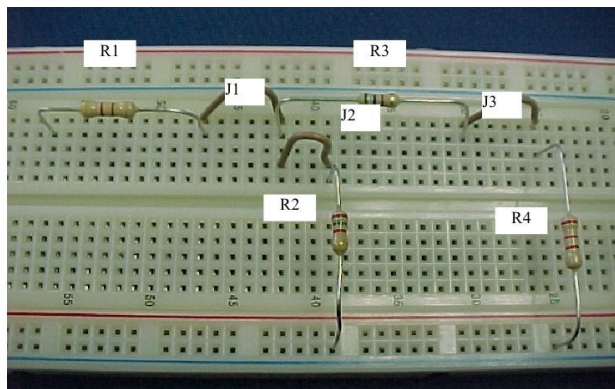


Fig. 3. **Example** of a common resistor circuit with jumper wires.

Note: Before wiring it to the breadboard, set the voltage to the input voltage. The circuit must be in the form of a closed loop. Current flowing from the positive terminal requires a path back to the power supply negative terminal. In the circuit diagram, the negative terminal of the power supply is connected to GND (ground). Because potential (voltage) is a relative measurement, the ground point is a reference point.

DC voltage & measurements

- Measure the voltage drops across R1 and R2 and compare to the calculated values.
- Measure the current in different points of the circuit, and compare it to the calculated value.


WARNING: Do not make voltage measurements while the multimeter is set for current measurements as this will blow the current limiting fuse.

Note: Current and Voltage measurements. A current measurement is distinctly different from voltage measurement and uses a different input port. A **voltage measurement** is made by placing the test lead across a component, i.e. the meter is *in parallel*. In contrast, **current is measured** by inserting the meter *in series*. To do this, the loop is broken open at a point and the meter is then inserted to complete the circuit.

Circuit 2

Construct the **Circuit 2** with additional resistors. Repeat the analysis for the following circuit:

- Make a table with the calculated values of voltage drop and current for all four resistors (8 values total).
- Build the circuit and measure the current and voltage.
- Compare the measurements with calculations.

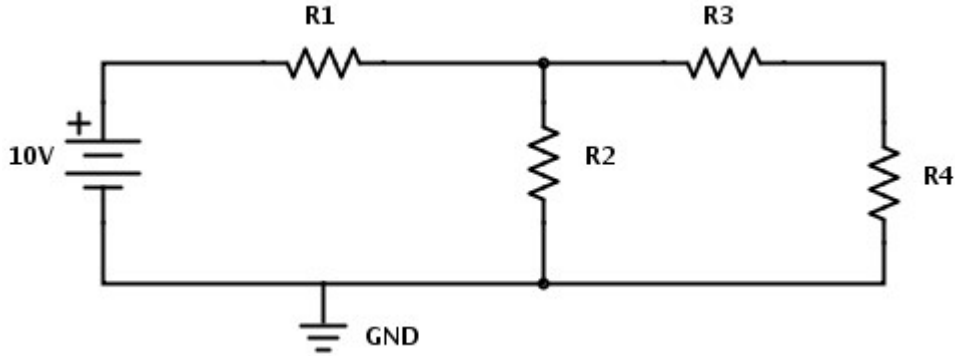

Circuit 2


Analysis:

For the analysis in your lab notebook, report all your measurements on tables. Describe calculations and derivations to get theoretical predictions. Describe experimental setup and procedure, including diagrams. Compare measurements with expected values and discuss. Discuss results.

Appendix

Manufacturers use colored bands to label resistors. The most common scheme uses 4 bands. Bands 1 and 2 specify the numerical value and Band 3 is the decimal multiplier. Band 4 indicates the production tolerance and is often offset from the other bands.

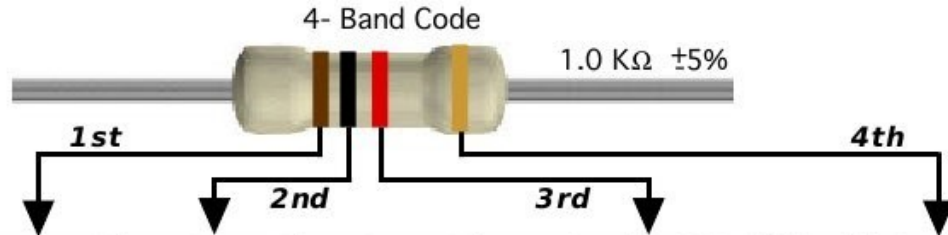In the example below, Bands 1—3 are brown-black-red. This is decoded as $10 \times 100 = 1000 \Omega$. Band 4 indicates it will have a value in the range $1000 \pm 50 \Omega$.



| Color | 1st Band | 2nd Band | 3rd Band | Decimal Multiplier | | Tolerance |
|---------------|----------|----------|----------|--------------------|---------------|-----------|
| Black | 0 | 0 | 0 | 1 | 1 | |
| Brown | 1 | 1 | 1 | 10 | 10 | ± 1 % |
| Red | 2 | 2 | 2 | 100 | 100 | ± 2 % |
| Orange | 3 | 3 | 3 | 1K | 1,000 | |
| Yellow | 4 | 4 | 4 | 10K | 10,000 | |
| Green | 5 | 5 | 5 | 100K | 100,000 | |
| Blue | 6 | 6 | 6 | 1M | 1,000,000 | |
| Violet | 7 | 7 | 7 | 10M | 10,000,000 | |
| Gray | 8 | 8 | 8 | | 100,000,000 | |
| White | 9 | 9 | 9 | | 1,000,000,000 | |
| Gold | | | | | 0.1 | ± 5 % |
| Silver | | | | | 0.01 | ± 10 % |
| None | | | | | | ± 20 % |