


Lab 2: AC Circuits and Oscilloscope

Ideal meters

VOLTMETER:

$$I_{\text{meter}} \approx 0$$


Example: 10x oscilloscope probe

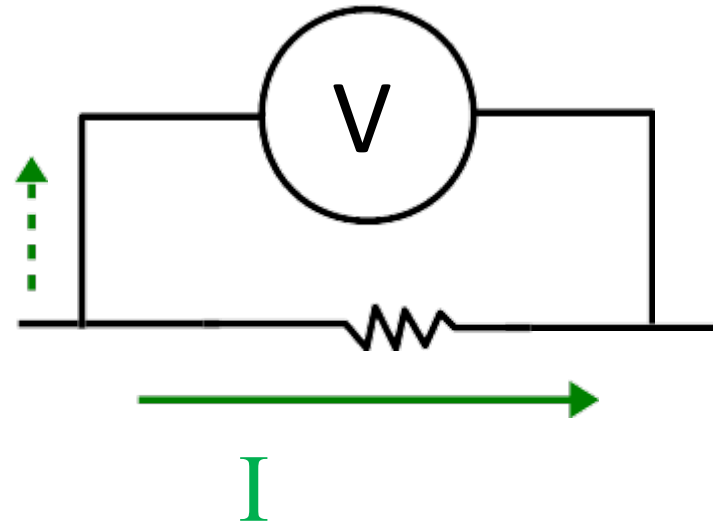

Ideal meters


VOLTMETER:

$$I_{\text{meter}} \approx 0$$

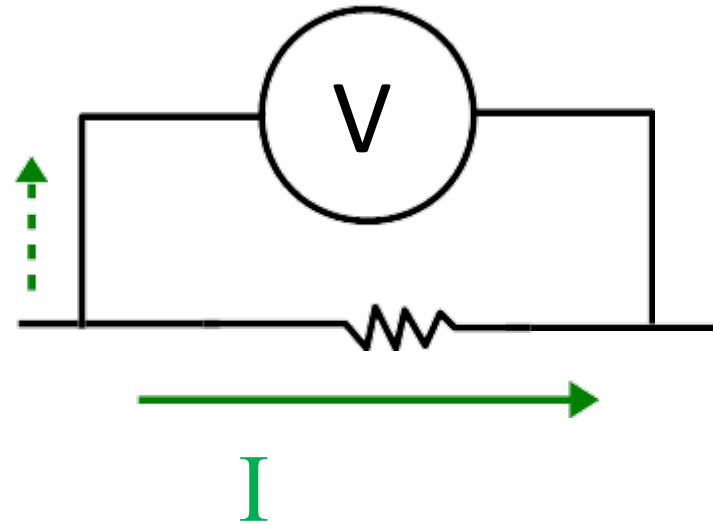


Example: 10x oscilloscope probe

AMMETER:

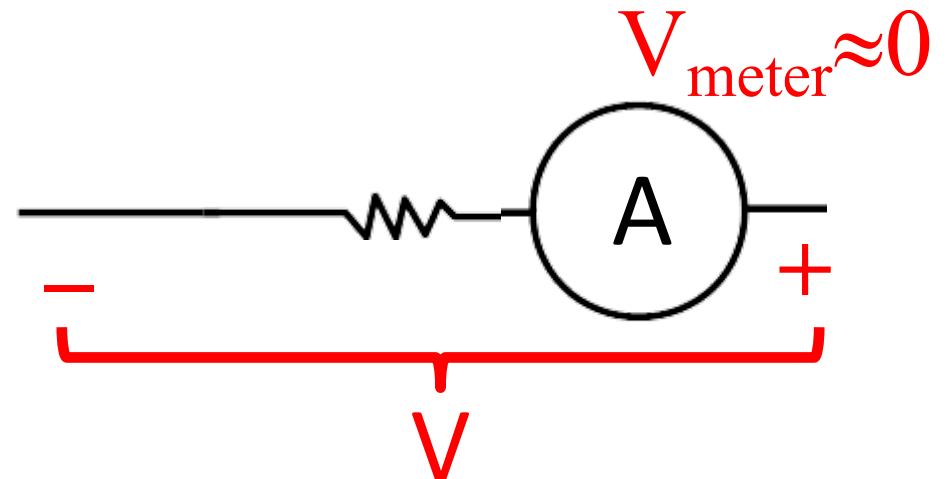

Power Dissipation

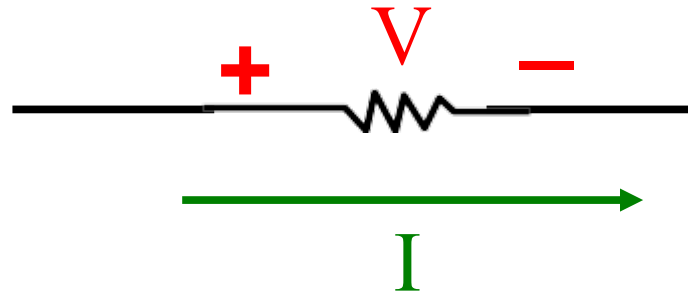


$$\text{Energy} = VQ$$

$$\text{Power} = d(\text{Energy})/dt$$

$$\text{Power dissipated} = \frac{V^2}{R} = I^2 R$$


AC (Alternating Current) Circuits

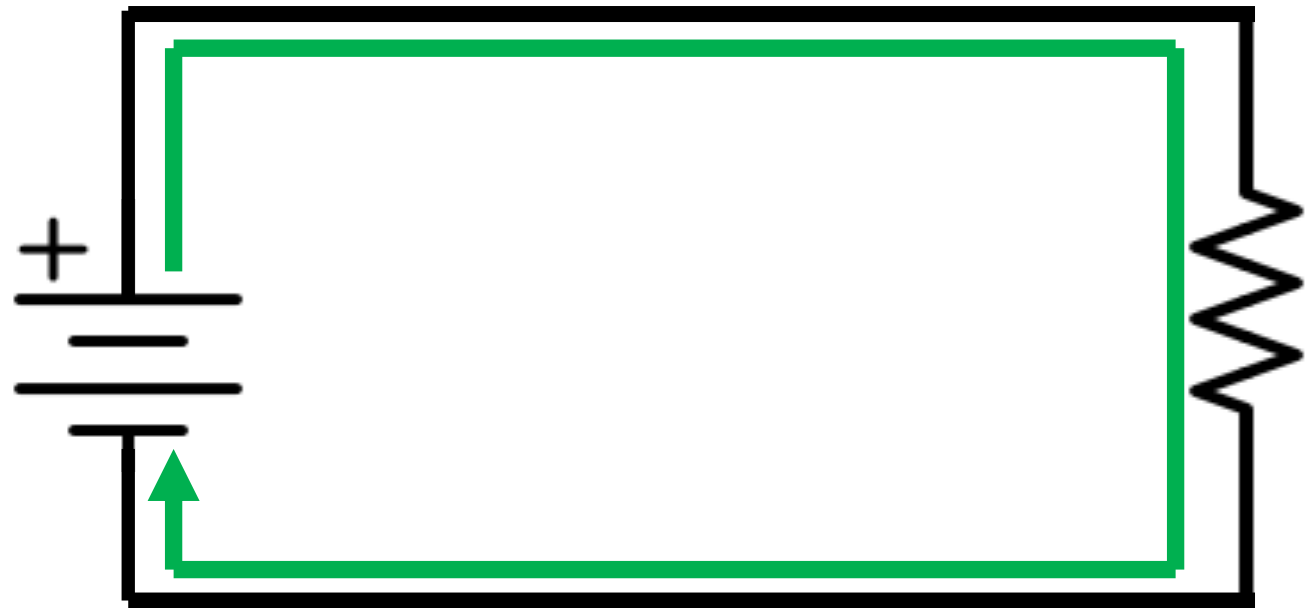


Current flow

AC (Alternating Current) Circuits


Current flow

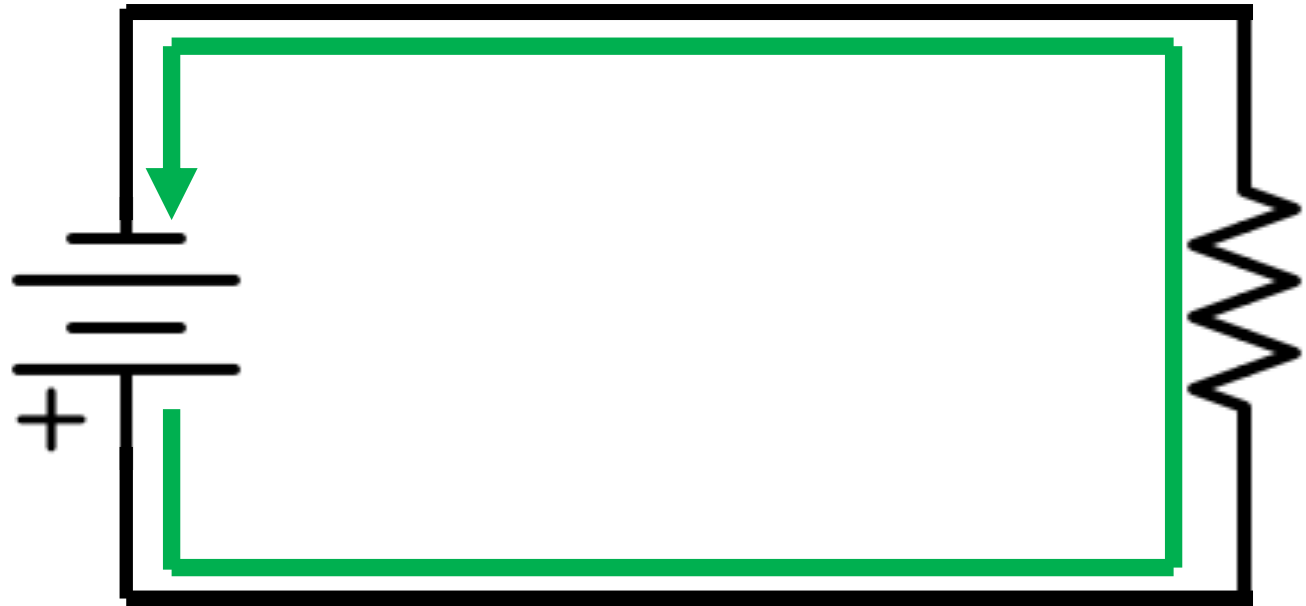



Square wave source

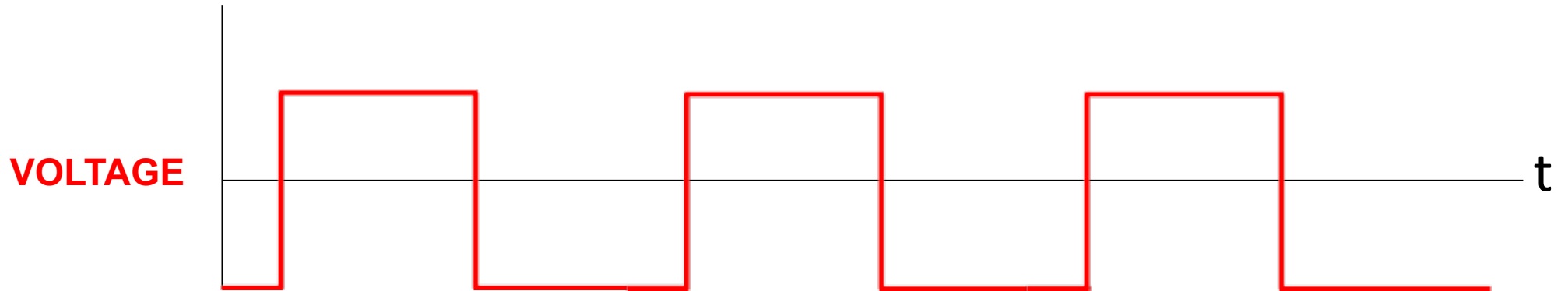



Square wave source

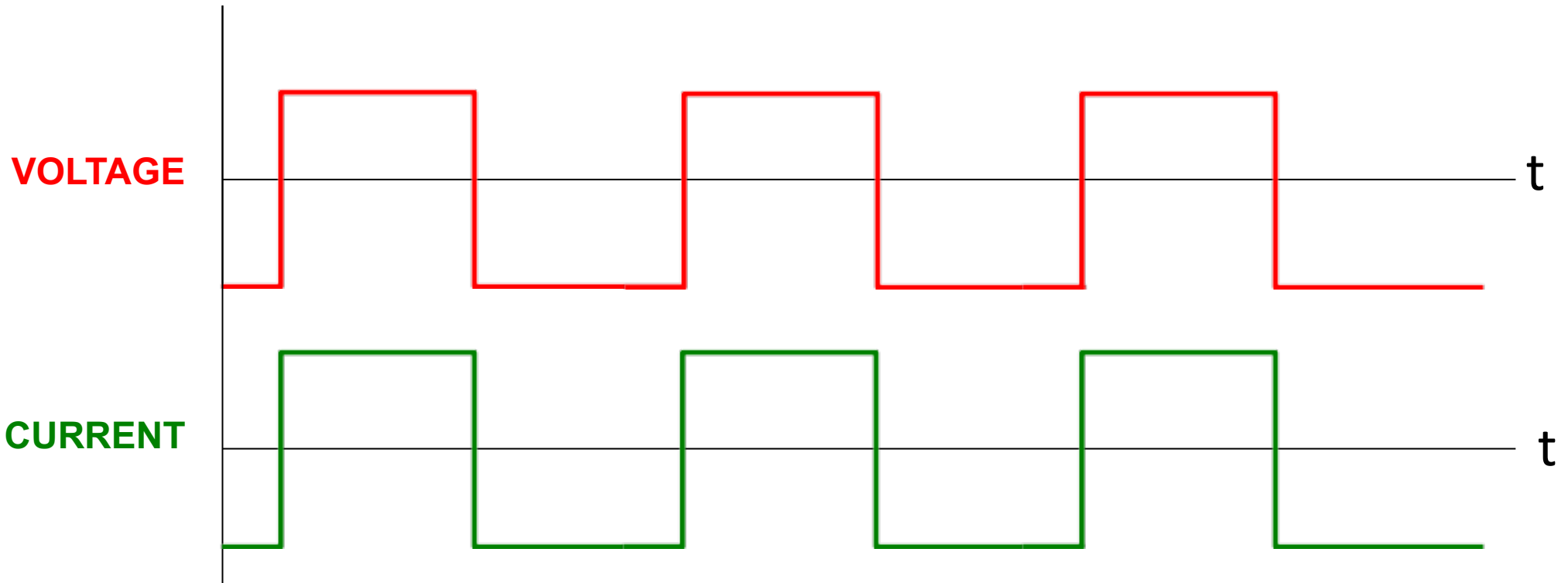



Square wave source +

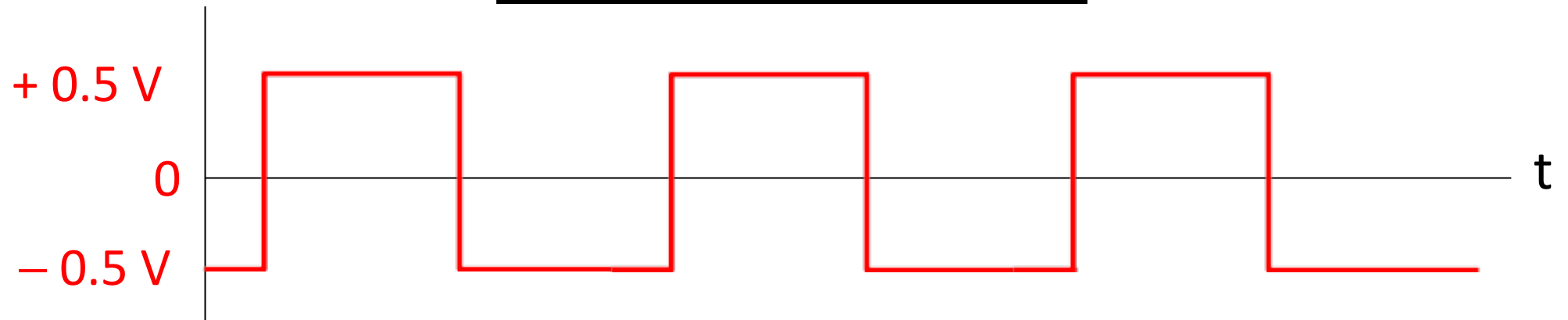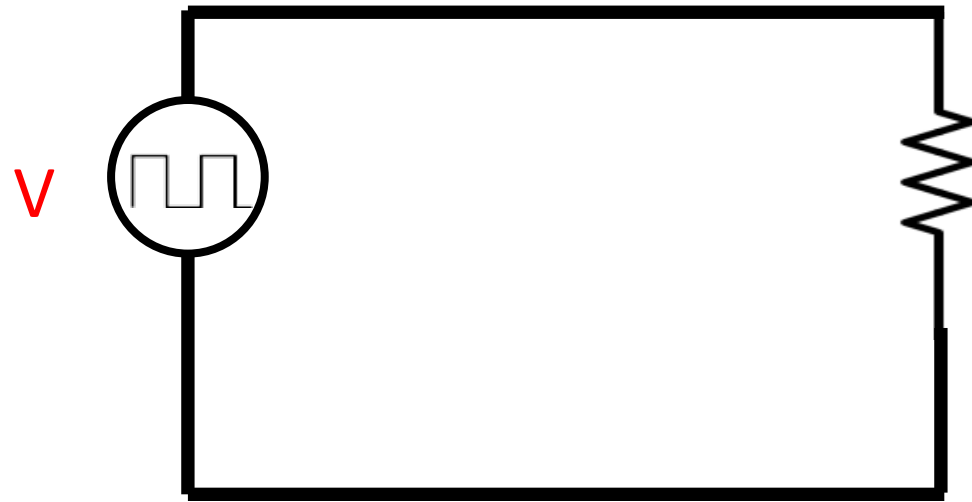


Square wave source + voltage offset

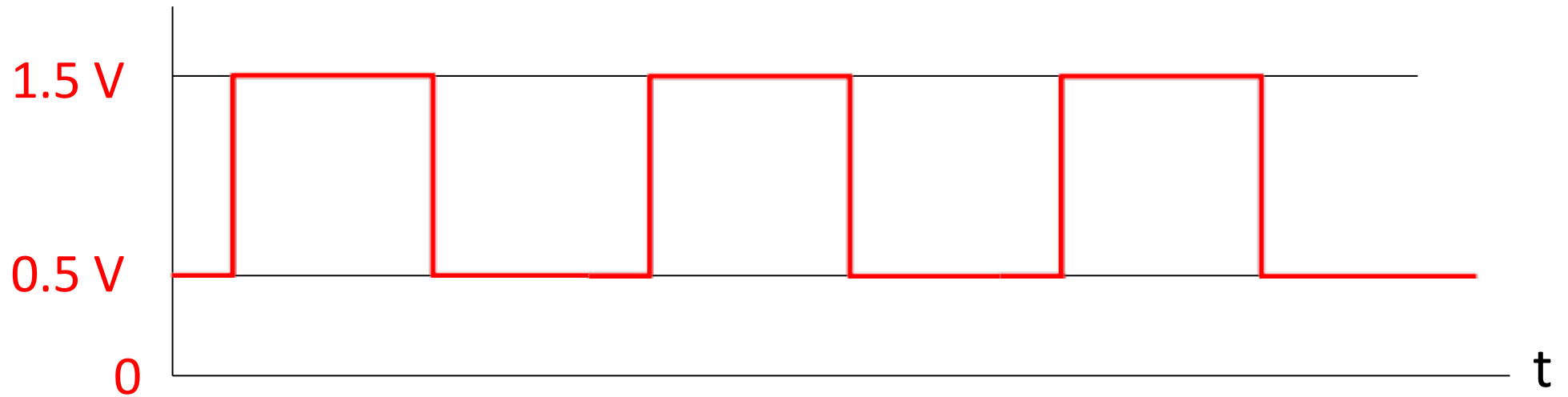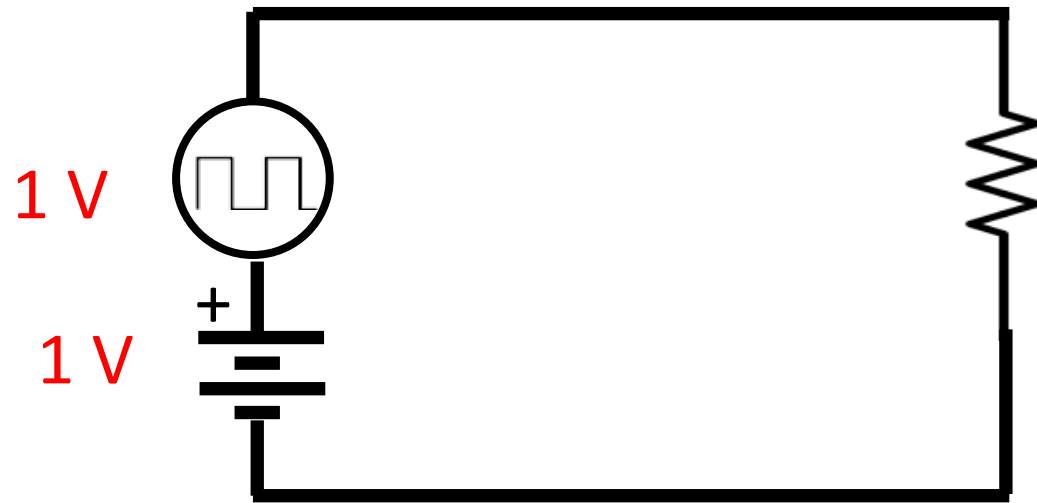



Square wave source + voltage offset

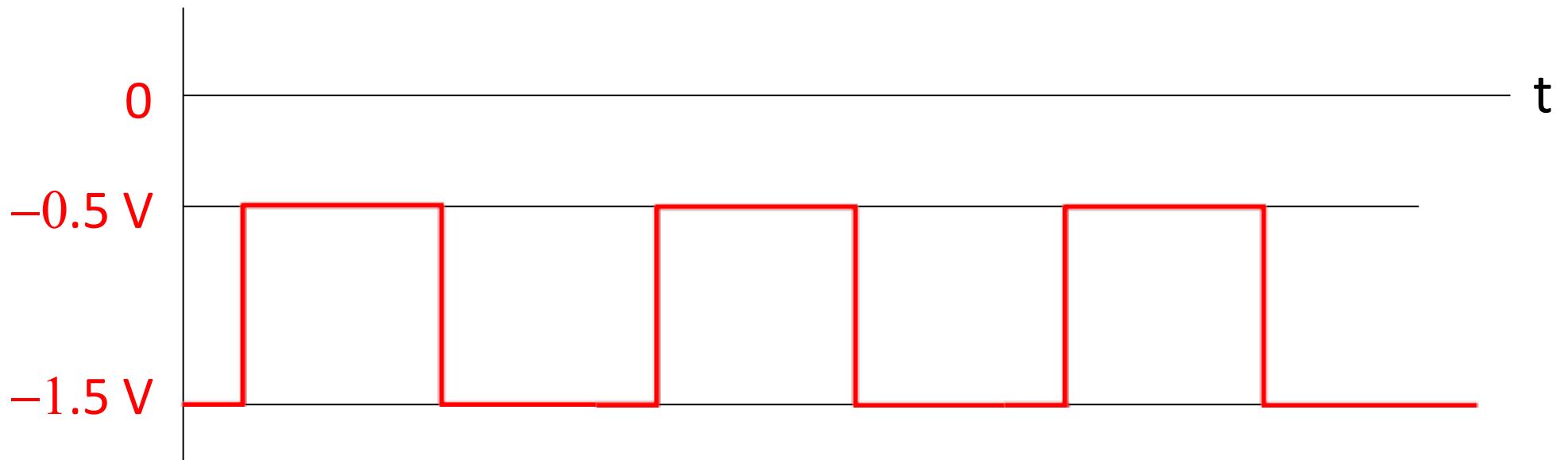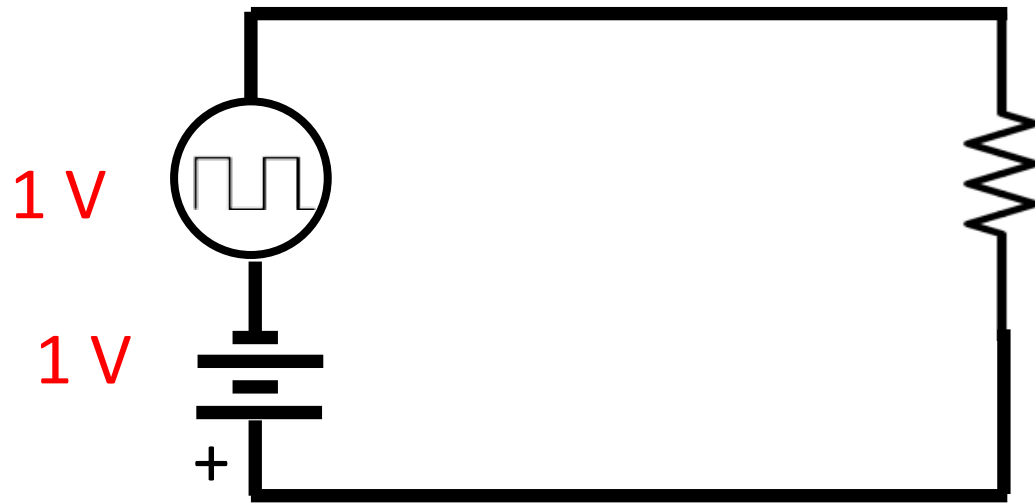



Square wave source + voltage offset

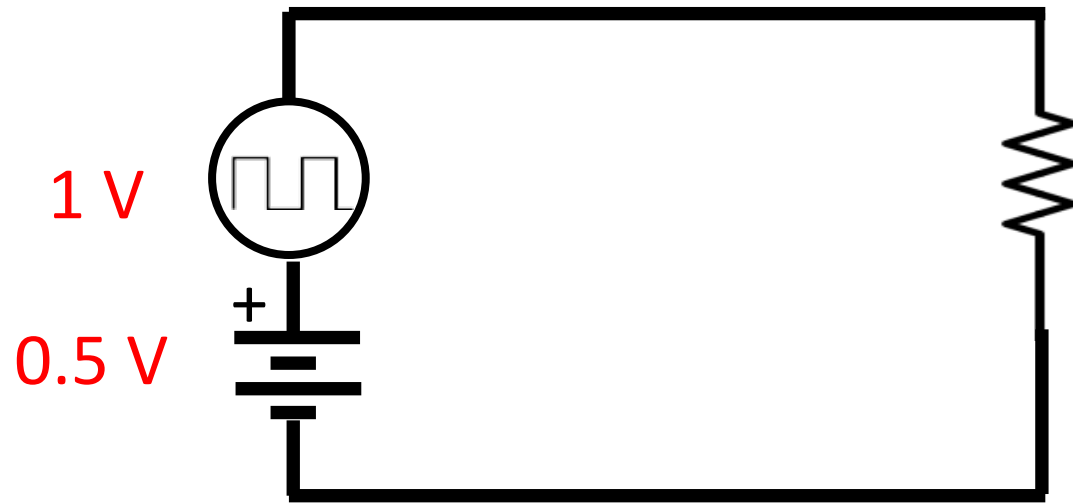


Triangle wave source

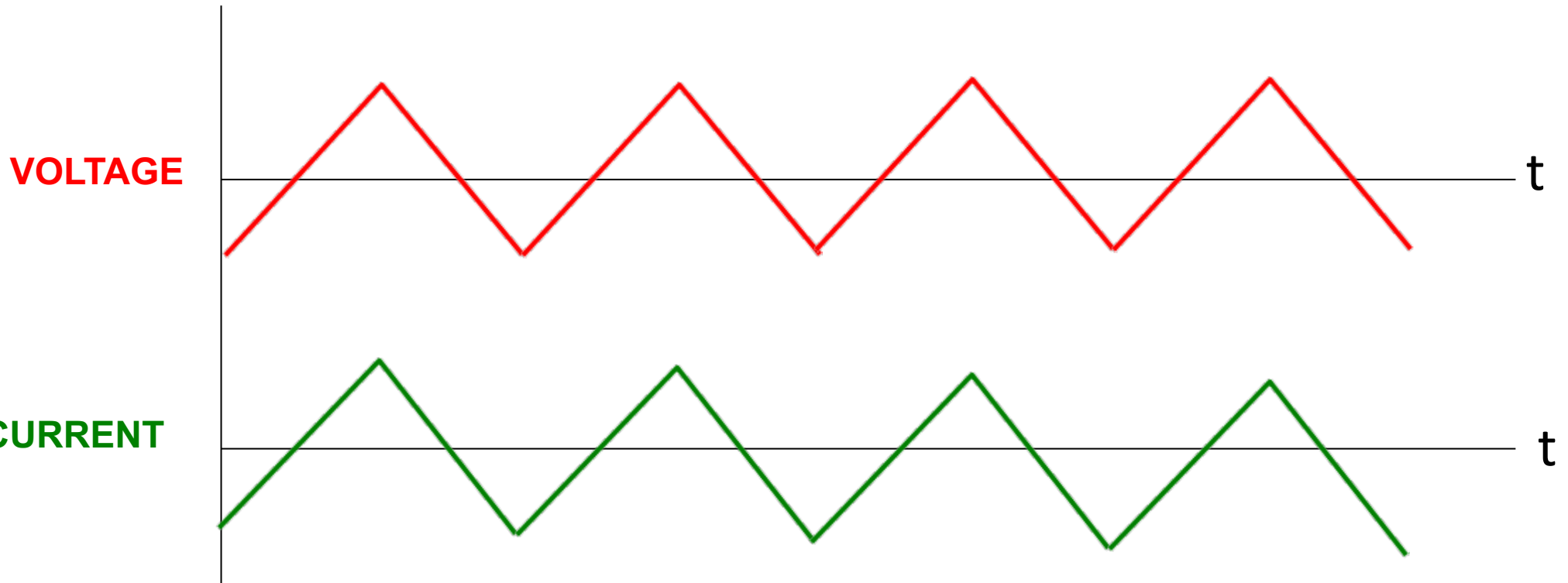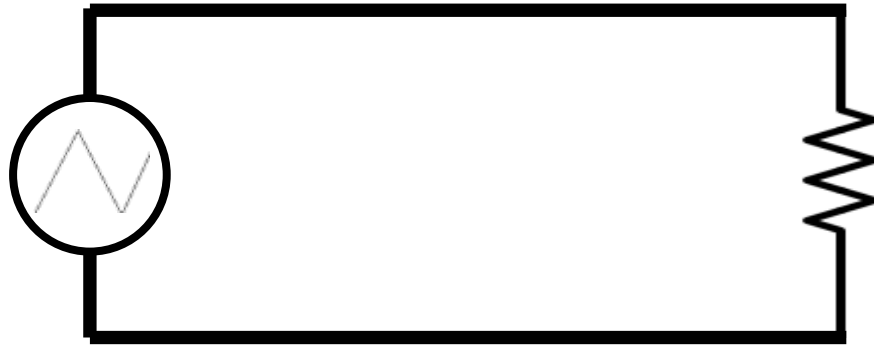

Sinusoidal wave source + dc offset

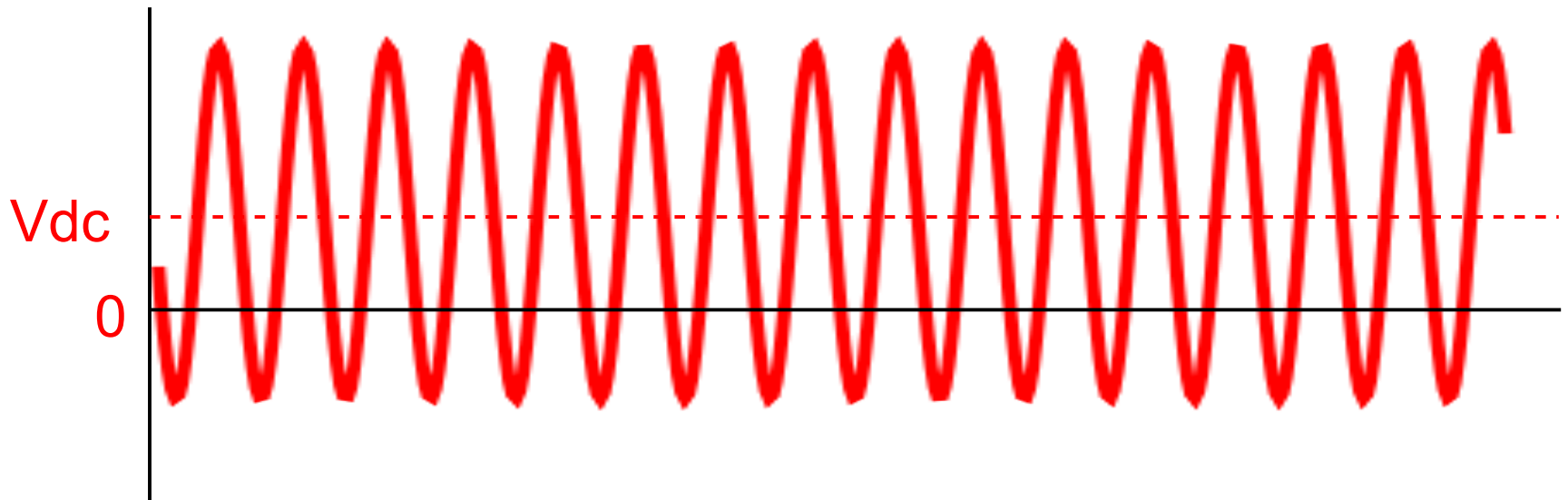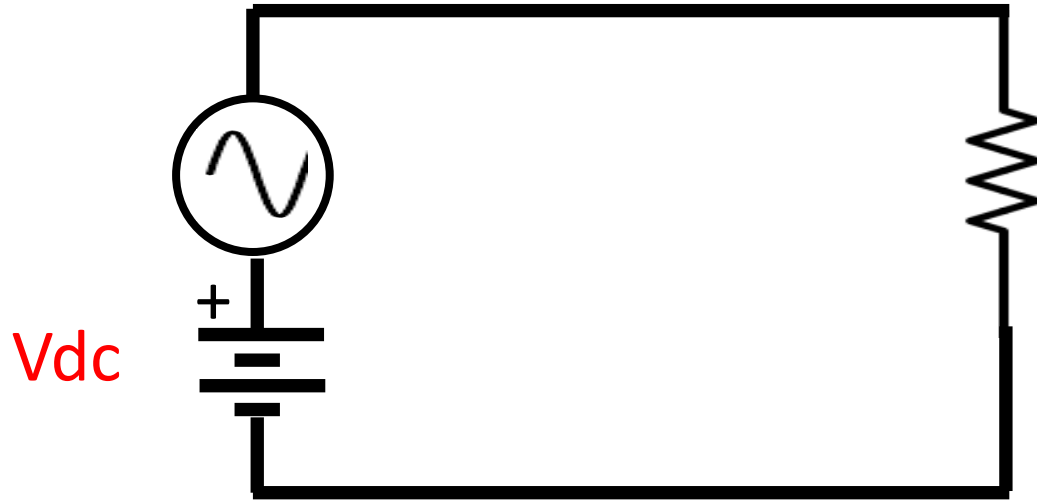

Characterizing an AC signal

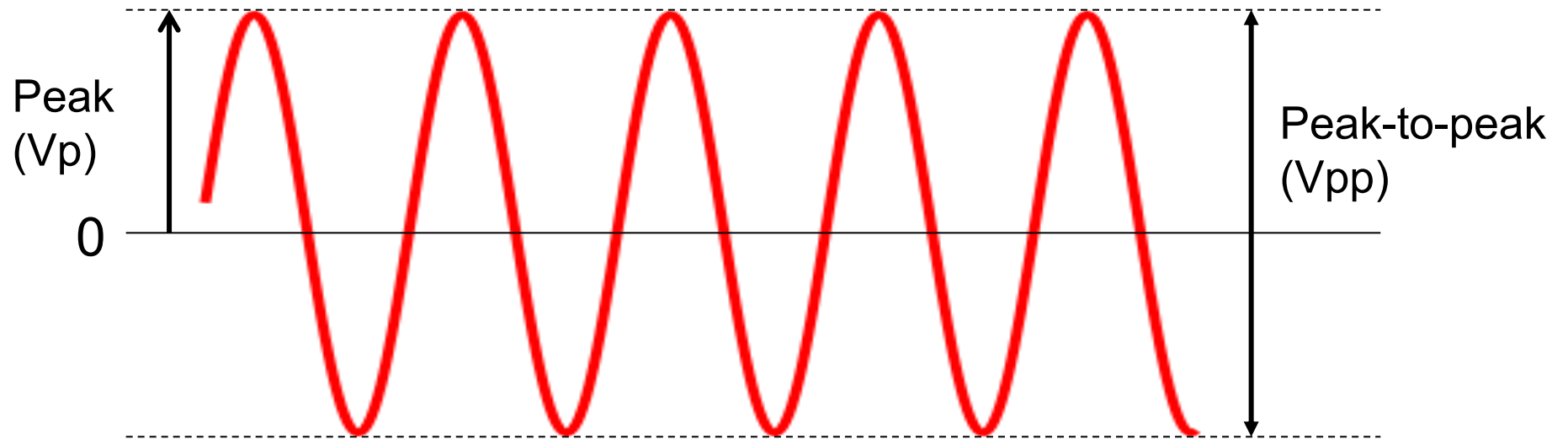

$$V(t) = V_p \sin(\omega t + \phi)$$

Root-mean-square (RMS)

Useful for determining power dissipated by an AC waveform

Allows comparison of power in AC and DC circuits



$$\text{POWER} = \frac{V_{dc}^2}{R}$$



$$\text{POWER} = \frac{V_{ac}^2}{R}$$

Root-mean-square (RMS)


Useful for determining power dissipated by an AC waveform

Allows comparison of power in AC and DC circuits







$$\text{POWER} = \frac{V_{ac}^2}{R} = \frac{V_p^2}{2R} \Rightarrow V_{RMS} = \frac{V_p}{\sqrt{2}}$$

OSCILLOSCOPE

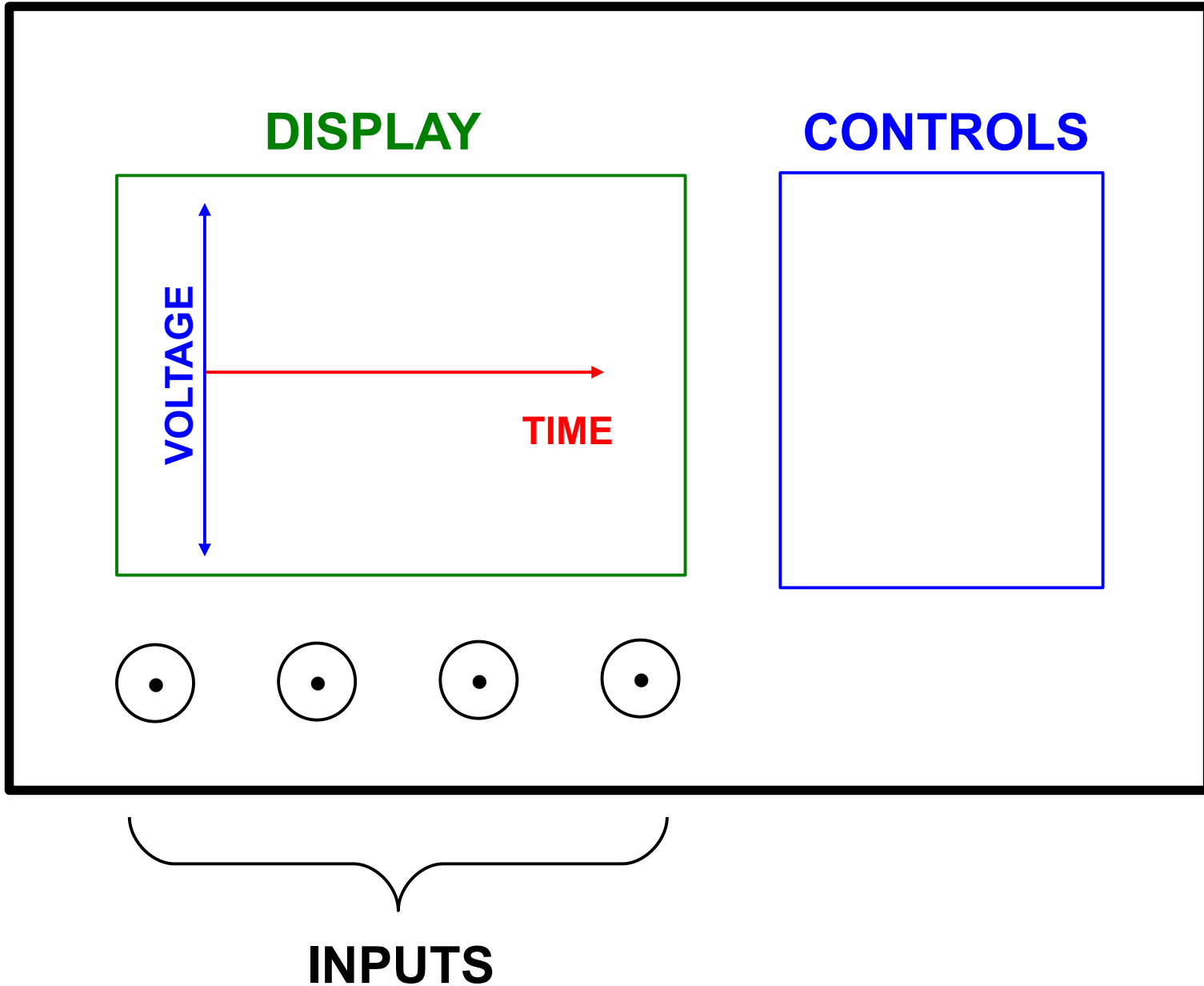

OSCILLOSCOPE

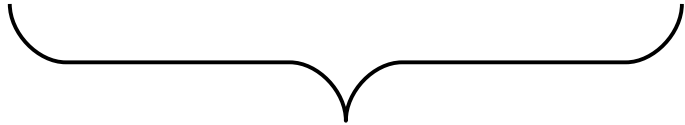 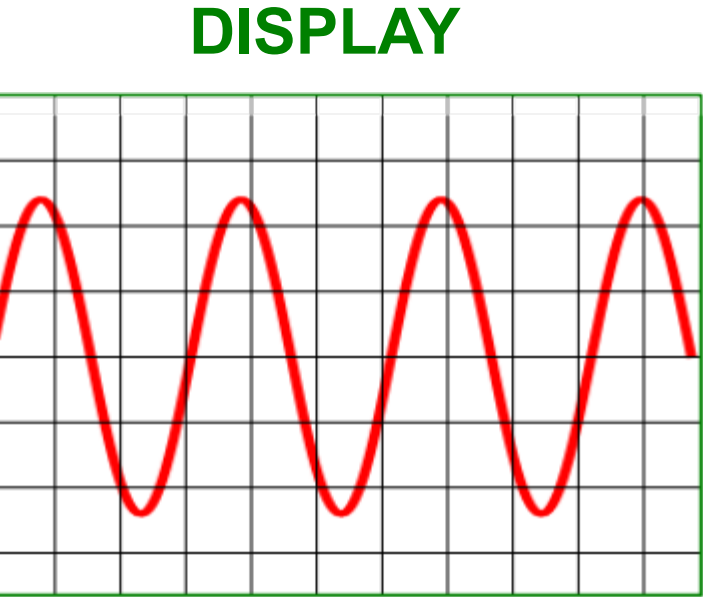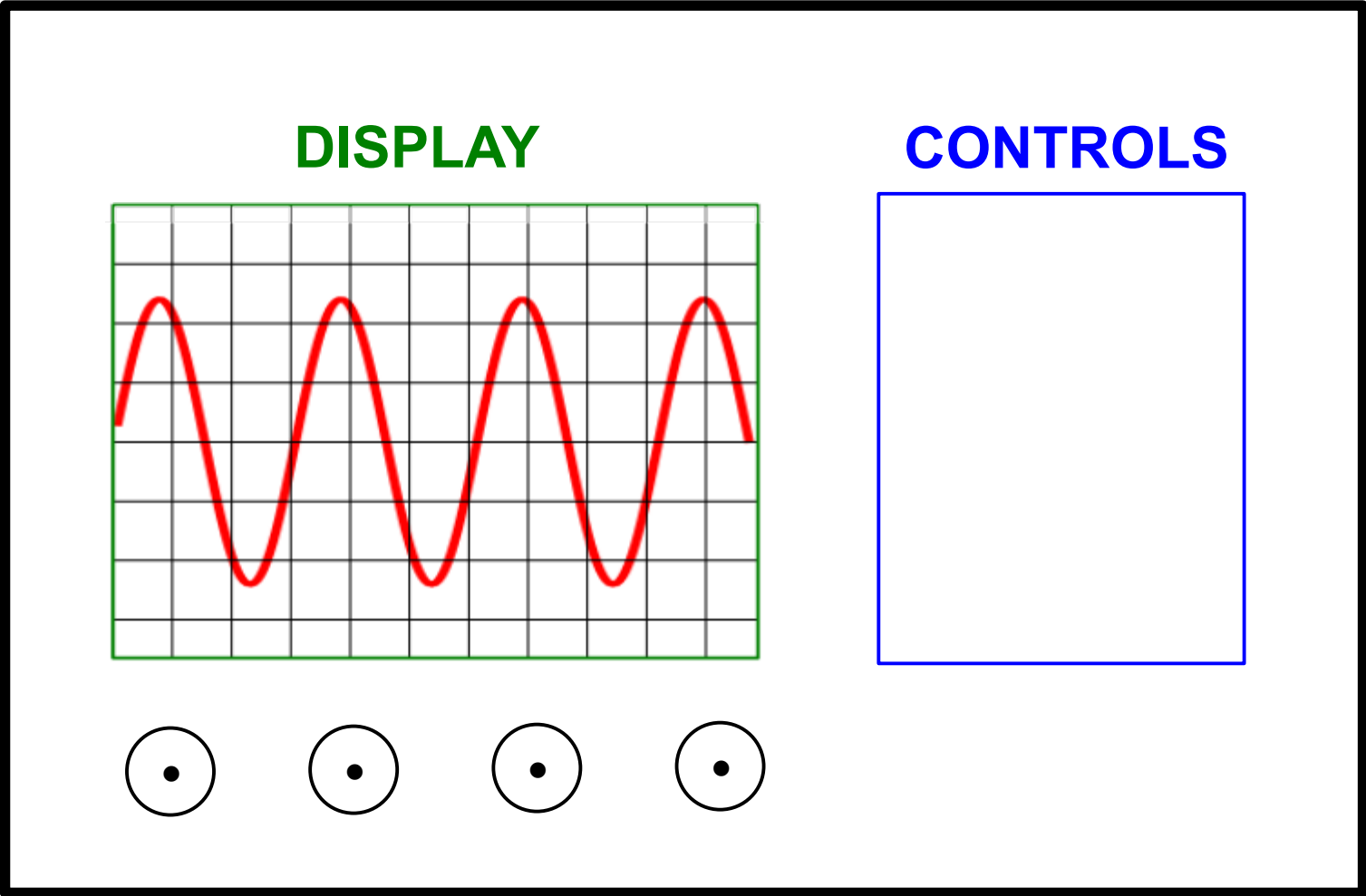


INPUTS

ANALOG: Cathode ray tube, swept electron beam


DIGITAL: A/D converter, LCD display

Although physical operation is completely different,
controls are nearly identical


DISPLAY ADJUSTMENT

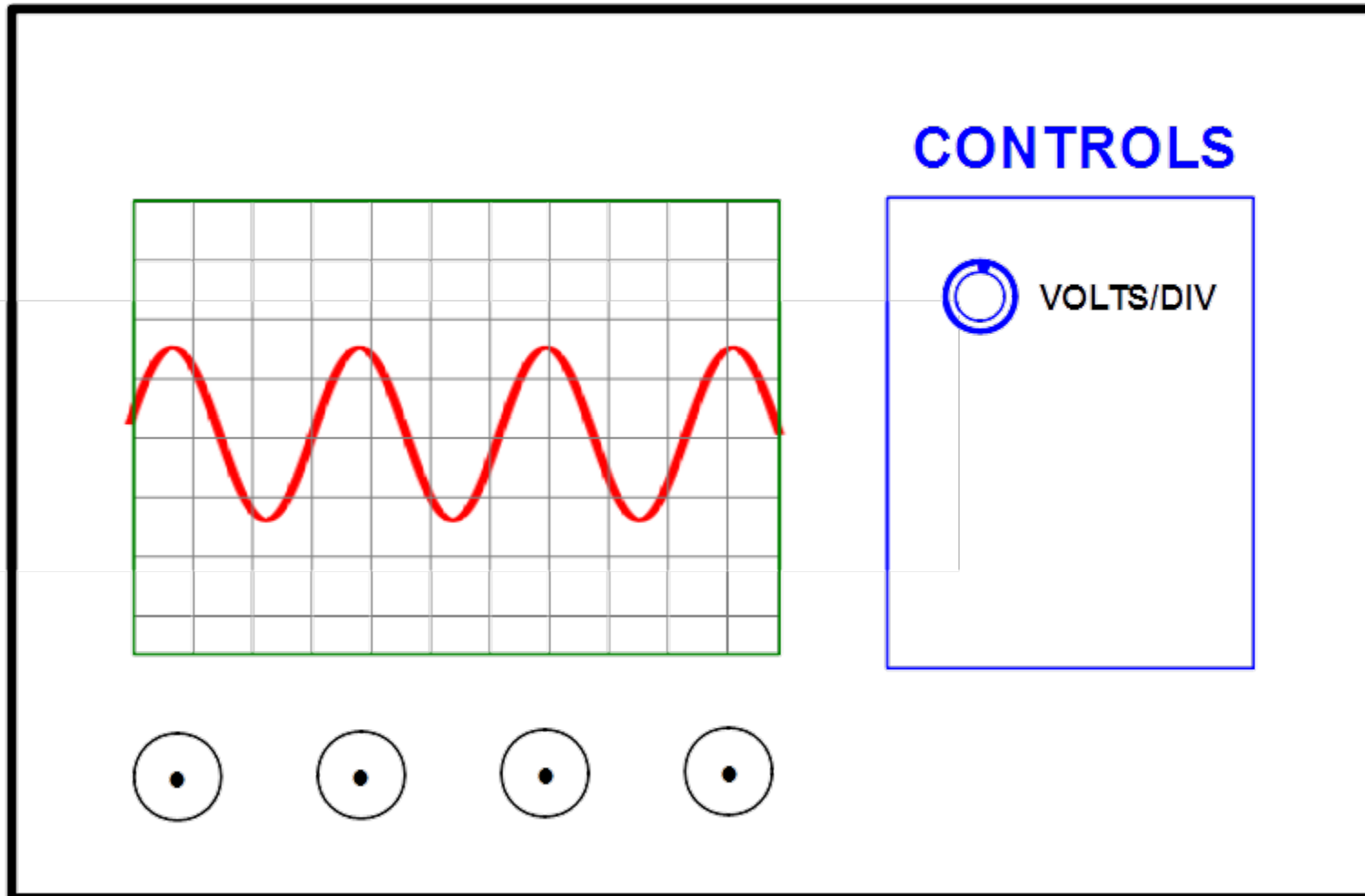


DISPLAY ADJUSTMENT

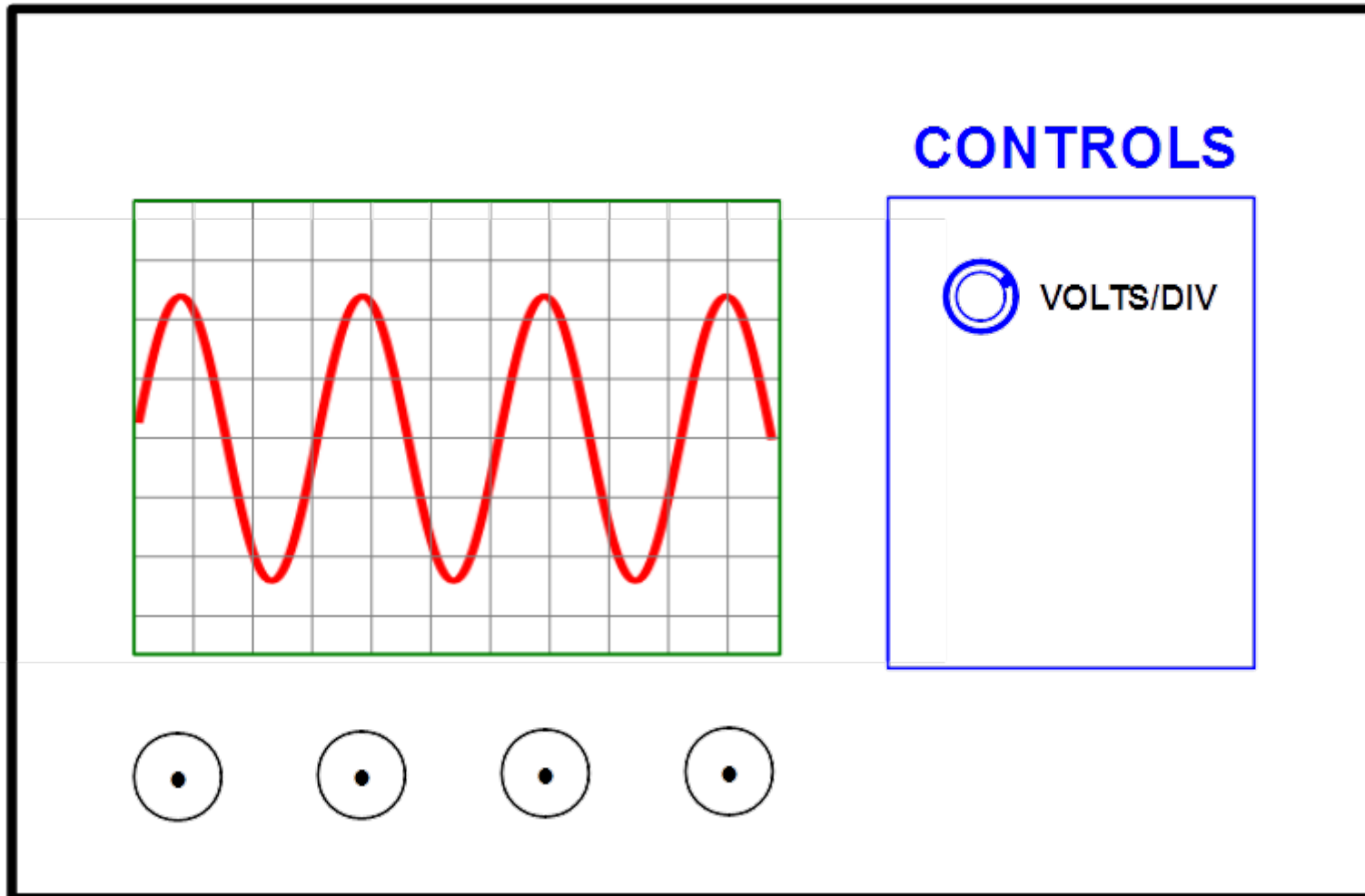


DISPLAY ADJUSTMENT

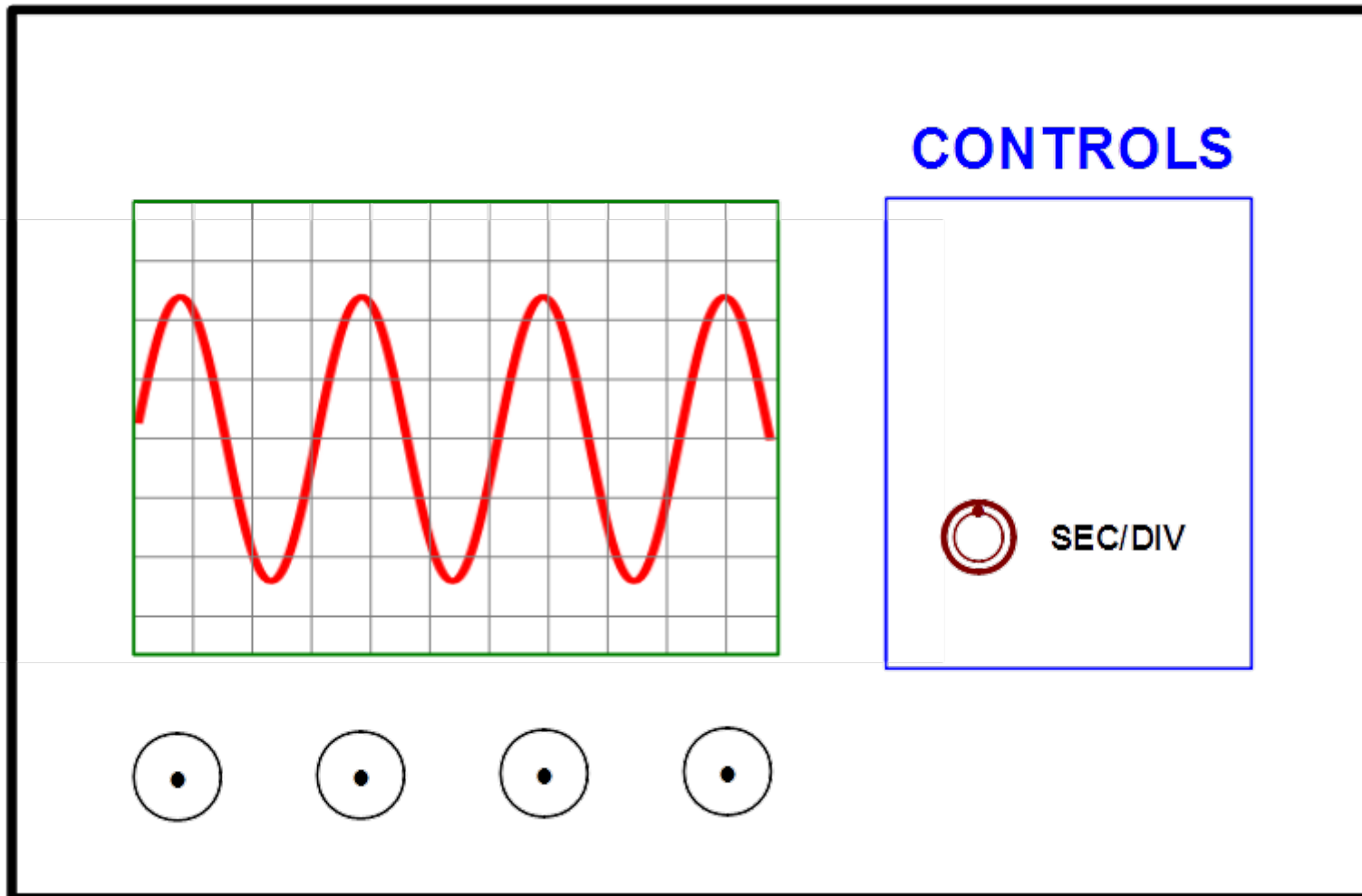



DISPLAY ADJUSTMENT

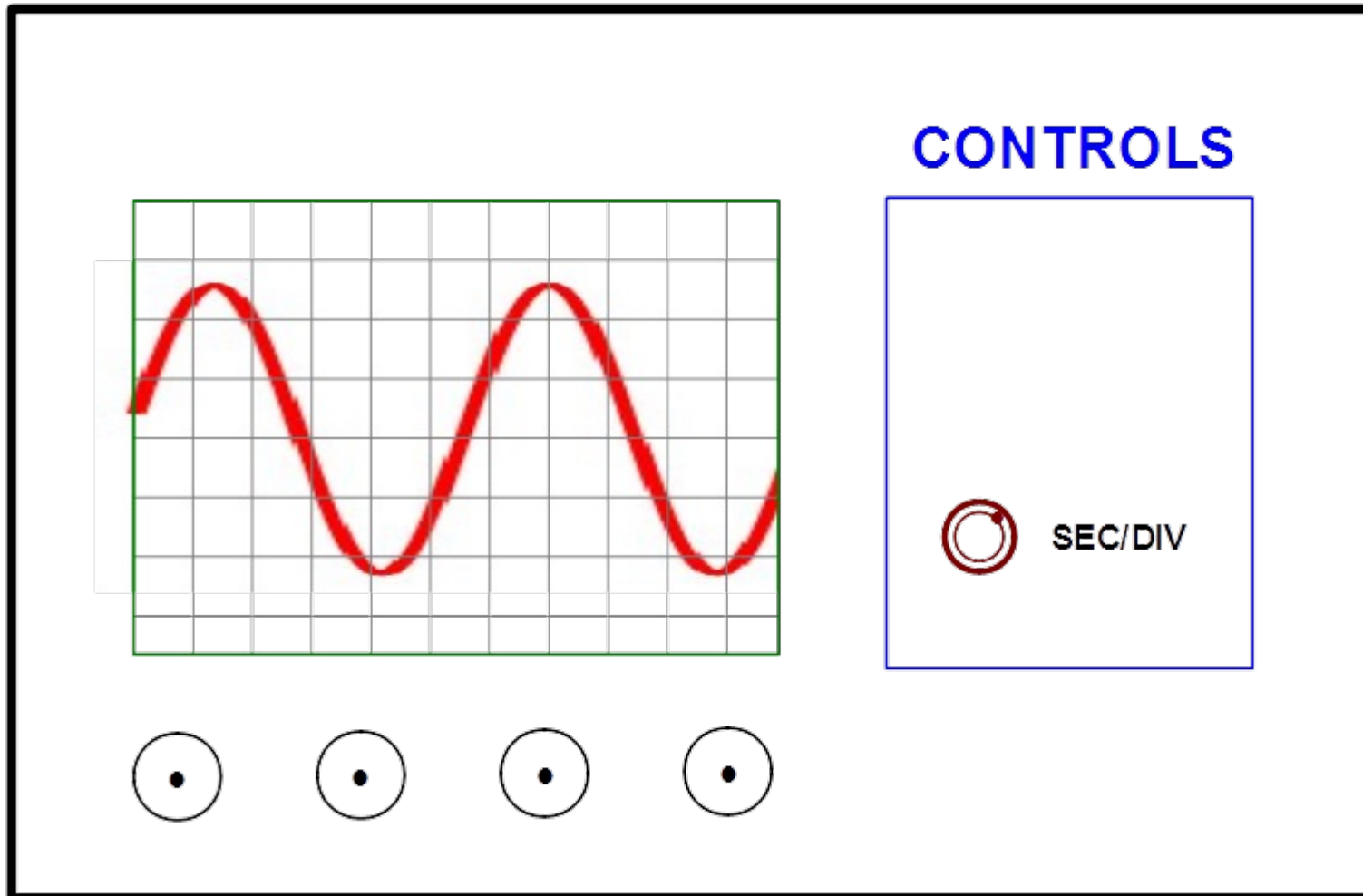


DC coupling, AC coupling, and Ground

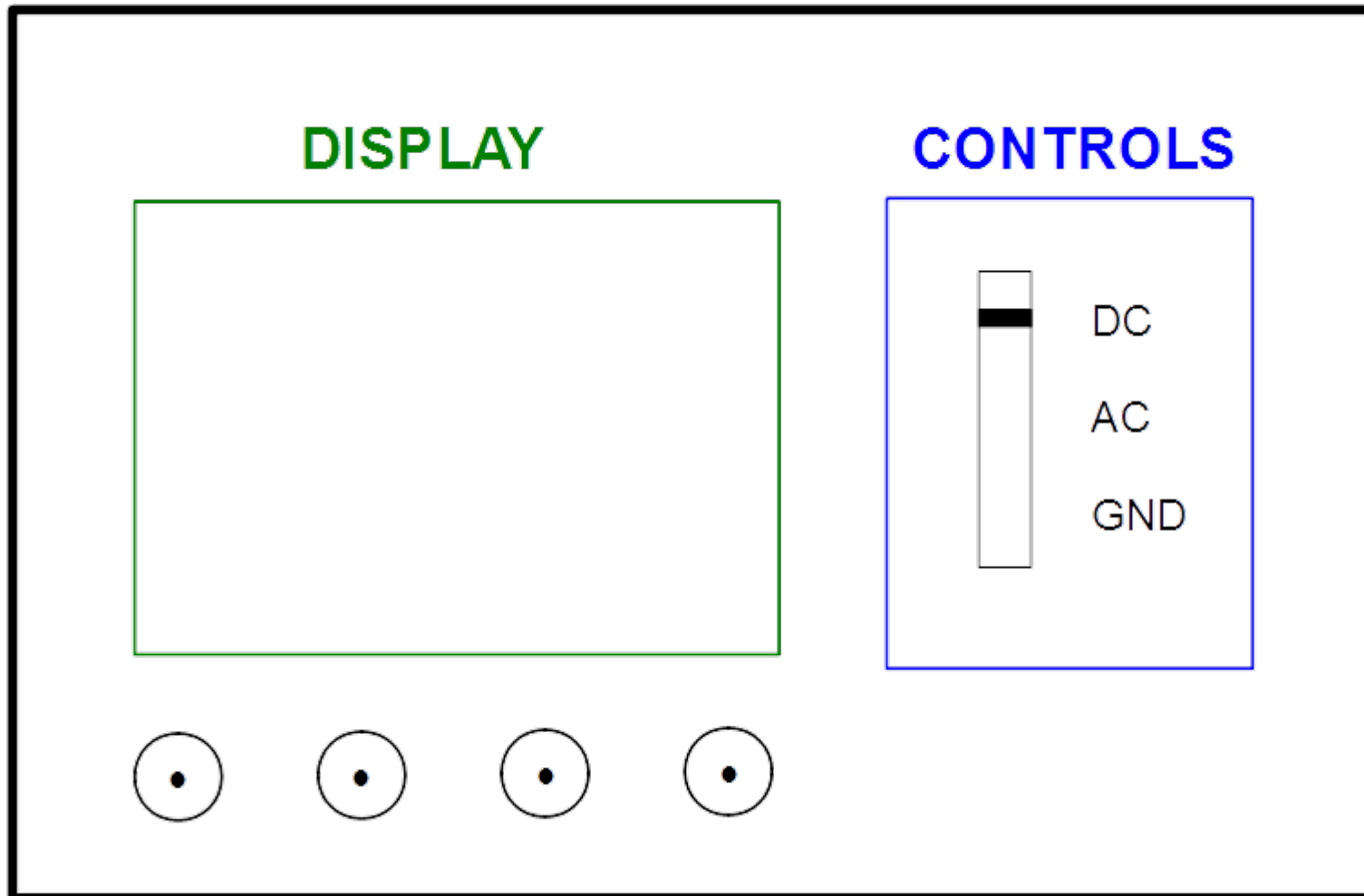


Sinusoidal wave source + dc offset

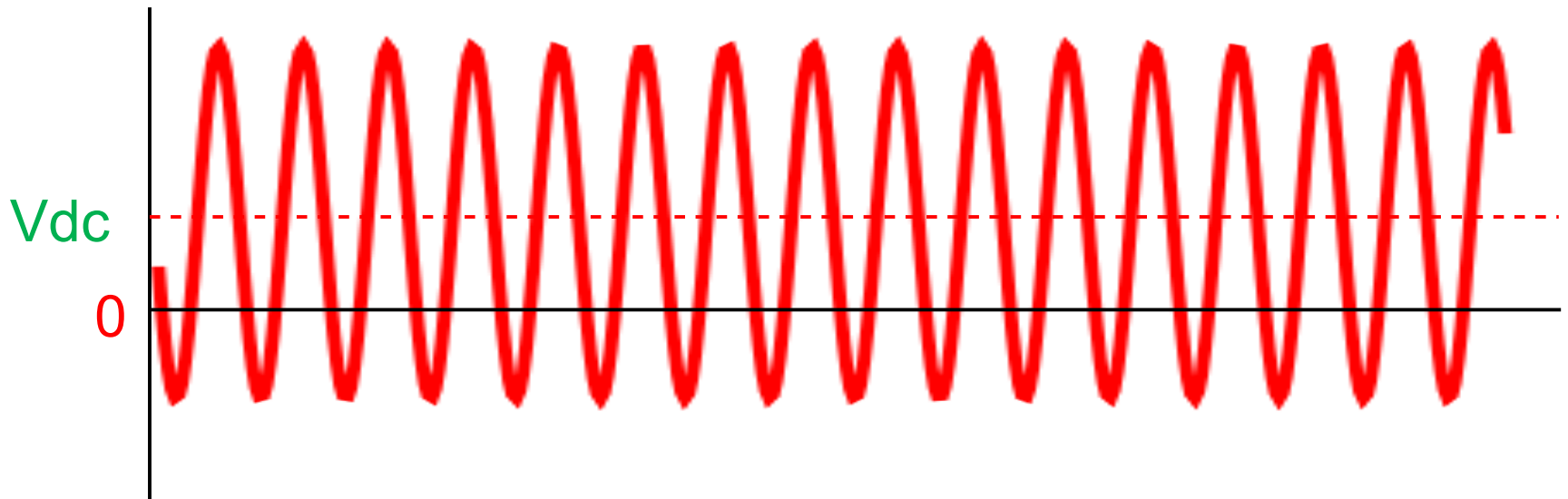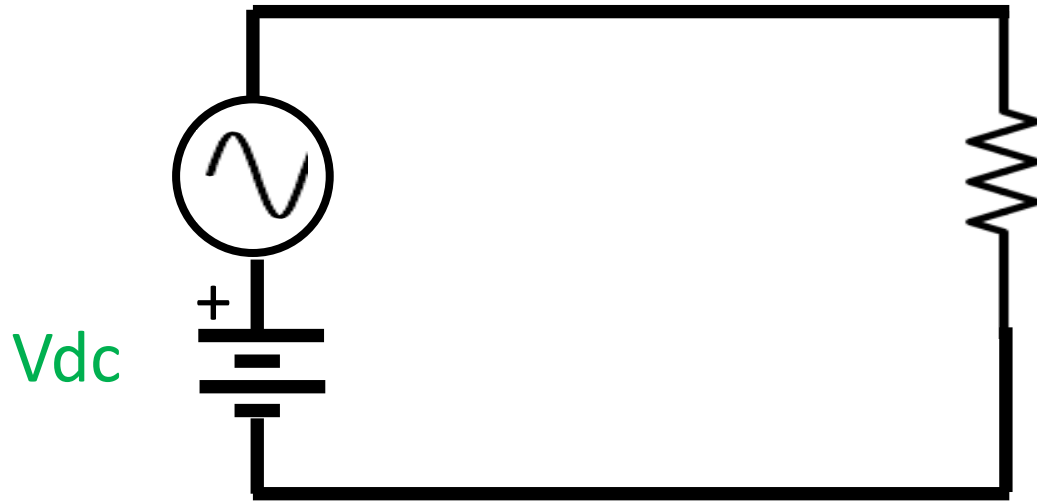


DC COUPLING

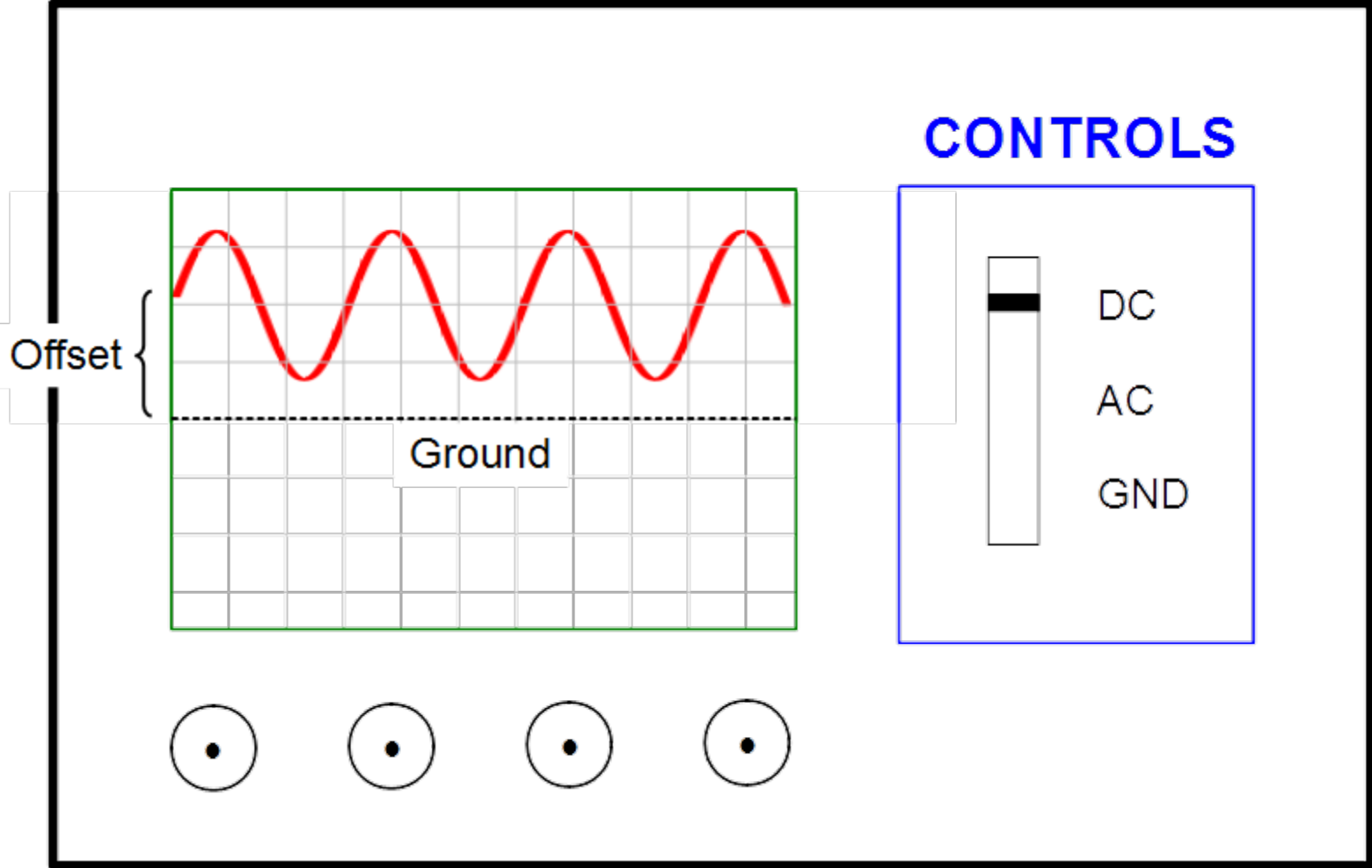


AC COUPLING

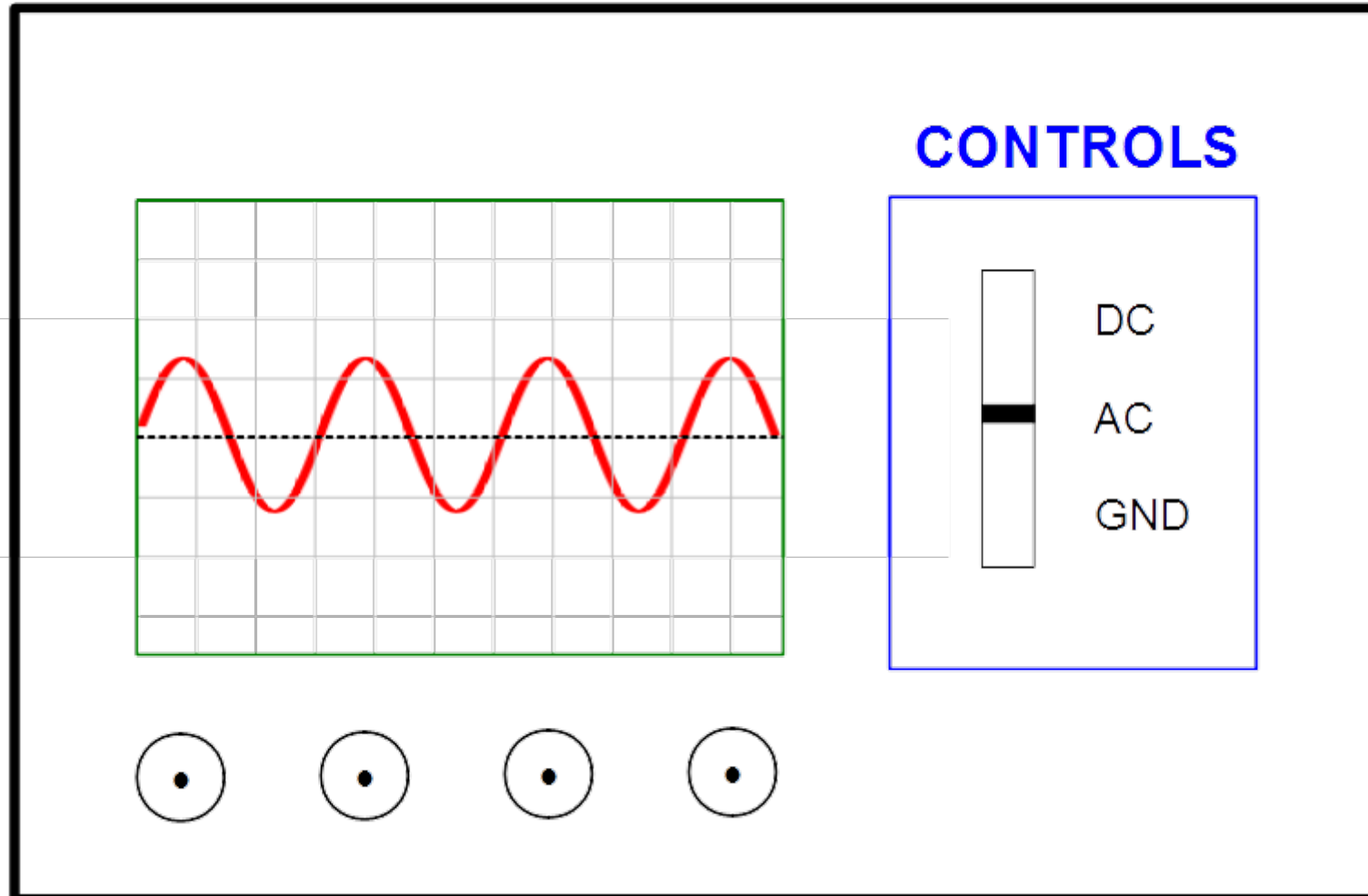


GROUND: Defines location of 0 Volts

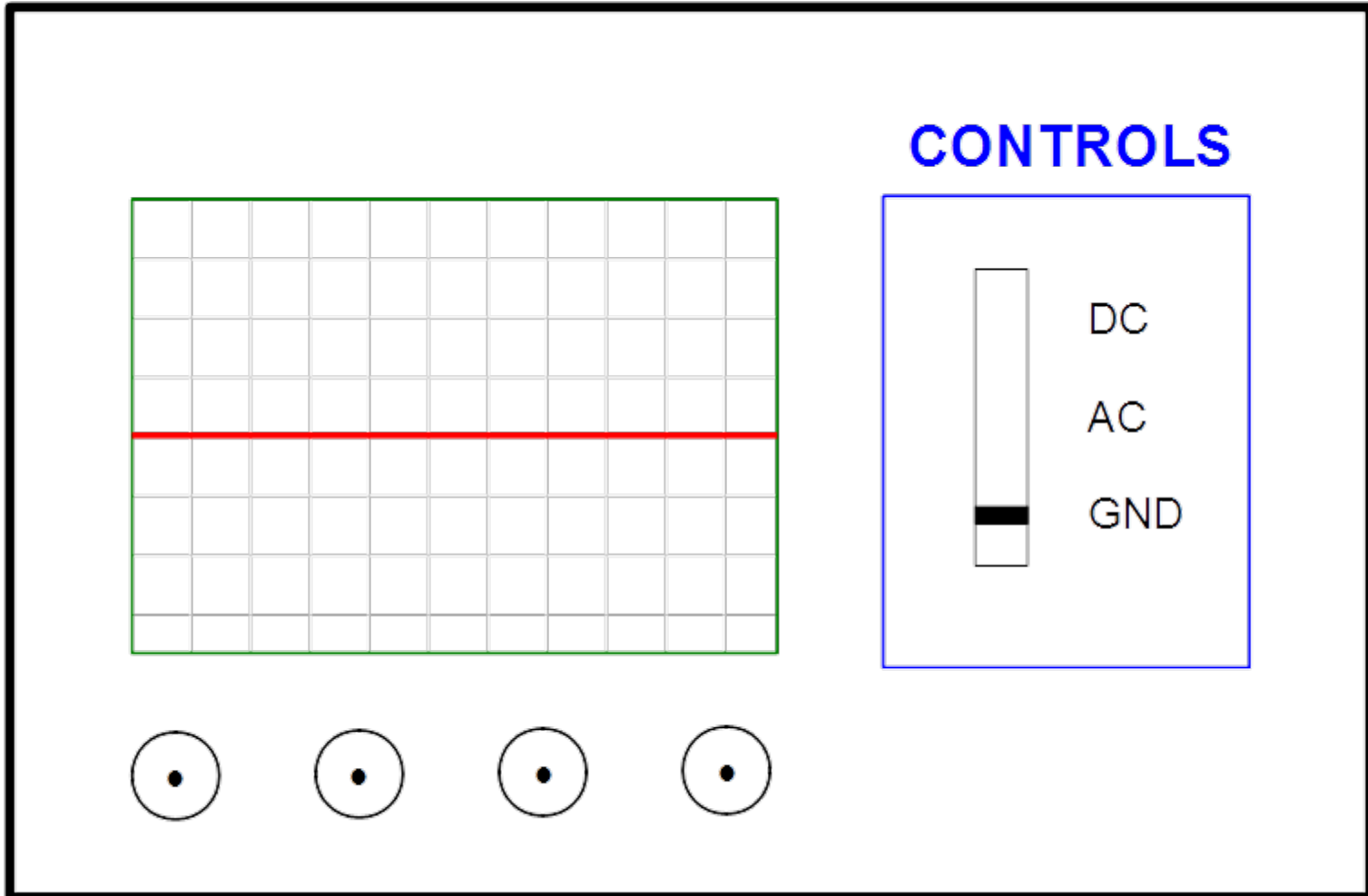

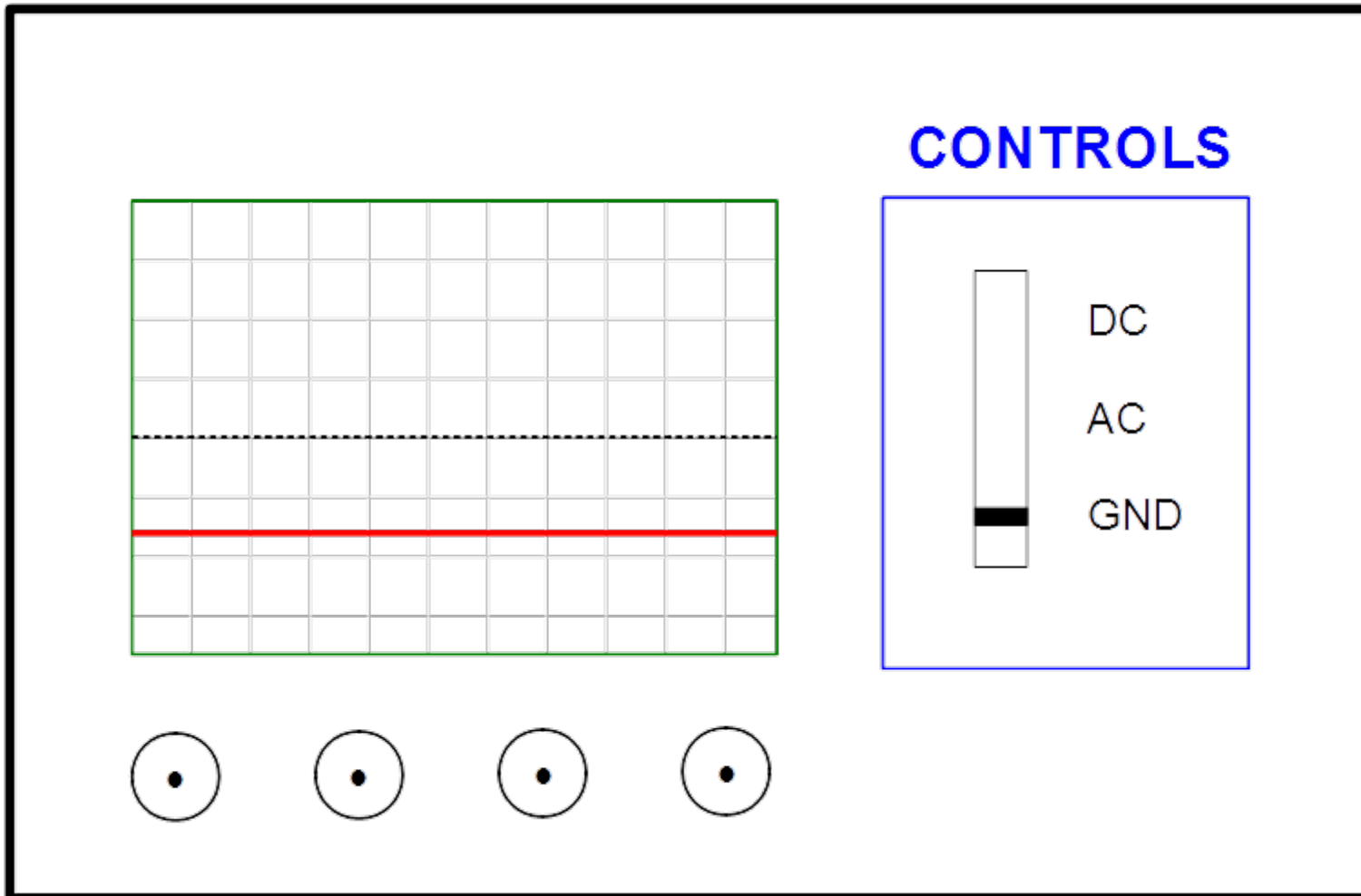
GROUND can be positioned at any convenient level




Trigger level

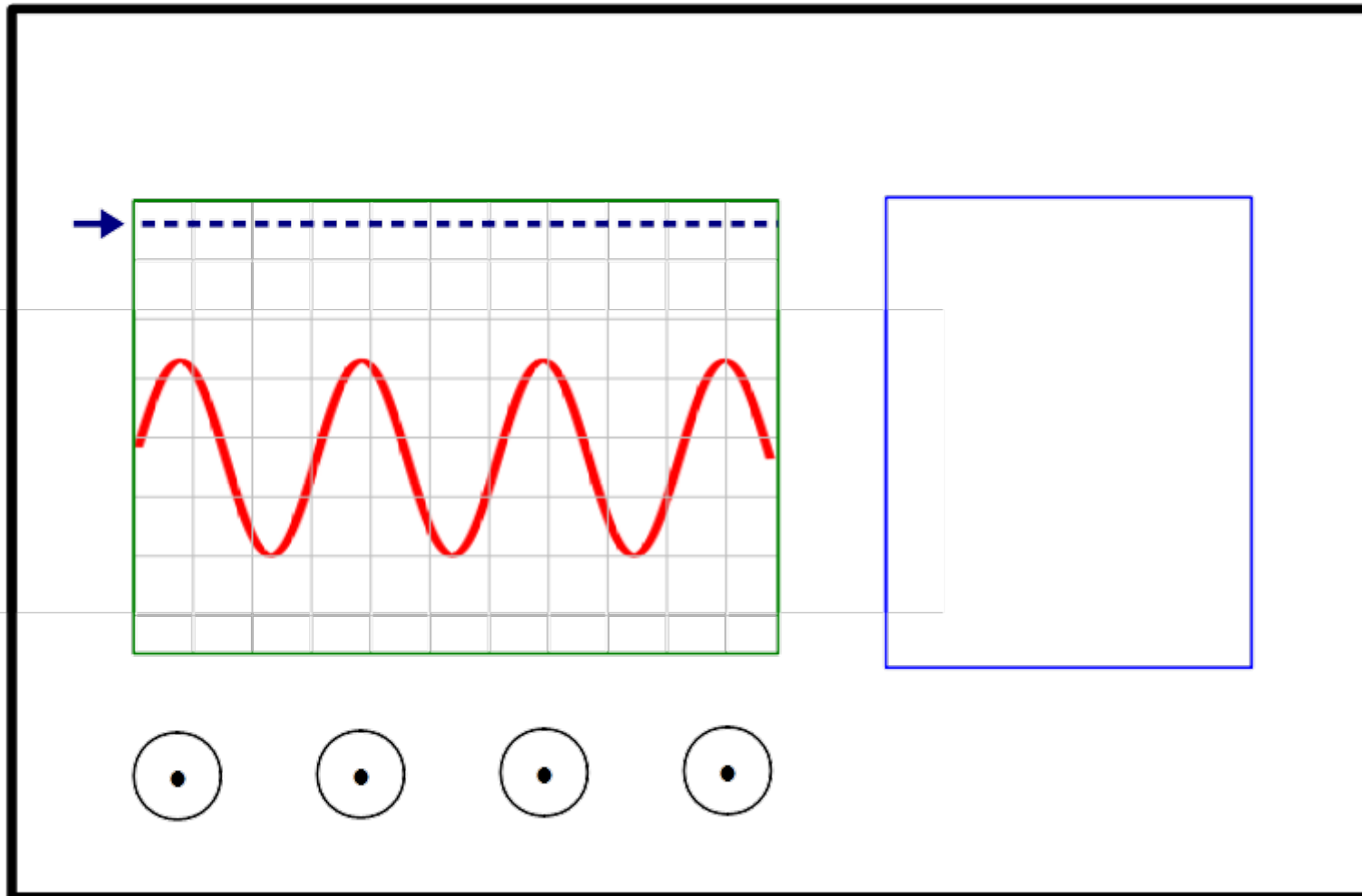

SAMPLING BANDWIDTH

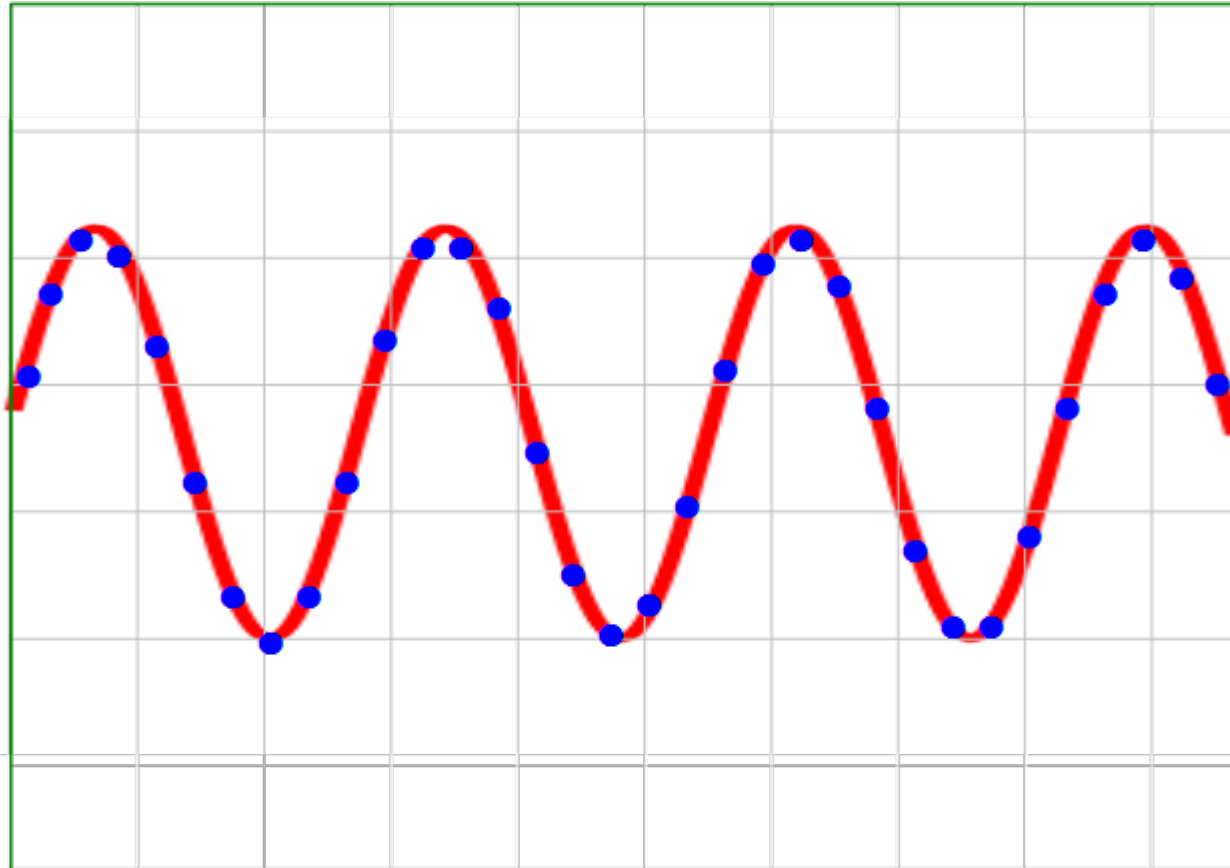


SAMPLING BANDWIDTH

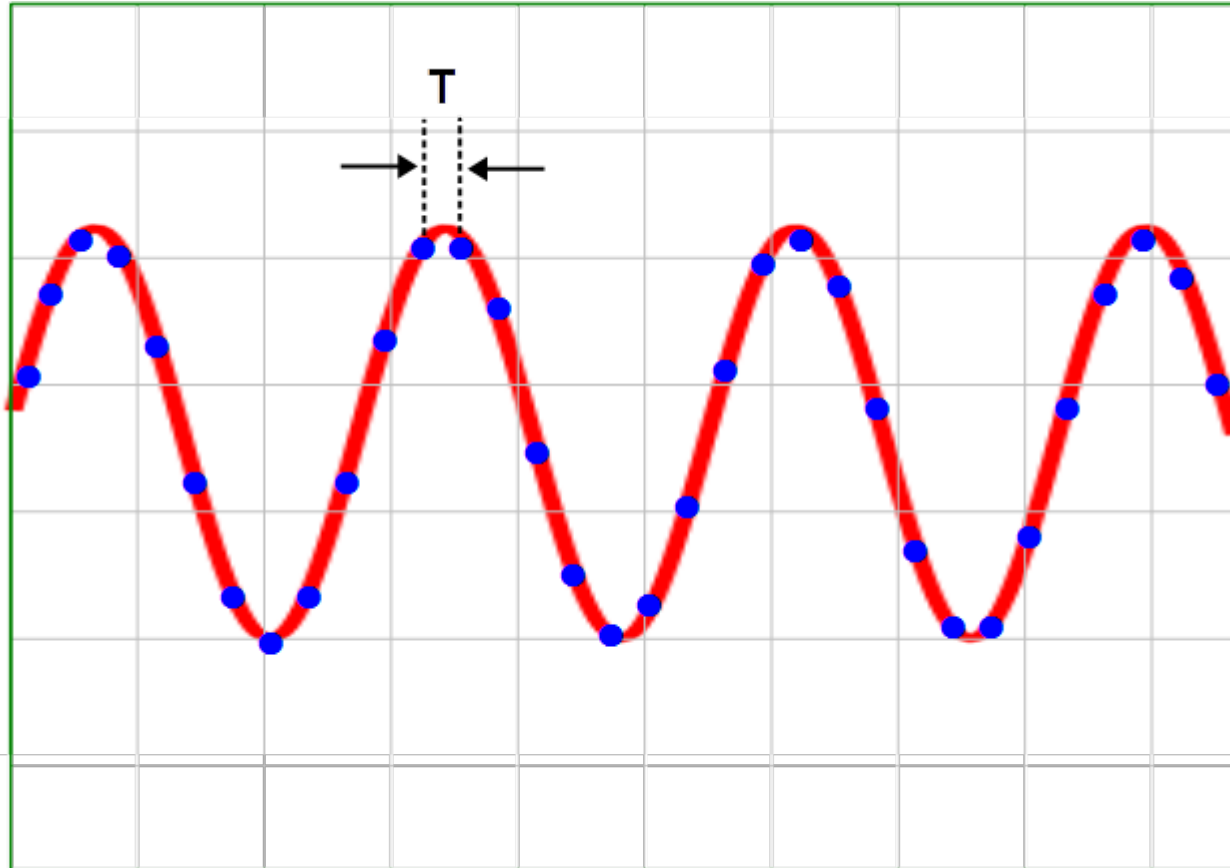

Sample spacing: T (sec)

Sampling bandwidth = $1 / T$ (samples/sec)


SAMPLING BANDWIDTH

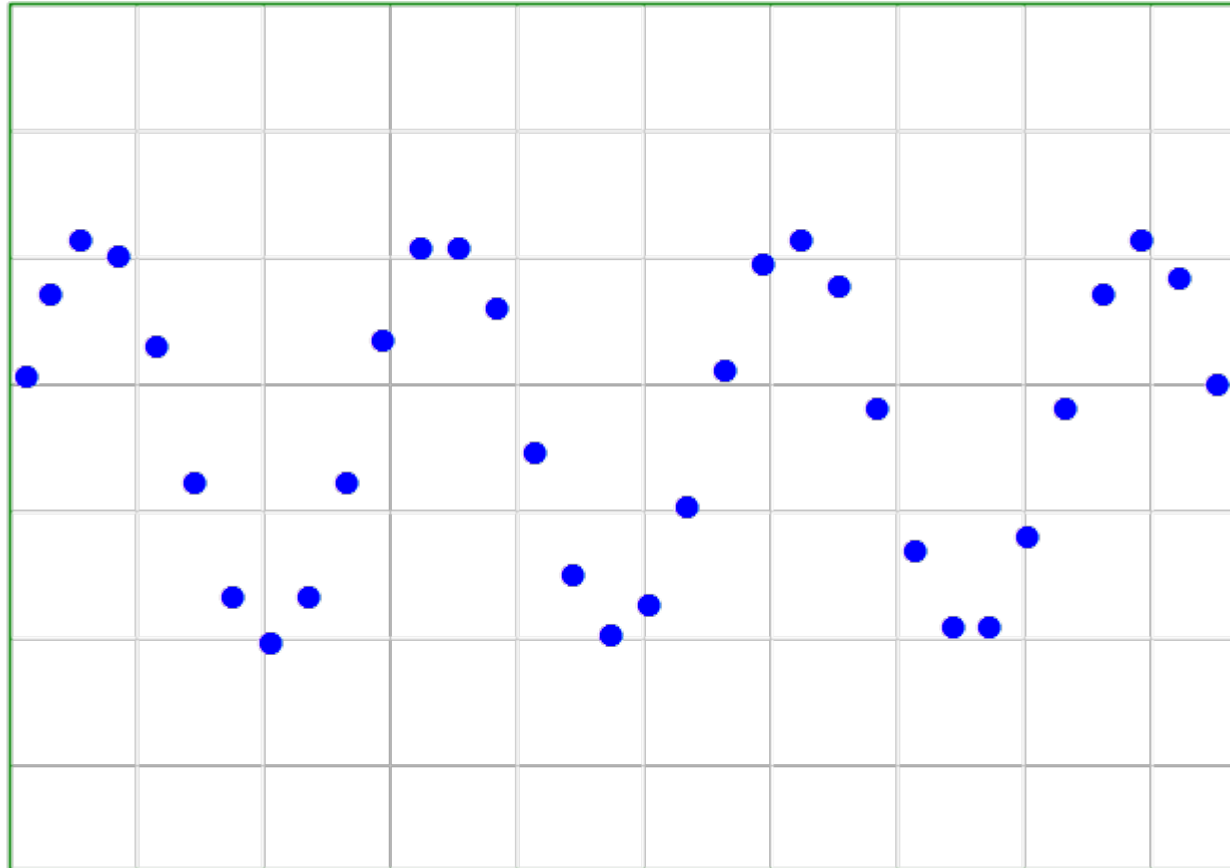

Sample spacing: T (sec)


Sampling bandwidth = $1 / T$ (samples/sec)

SAMPLING BANDWIDTH

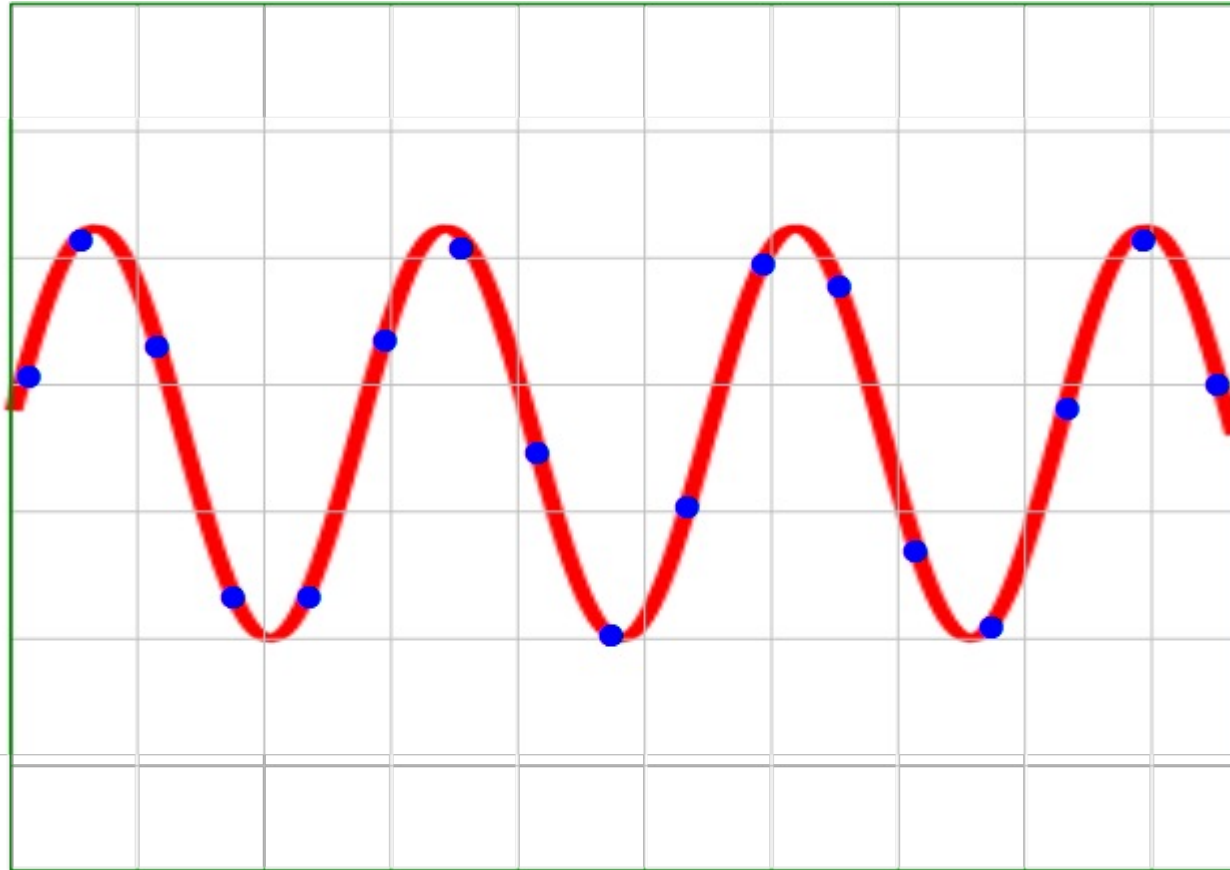

Reduce sample bandwidth 2x \Rightarrow Increase time spacing 2x

SAMPLING BANDWIDTH

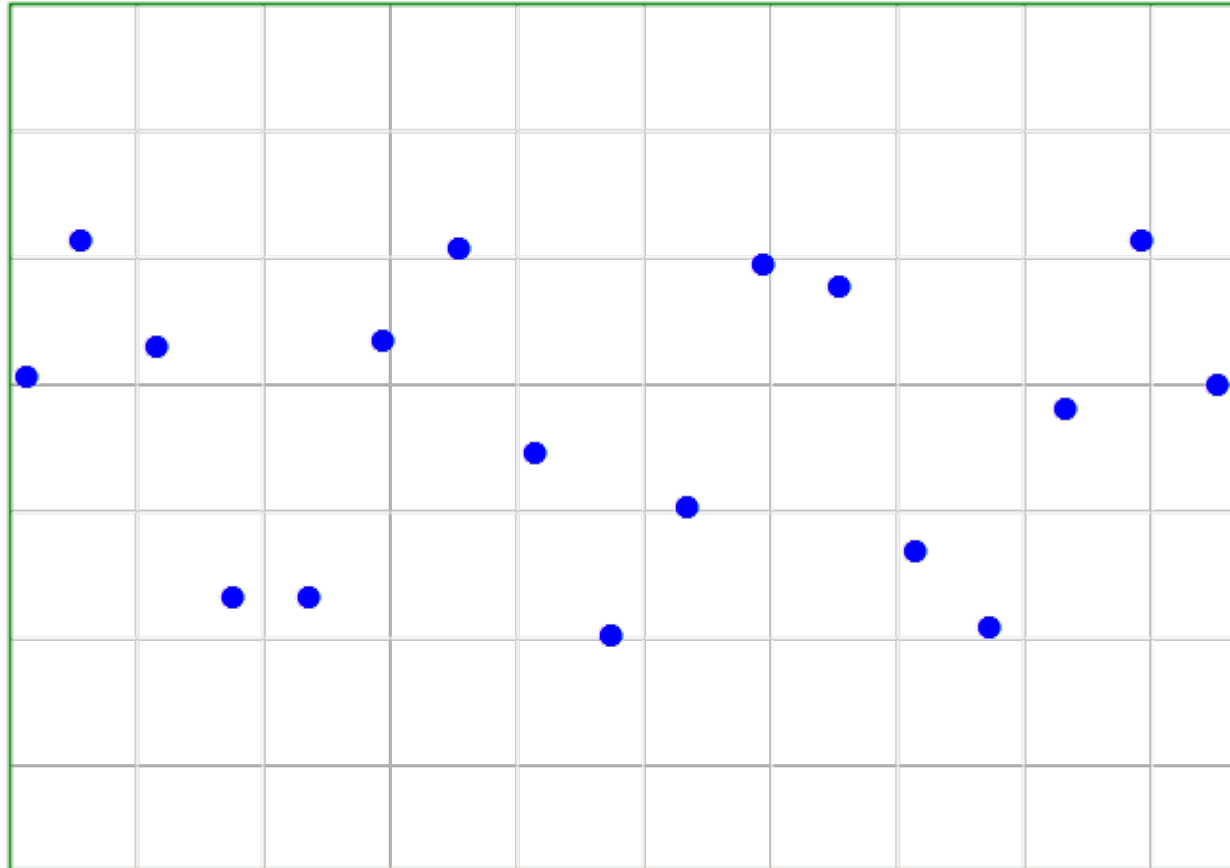

Reduce sample bandwidth $2x$ \Rightarrow Increase period $2x$

ANALOG BANDWIDTH \neq SAMPLING BANDWIDTH

