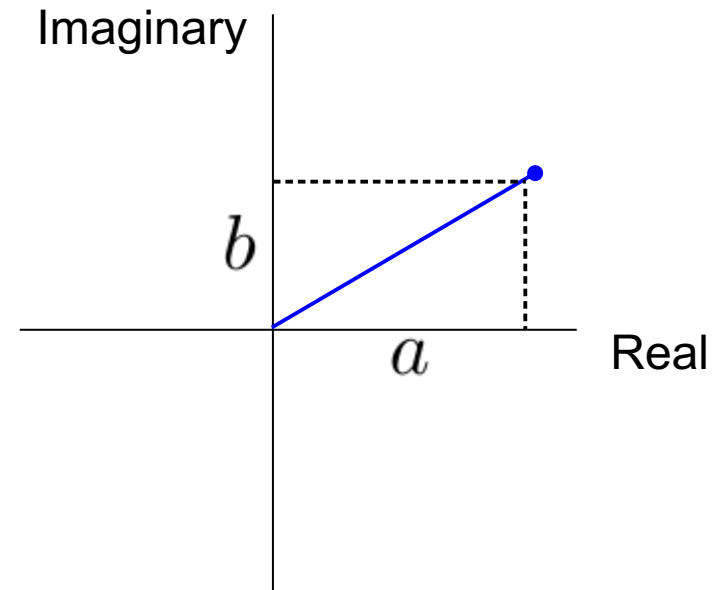


Lab 3: Capacitors and Inductors in AC circuits

Review of Complex Numbers

$$j = \sqrt{-1}$$

$$z = a + jb$$




Review of Complex Numbers

$$j = \sqrt{-1}$$

$$z = a + jb = Ae^{j\phi}$$

Amplitude $A = \sqrt{a^2 + b^2}$

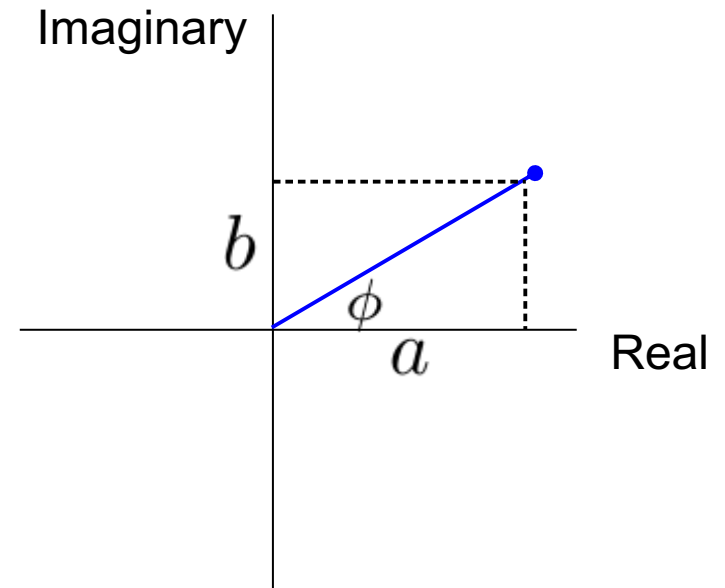Phase $\phi = \tan^{-1} \left(\frac{b}{a} \right)$




Review of Complex Numbers

$$j = \sqrt{-1}$$

$$z = a + jb = Ae^{j\phi}$$

Amplitude $A = \sqrt{a^2 + b^2}$

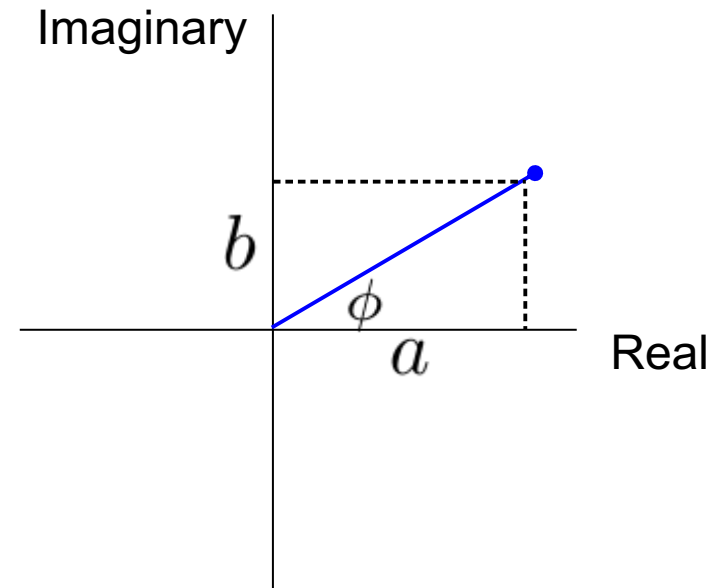Phase $\phi = \tan^{-1} \left(\frac{b}{a} \right)$



Phaseshift


$$e^{j\phi} = \cos \phi + j \sin \phi$$

$$e^{j\frac{\pi}{2}} = \cos\left(\frac{\pi}{2}\right) + j \sin\left(\frac{\pi}{2}\right) = j$$

OUR ESSENTIAL WORKING ASSUMPTION:

AC \equiv SINUSOIDAL FUNCTION

$$V(t) = A \sin(\omega t + \phi)$$

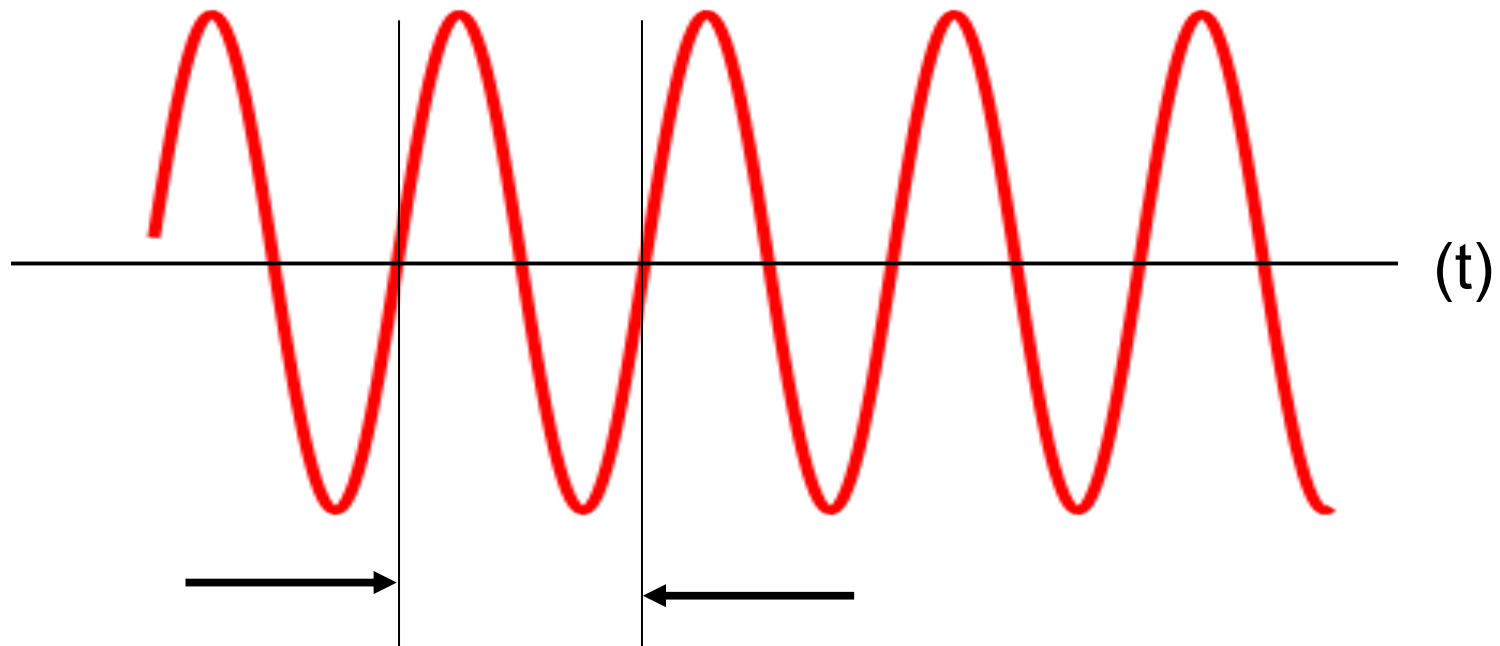

T: Period

Frequency: $f = 1/T$

Capacitor in AC circuit

$$V_{ac} = V_o \sin \omega t$$

$$\omega = 2\pi f$$

ω : radians/sec

f : Herz (1/sec)



Capacitor in AC circuit

$$V_{ac} = V_0 \sin \omega t$$




$$\omega = 2\pi f$$


ω : radians/sec
 f : Herz (1/sec)

$$V(t) = V_0 \sin(\omega t + \phi_0) \quad \text{VOLTAGE}$$

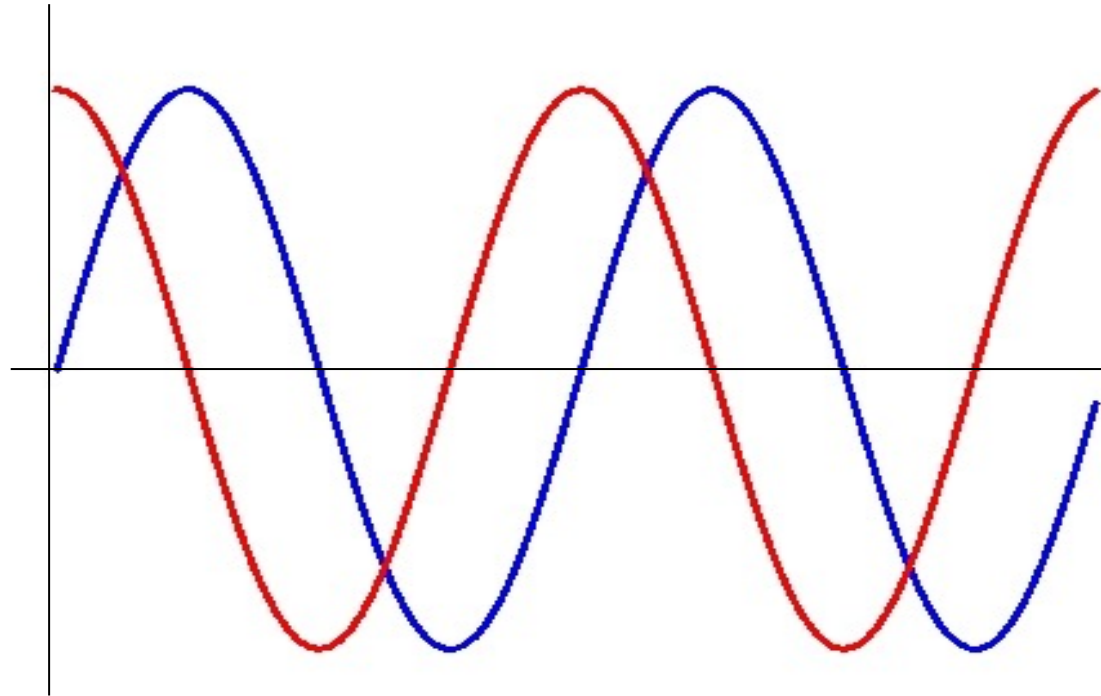
$$I(t) = I_0 \sin(\omega t + \phi_1) \quad \text{CURRENT}$$



Inductor in AC circuit

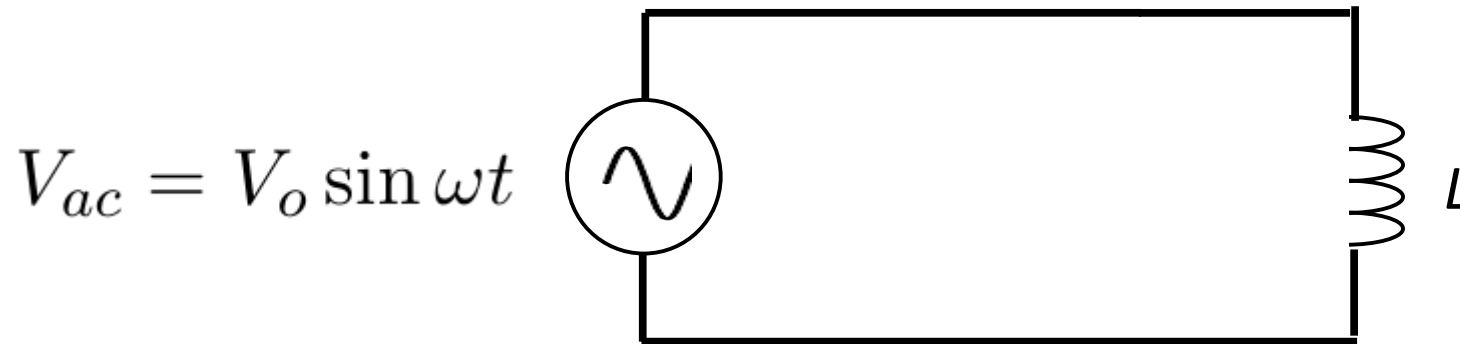


Inductor in AC circuit

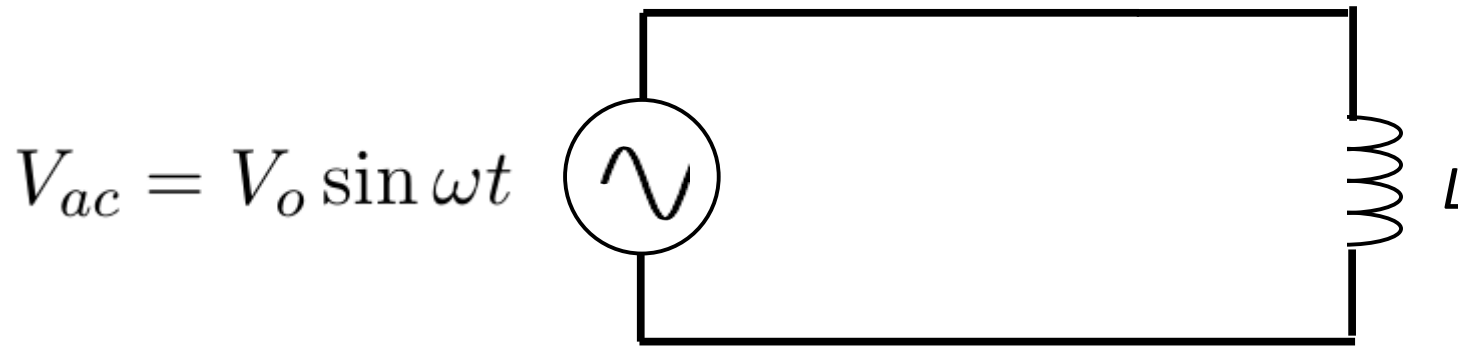


$V(t) = V_o \sin(\omega t + \phi_0)$ **VOLTAGE**

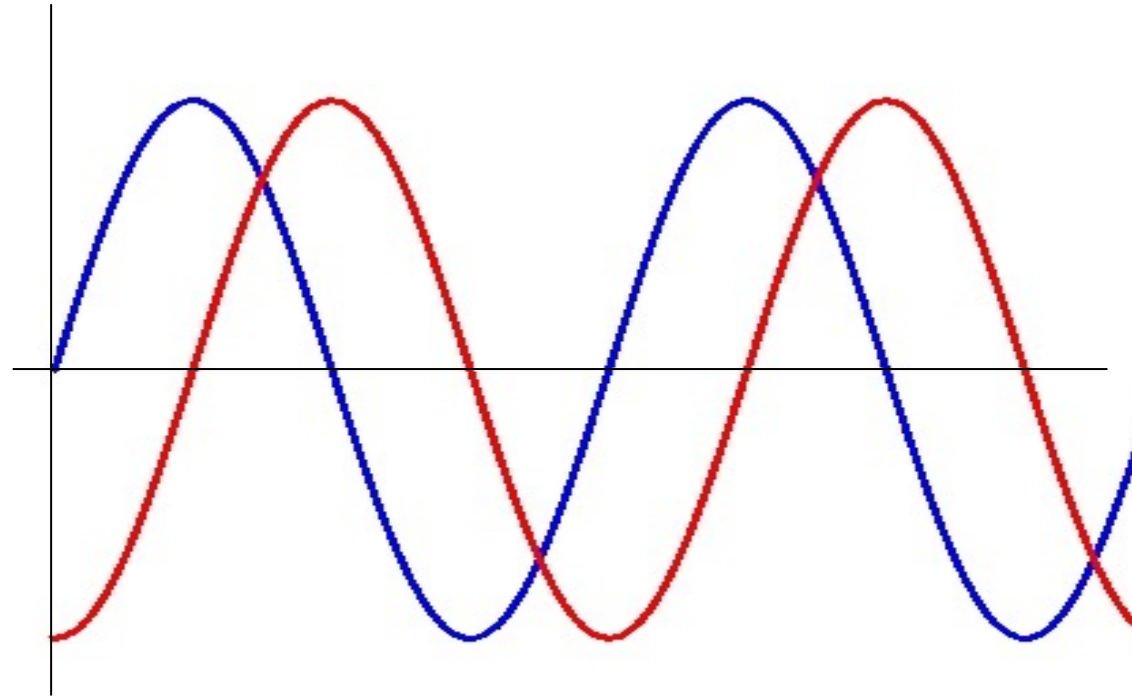$I(t) = I_o \sin(\omega t + \phi_1)$ **CURRENT**



Ohm's Law for L and C: Impedance (Z)

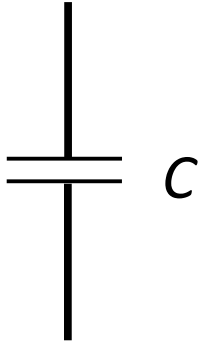


$(Q = CV)$

$$Z_C = \frac{V_C}{I_C} = \frac{V_o \sin \omega t}{\omega C V_o \cos \omega t} = \frac{V_o \sin \omega t}{\omega C V_o \sin \left(\omega t + \frac{\pi}{2} \right)}$$


$$V(t) = V_o \sin(\omega t + \phi_0)$$

$$I(t) = I_o \sin(\omega t + \phi_1)$$

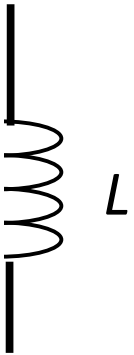

$(V = L di/dt)$

Ohm's Law for L and C: Impedance (Z)

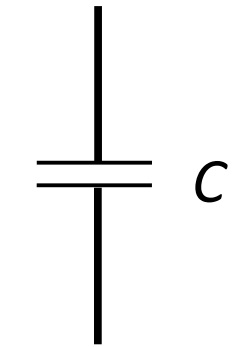


C

$(Q = CV)$

$$Z_C = \frac{V_C}{I_C} = \frac{V_o \sin \omega t}{\omega C V_o \cos \omega t} = \frac{V_o \sin \omega t}{\omega C V_o \sin \left(\omega t + \frac{\pi}{2} \right)}$$

$$V(t) = V_o \sin(\omega t + \phi_0)$$

$$I(t) = I_o \sin(\omega t + \phi_1)$$

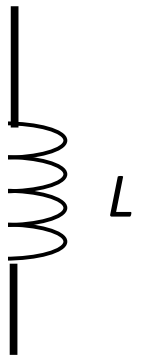


L

$(V = L di/dt)$

$$Z_L = \frac{V_L}{I_L} = \frac{V_o \sin \omega t}{-(V_o/\omega L) \cos \omega t} = \frac{V_o \sin \omega t}{-(V_o/\omega L) \sin \left(\omega t + \frac{\pi}{2} \right)}$$

Ohm's Law for L and C: Impedance (Z)

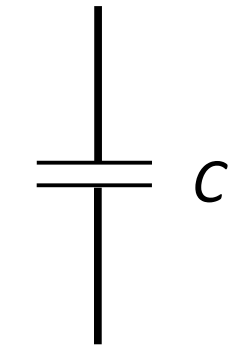

C


$$(Q = CV)$$

$$Z_C = \frac{V_C}{I_C} = \frac{V_o \sin \omega t}{\omega C V_o \cos \omega t} = \frac{V_o \sin \omega t}{\omega C V_o \sin \left(\omega t + \frac{\pi}{2} \right)}$$

$$V(t) = V_o \sin(\omega t + \phi_0)$$

$$I(t) = I_o \sin(\omega t + \phi_1)$$

90° phase shift

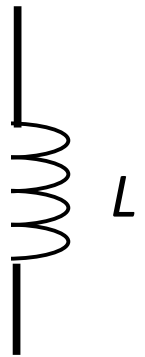


L

$$(V = L di/dt)$$


$$Z_L = \frac{V_L}{I_L} = \frac{V_o \sin \omega t}{-(V_o/\omega L) \cos \omega t} = \frac{V_o \sin \omega t}{-(V_o/\omega L) \sin \left(\omega t + \frac{\pi}{2} \right)}$$

90° phase shift

Ohm's Law for L and C: Impedance (Z)

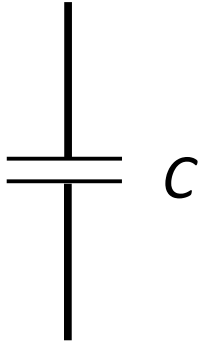

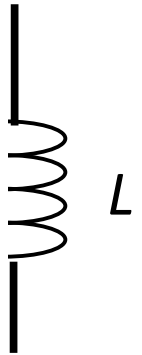
$$Z_C = \frac{V_C}{I_C} = \frac{1}{j\omega C}$$



$$Z_L = \frac{V_L}{I_L} = \frac{\omega L}{-j} = j\omega L$$



90° phase-shift in polar form: $e^{j\frac{\pi}{2}} = \cos\left(\frac{\pi}{2}\right) + j \sin\left(\frac{\pi}{2}\right) = j$

Impedance of a Resistor:

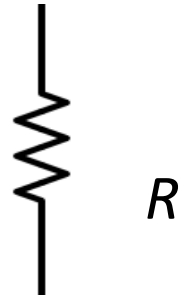


$$Z_R = \frac{V_R}{I_R} = R$$

Impedance arithmetic: same as a resistor

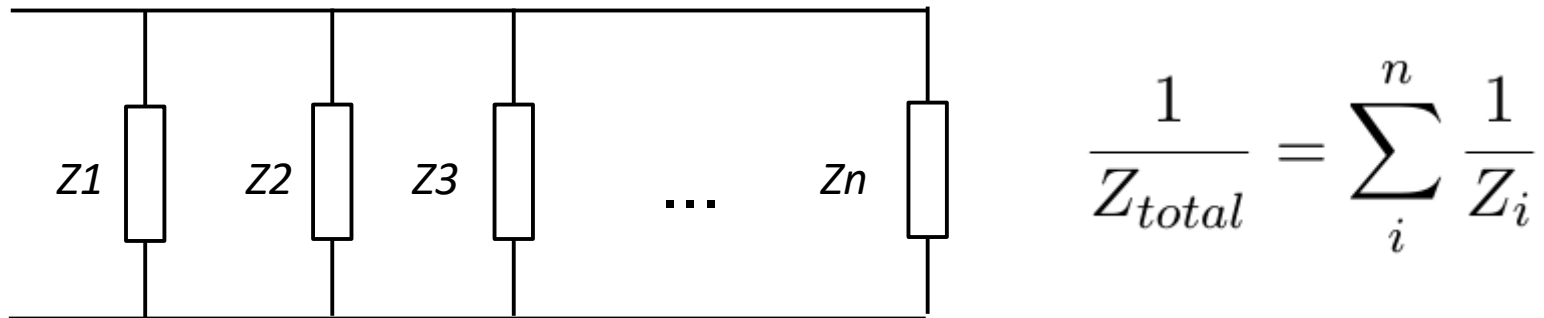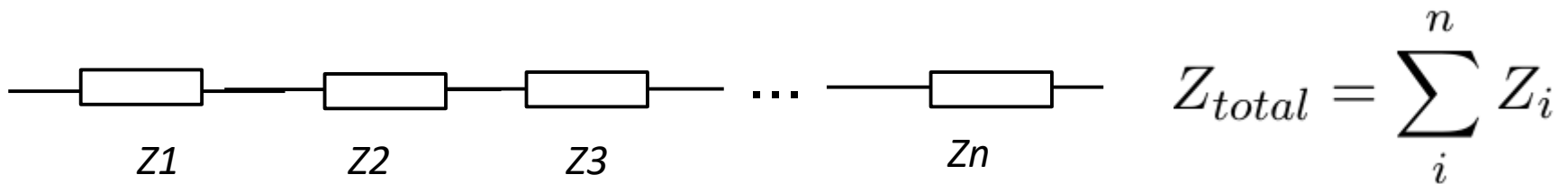

EXAMPLE 1

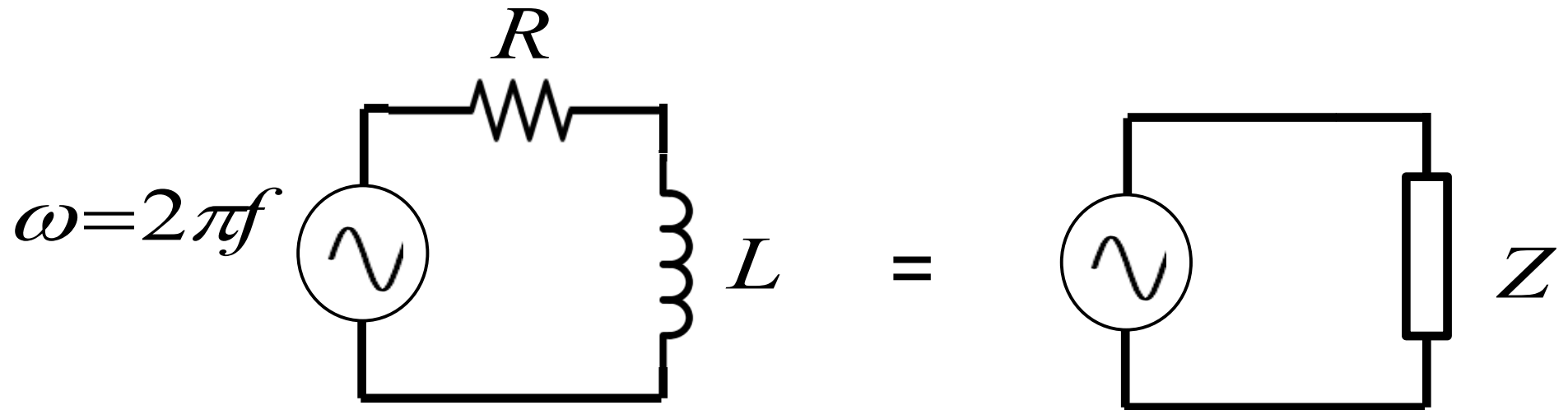


$$Z = Z_R + Z_L = R + j\omega L$$

Resistance

Reactance


EXAMPLE 2

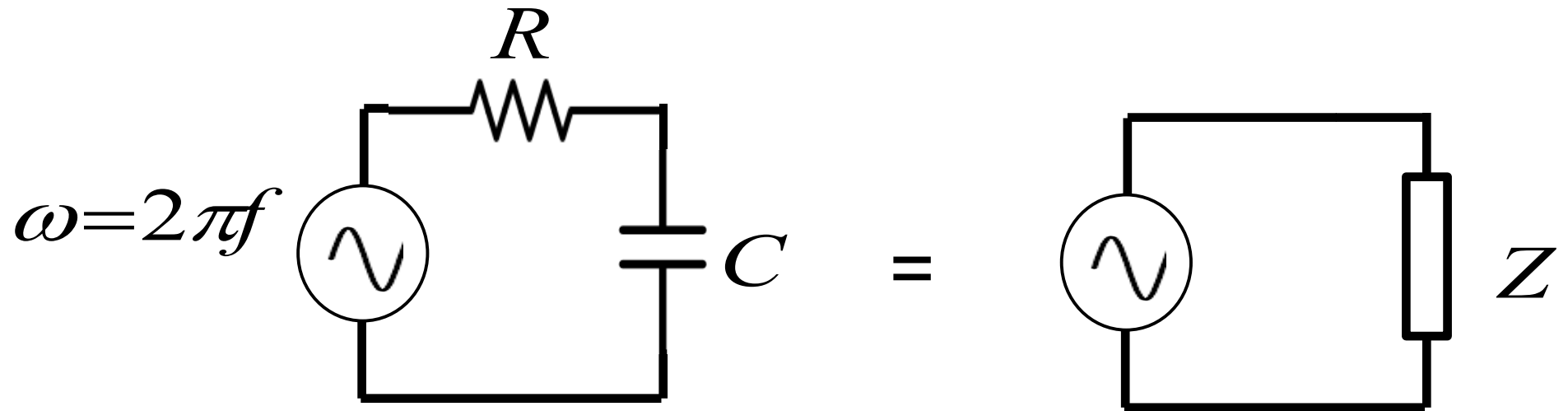

$$Z = Z_R + Z_L = R - \frac{j}{\omega C}$$

Resistance **Reactance**

EXAMPLE 3: Voltage Divider

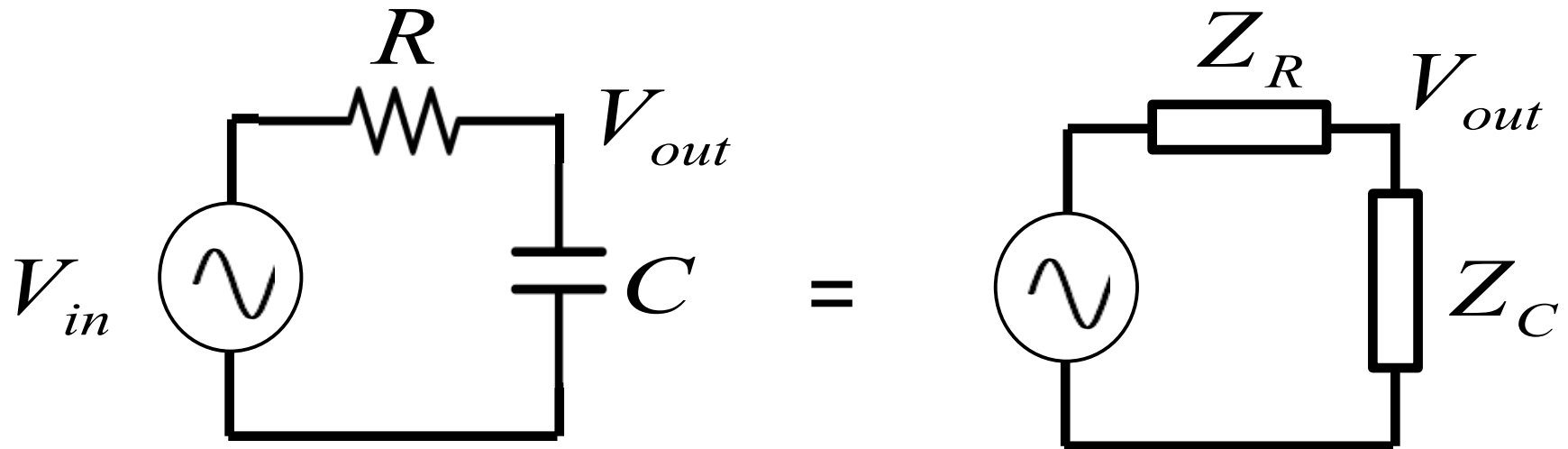


$$\frac{V_{out}}{V_{in}} = \frac{Z_C}{Z_R + Z_C} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

$$V_{in}(t) = V_0^{in} \sin(\omega t + \phi_0)$$

$$V_{out}(t) = V_0^{out} \sin(\omega t + \phi_1)$$


EXAMPLE 4: Voltage Divider

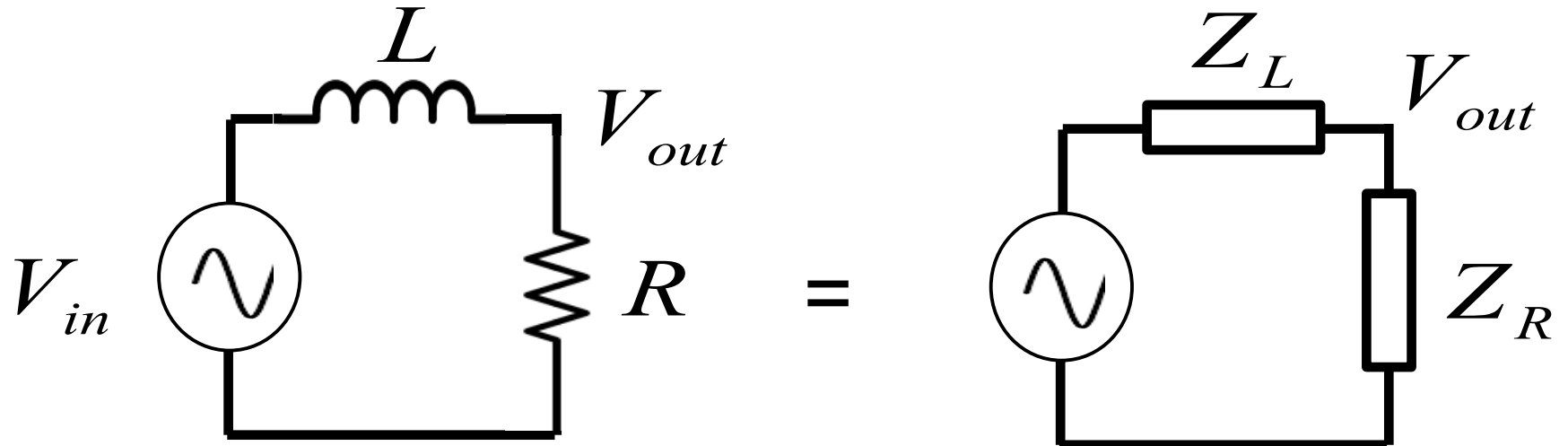

$$\frac{V_{out}}{V_{in}} = \frac{Z_R}{Z_R + Z_L} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R}$$

$$V_{in}(t) = V_0^{in} \sin(\omega t + \phi_0)$$

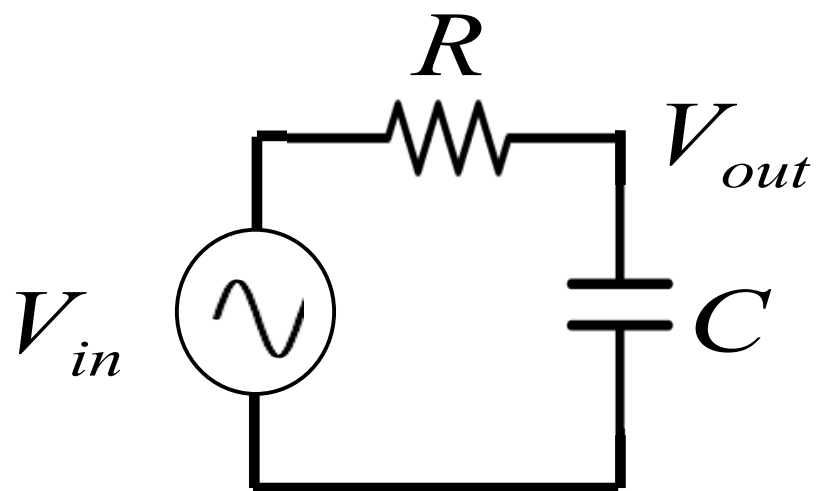
$$V_{out}(t) = V_0^{out} \sin(\omega t + \phi_1)$$



$$R = 217.8 \, \Omega$$

$$C = 145.6 \, \text{nF}$$

AMPLITUDE

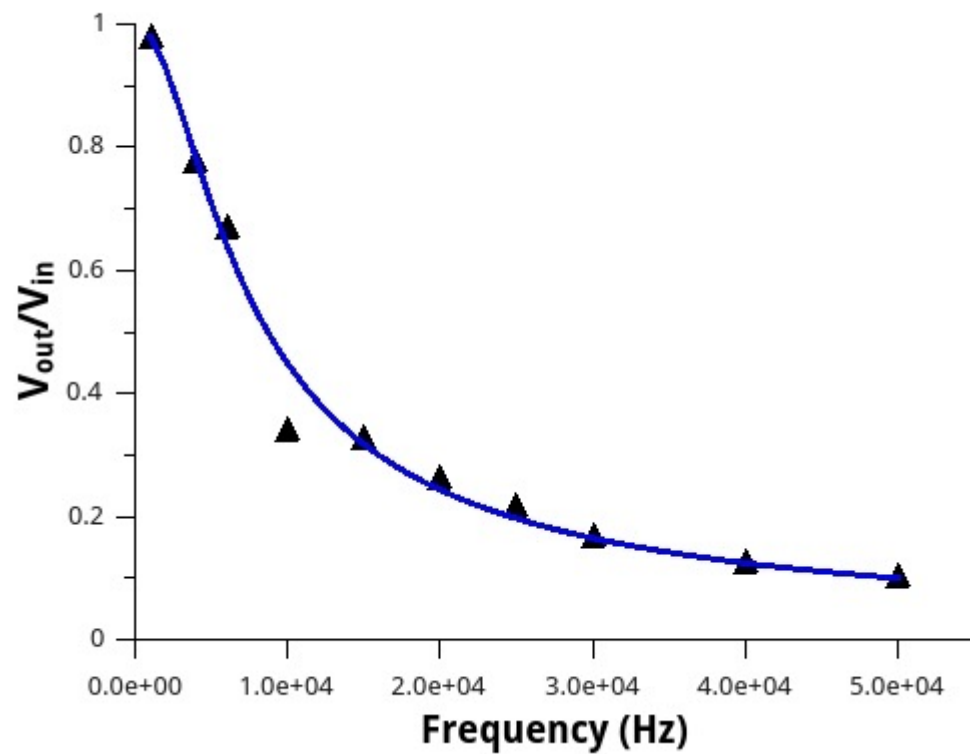

PHASE

