
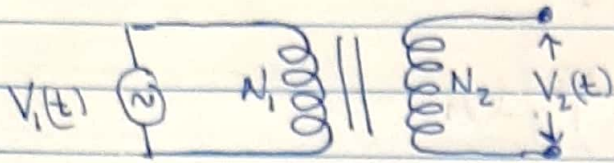


# Flashcards for Exam 3 Part 5

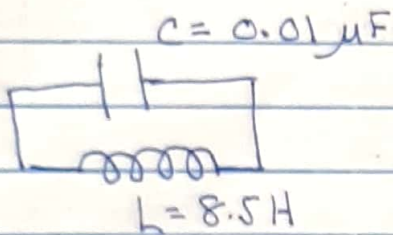

If  $N_1 = 10$  and  $N_2 = 5000$   
 and  $V_1(t) = 170 \text{ Volts } \cos(\omega t)$   
 and  $V_2(t) = \mathcal{E}_2 \cos(\omega t)$ ,  
 what is  $\mathcal{E}_2$ ?

$$\mathcal{E}_2 = \frac{5000}{10} \cdot 170 \text{ Volts} = 85 \text{ kV}$$




What is the oscillation  
 frequency of this LC  
 series circuit?

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(8.5)(1 \times 10^{-8})}}$$

$$= \frac{1}{\sqrt{9.5}} \times 10^4 = 343 \text{ rad/sec}$$
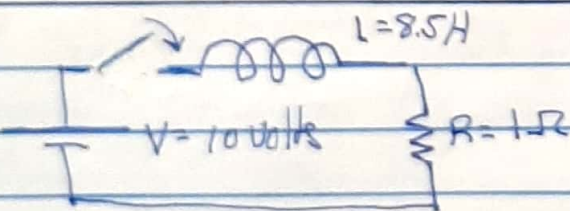
$$f = 343 \frac{\text{rad}}{\text{sec}} \times \frac{1 \text{ cycle}}{2\pi \text{ rad}} = 546 \text{ Hz}$$




Switch is closed. How much  
 energy will be stored in the  
 inductor when steady state  
 is reached?

$$I_{\text{steady state}} = \frac{V}{R} = \frac{10}{1} = 10 \text{ Amps}$$

$$U = \frac{1}{2} L I^2 = \frac{1}{2} (8.5) (10)^2$$

$$= 425 \text{ Joules.}$$




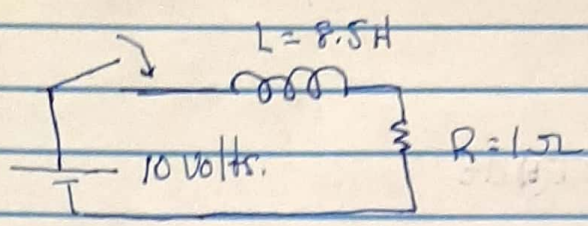

after switch is thrown, on what time scale is steady state achieved?

$$\tau = L/R = \frac{8.5}{1} = 8.5 \text{ sec} \approx \underline{10 \text{ sec.}}$$

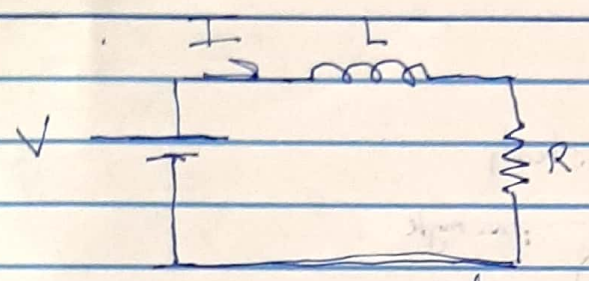so steady state is obtained on the order of 10's of seconds.



write down the modified kirchoff loop rule for this RL circuit. Assuming  $I(0) = 0$ , solve for  $I(t)$ .

$$V - L \frac{dI}{dt} - IR = 0$$

$$L \frac{dI}{dt} = V - IR$$

$$\int_0^I \frac{dI}{V - IR} = \int_0^t \frac{dt}{L}$$

$$-\frac{1}{R} \ln\left(\frac{V - IR}{V}\right) = \frac{t}{L}$$

$$1 - \frac{IR}{V} = e^{-Rt/L}$$

$$I = \frac{V}{R} (1 - e^{-Rt/L})$$

If  $V = 10 \text{ volts}$  and  $R = 1 \Omega$ , and  $L = 10 \text{ H}$ , how long before  $I = 5 \text{ Amps}$  in situation above?

$$5 \text{ Amps} = \frac{10 \text{ Volts}}{1 \Omega} (1 - e^{-t/10 \text{ sec}})$$

$$\text{set } 1 - e^{-t/10} = \frac{1}{2}$$

$$e^{-t/10} = 1 - 1/2 = 1/2$$

$$t/10 = -\ln(1/2)$$

$$t = 10 \text{ sec} \ln(2) = \underline{6.9 \text{ sec}}$$

How high is typical  $E$  for ac power transmission over long distances?

$$E \approx 345,000 \text{ Volts.}$$