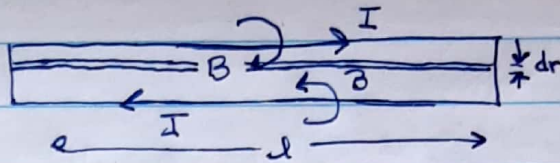


Solutions for Homework 13

5/1/2022


1) (a) (This calculation was worked out in class on Wed.)



$$\begin{aligned} \Phi &= \int_{\text{loop area}} \vec{B} \cdot d\vec{A} = \int B_{\text{from top wire}} dA + \int B_{\text{from bottom wire}} dA \\ &= 2 \int B_{\text{from top wire}} dA \\ &= 2 \int_{r=a}^w \frac{\mu_0 I}{2\pi r} \cdot l dr \\ &= \frac{\mu_0 I l}{\pi} \int_a^w \frac{dr}{r} = \frac{\mu_0 I l}{\pi} \ln(w/a) \\ L &= \Phi / I = \left[\frac{\mu_0 l}{\pi} \ln(w/a) \right] \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad L &= \frac{4\pi \times 10^{-7} \cdot 300 \times 10^3}{\pi} \ln(5/0.01) \\ &= \boxed{0.75 \text{ H}} \end{aligned}$$

2)

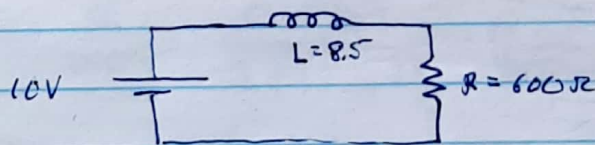

$$\begin{aligned} V - L \frac{dI}{dt} - IR &= 0 \\ L \frac{dI}{dt} &= V - IR \\ \int_0^I \frac{L dI}{V - IR} &= \int 1 \cdot dt = t \\ u = V - IR \quad du &= -R dI \end{aligned}$$

$$\begin{aligned} u &= V - IR \\ -\frac{L}{R} \int \frac{du}{u} &= t \\ u &= V \end{aligned}$$


$$\ln\left(\frac{V - IR}{V}\right) = -\frac{R}{L} t$$

$$1 - \frac{IR}{V} = e^{-\frac{R}{L} t}$$

$$I = \frac{V}{R} \left(1 - e^{-\frac{R}{L} t}\right)$$

$$\boxed{16.7 \text{ mA}} = I(\infty)$$
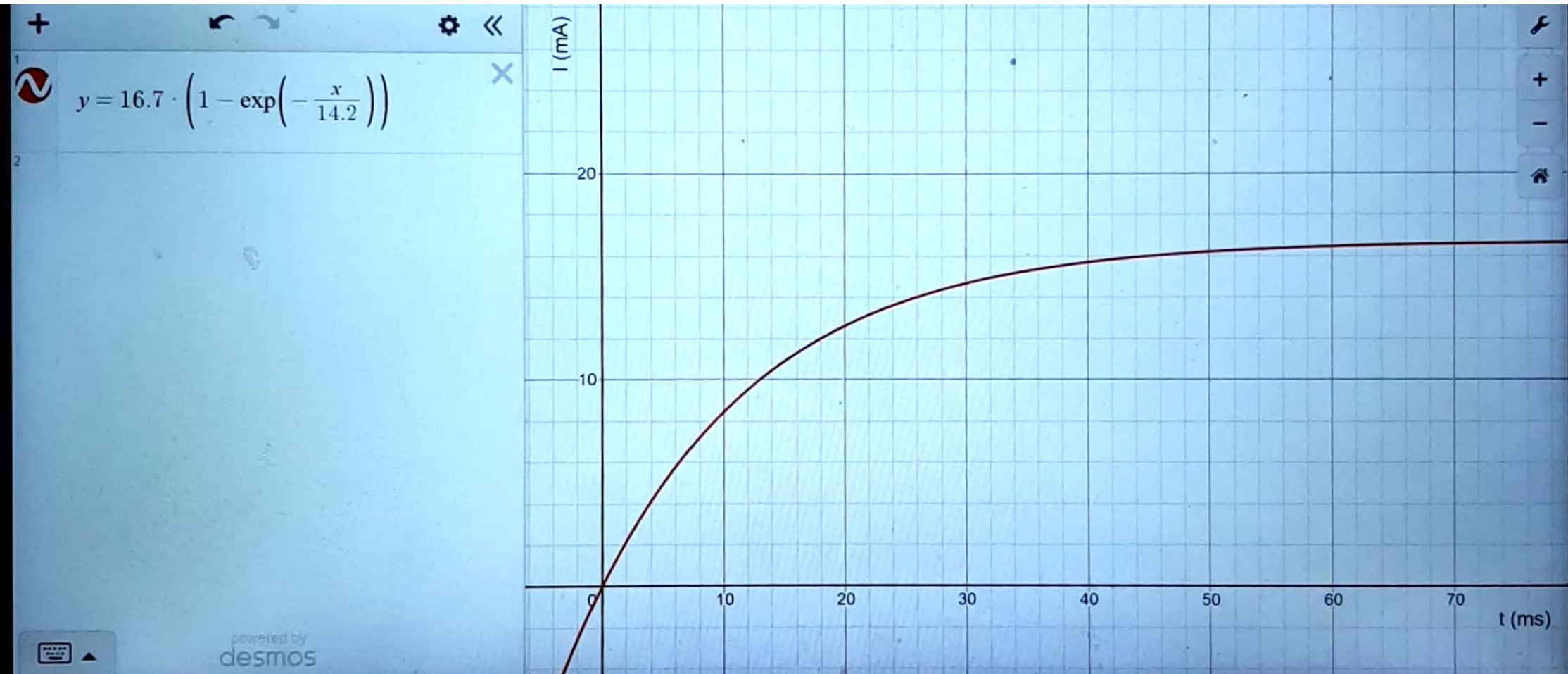
$$\begin{aligned} \frac{R}{L} &= \frac{70.6 \text{ s}^{-1}}{1} \\ \tau = \frac{1}{R/L} &= \boxed{14.2 \text{ ms}} \end{aligned}$$



3)

$$(a) \quad B_1 = \frac{\mu N_1 I_1}{l} \quad ; \quad B_2 = \frac{\mu N_2 I_2}{l}$$

$$(b) \quad \frac{V(t) - I_1 R_1}{N_1} = \frac{d}{dt} [N_1 (B_1 + B_2) A]$$

$$\frac{-I_2 R_2}{N_2} = \frac{d}{dt} [N_2 (B_1 + B_2) A]$$

$$\left(\frac{V(t) - I_1 R_1}{N_1} \right) - \left(\frac{-I_2 R_2}{N_2} \right) = 0$$

$$\boxed{V(t) - I_1 R_1 = - \frac{N_1}{N_2} (I_2 R_2)}$$

$$(c) \quad \frac{N_2}{N_1} (13,000) = 240$$

$$\boxed{\frac{N_2}{N_1} = \frac{1}{54}}$$

$$4) \quad \frac{Q^2}{2C} = \frac{(5 \times 10^{-2} \text{C})^2}{2(1 \times 10^{-3})} = \boxed{1.25 \text{J}} = \frac{1}{2} L I^2$$

$$I = \sqrt{\frac{2(1.25 \text{J})}{1.0 \text{H}}} = \boxed{1.6 \text{A}}$$

$$5) (a) \quad -\frac{Q}{C} = L \frac{dI}{dt} = L \frac{d}{dt} \left(\frac{dQ}{dt} \right) = L \frac{d^2 Q}{dt^2}$$

$$\boxed{\frac{d^2 Q}{dt^2} + \frac{1}{LC} Q = 0}$$

$$(b) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \cdot 10^{-5}}} = \boxed{10^4 \text{ rad/s}}$$

$$c) \quad \Phi = \Phi_0 \cos(\omega_0 t)$$

$$I = \frac{d\Phi}{dt} = -\underline{\Phi_0 \omega_0} \sin \omega_0 t$$

$$\frac{dI}{dt} = -\Phi_0 \omega_0^2 \cos(\omega_0 t)$$

$$\begin{aligned} L \frac{dI}{dt} &= -\Phi_0 L \omega_0^2 \cos(\omega_0 t) \\ &= -\Phi_0 L \cdot \frac{1}{LC} \cos(\omega_0 t) \\ &= -\left[\frac{\Phi_0}{C} \right] \cos(\omega_0 t) \end{aligned}$$

$$\left| L \frac{dI}{dt} \right|_{\max} = \frac{\Phi_0}{C} = \frac{1 \times 10^{-3} \text{ C}}{1 \times 10^{-5} \text{ F}} = \underline{\underline{100 \text{ Volts}}}$$

$$\left| \frac{\Phi}{C} \right|_{\max} = \frac{\Phi_0}{C} = \underline{\underline{100 \text{ Volts}}}$$

$$+\frac{\Phi}{C} = -L \frac{dI}{dt}$$

$$\underline{\Delta V_{\text{capacitor}}} + \underline{\Delta V_{\text{inductor}}} = 0$$

They are equal and opposite.

$$\begin{aligned} g) \quad \frac{1}{2} \frac{1}{\mu_0} \int_{\text{all space}} B^2 dV &= \frac{1}{2} \frac{1}{4\pi \times 10^{-7}} \cdot (7.7 \text{ T})^2 \cdot (27 \times 10^3) (3 \times 10^{-4}) \\ &= \underline{\underline{191 \text{ MJoules}}} \end{aligned}$$