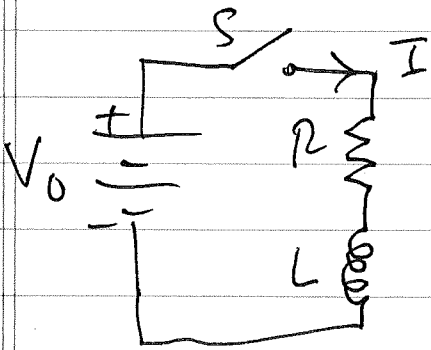


Circuits | RC, RL, LC, RLC...

Kirchoff's Law: $\sum_i V = 0$ } From closed circuit } $\oint \vec{E} \cdot d\vec{l} = 0$

E.g: R-L circuit



$$\sum_i V = 0 \rightarrow V_0 = V_R + V_L$$

\uparrow \uparrow
 IR $L \frac{dI}{dt}$

$$V_0 = IR + L \frac{dI}{dt}$$


Quasi-Static Approx!

For t near zero, I is small so: $\frac{dI}{dt} \approx \frac{V_0}{L}$

$$\Rightarrow I \approx \frac{V_0}{L} t \quad (I(t=0) = 0)$$

For large t , $\frac{dI}{dt} \rightarrow 0$, so standard solution

of battery + R: $I \rightarrow V_0/R$

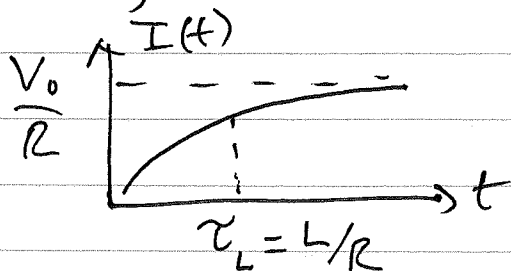

Full solution:

$$I(t) = \underbrace{A e^{-\frac{R}{L}t}}_{\text{homogeneous soln}} + \underbrace{V_0/R}_{\text{particular soln}}$$


Init. conditions: $I(0) = 0$ gives $A = -\frac{V_0}{R}$

$$\text{So, } \boxed{I(t) = \frac{V_0}{R} (1 - e^{-Rt/L})}$$

Inductors act like ∞ resistance when $\frac{dI}{dt}$ is large. But they act like short circuits for $I \approx \text{constant}$ or $\frac{dI}{dt} \approx 0$

RC circuits

Review these from P161!

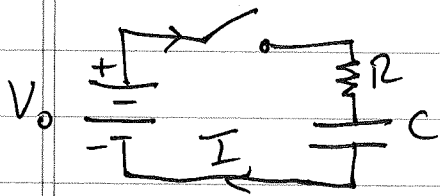


$$V_0 = V_R + V_C = IR + V_C$$

$$I = C \frac{dV_C}{dt}$$

$$\rightarrow V_0 = RC \frac{dV_C}{dt} + V_C$$

$$\text{or } \boxed{\frac{dV_C}{dt} = -\frac{1}{RC} V_C + \frac{V_0}{RC}}$$

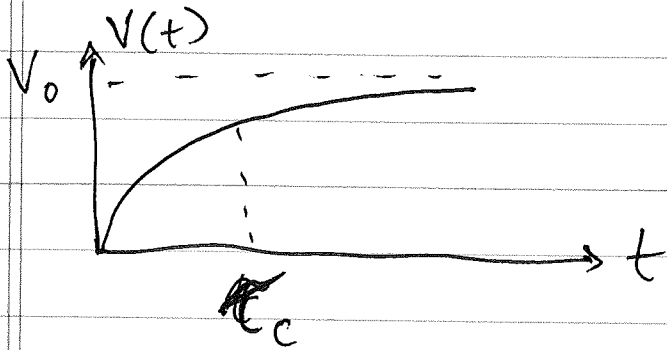Full soln: $V(t) = V_0 (1 - e^{-t/\tau_c})$



$\tau_c \equiv RC$ time-const.

When $V(t) \rightarrow V_0$ (stops changing), I stops:
 Caps. act as open circuits or ∞ resistors
 when dV/dt is small

AC Circuits

Review complex vars, exponential notation, etc

$$e^{-i\omega t} = \cos \omega t - i \sin \omega t$$

Impedance

Using complex notation: $V(t) = \text{Re}(\tilde{V} e^{-i\omega t})$
 Same with $I(t)$.

\rightarrow Impedance $Z = \tilde{V} / \tilde{I}$

Examples: $I \downarrow \uparrow R \leftarrow V$ $V = IR$, $Z_R = \frac{V}{I} = R$, real

Using complex notation we write

$$V(t) = \tilde{V} e^{-i\omega t}$$


$$I(t) = \tilde{I} e^{-i\omega t}$$

with \tilde{V} , \tilde{I} the complex (in general) phasors.


Impedance Z . This quantity is defined

as the ratio of the complex V/I across a circuit element

Examples

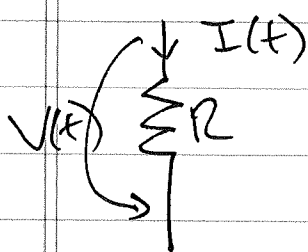

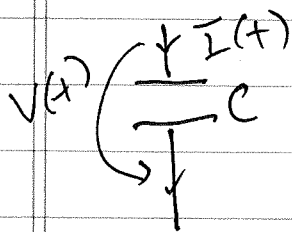
$$Z = \frac{V}{I} = \frac{IR}{I} = R, \text{ a real \# here}$$



$$Z_c = \frac{V}{I}; Q = CV, I = \frac{dQ}{dt} = C \frac{dV}{dt}$$


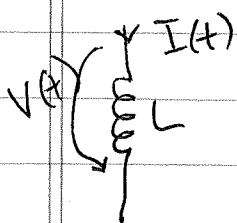
$$\rightarrow I = C(-i\omega)V, \text{ so } Z_c = \frac{1}{-i\omega C}$$



$$-E = V = L \frac{dI}{dt} = L(-i\omega)I$$

$$\rightarrow Z_L = \frac{V}{I} = -i\omega L$$

Impedance of circuits:

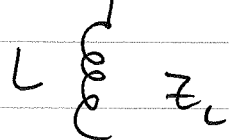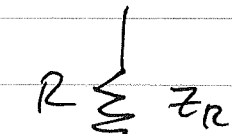


In series they effective

Z of circuit is $\sum Z$'s

$$\rightarrow Z = Z_R + Z_L + Z_C$$

$$Z = R + \frac{1}{-i\omega C} - i\omega L$$

For following circuit:

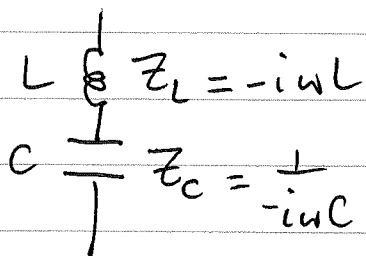





$$\Rightarrow Z_{\text{total}} = -i\omega L + \frac{1}{-i\omega C} = \frac{1 - \omega^2 LC}{-i\omega C}$$

Here, as we'll see in a bit, when

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}, \quad Z_{\text{total}} = 0$$

\Rightarrow Out of phase impedances cancel!

Summary : AC circuit

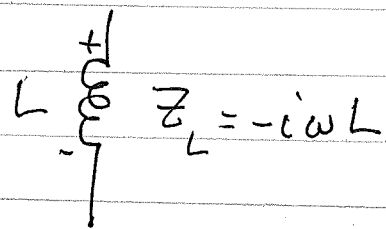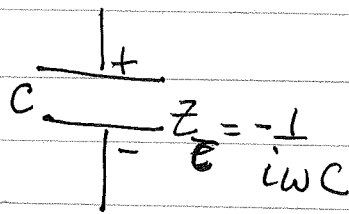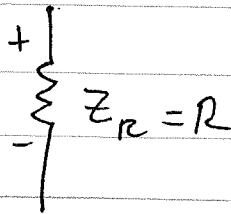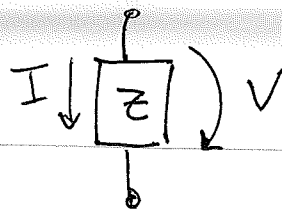


DC ? limit $\omega \rightarrow 0$:

$Z_R = R$; $Z_C \rightarrow \infty$ an open circuit ! ; $Z_L \rightarrow 0$ a short circuit !

Note that these components are called passive :

they respond to external conditions, e.g. changes in V or I

Back to LC circuit :

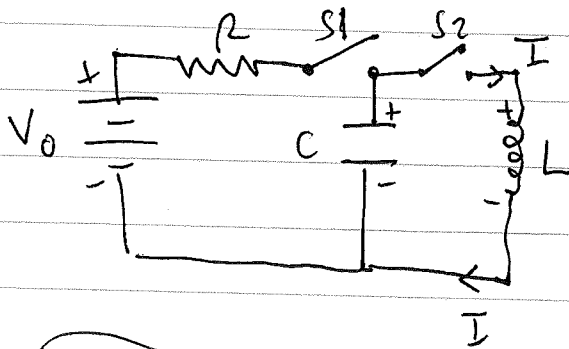

- close S_1 till C is charged
- open (close) S_1 (S_2)

$$Q = C V_C ; I_C = -dQ/dt$$

$$I_C = C \frac{dV_C}{dt} \quad \text{why?}$$

induced

$$V_L = V_C ; I_L = +I_C = -C \frac{dV_C}{dt} = -C \frac{dV_L}{dt}$$

also

$$V_L = L \frac{dI_L}{dt} = -LC \frac{d^2 V_L}{dt^2}$$

or SHO: $\frac{d^2 V_L}{dt^2} + \frac{1}{LC} V_L = 0$

Solution: (P160) $\omega_0^2 \equiv \frac{1}{LC}$ resonant freq.

$V_L(t) = a \cos \omega_0 t + b \sin \omega_0 t$

B.c.'s $I_L(0) = 0, V_L(0) = V_0$

$I_L(t) = -C \frac{dV_L}{dt}$

$\rightarrow a = V_0, b = 0$


$= \frac{a}{\sqrt{LC}} \sin \omega_0 t$

$-\frac{b}{\sqrt{LC}} \cos \omega_0 t$

$(V_c) V_L(t) = V_0 \cos \omega_0 t$

$I_L(t) = I_0 \sin \omega_0 t$ 90° out of phase

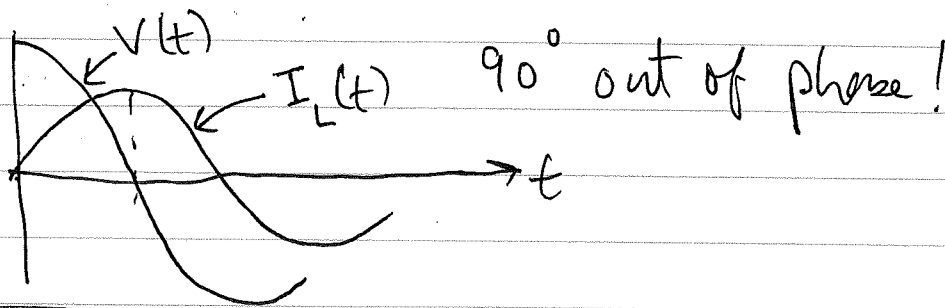Ratio of $\frac{V_0}{I_0} \equiv Z = \sqrt{L/C}$ characteristic impedance



Energy


In Cap:

$U_c = \frac{1}{2} C V_c^2 = \frac{1}{2} C V_0^2 \cos^2 \omega_0 t$
 $\underbrace{\hspace{10em}}_{LI_0^2} !$

In Inductor

$U_L = \frac{1}{2} L I_L^2 = \frac{1}{2} L I_0^2 \sin^2 \omega_0 t$

RLC circuit

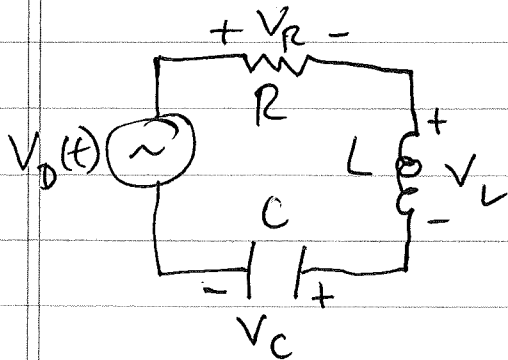

$$V_D(t) = V_R + V_L + V_C$$

$$I_R = I_L = I_C = I(t)$$

$$I(t) = \underbrace{I_{\text{Homog.}}}_{\text{transient}} + \underbrace{I_{\text{particular}}}_{\text{Steady-state}}$$

w/ $V_D = 0$
after C is charged

Transient solution: $V_D = 0$

$$V_R + V_L + V_C = 0 = IR + L \frac{dI}{dt} + \frac{Q}{C}$$

$$R \frac{dI}{dt} + L \frac{d^2 I}{dt^2} + \frac{I}{C} = 0$$

Damped S.H.O. $\left\{ \begin{array}{l} \ddot{I} + \Gamma \dot{I} + \omega_0^2 I = 0 \end{array} \right.$ Damping

where $\omega_0 \equiv \frac{1}{\sqrt{LC}}$ and $\Gamma = \frac{R}{L}$

Ansatz: $I = \text{Re} \left[\tilde{I} e^{\frac{st}{i\omega_0}} \right]$ where s is complex in general

Subbing above gives:

$$\underbrace{(s^2 + s\Gamma + \omega_0^2)}_{=0} \tilde{I} = 0 \Rightarrow \boxed{s_{\pm} = \frac{-\Gamma}{2} \pm \frac{\sqrt{\Gamma^2 - 4\omega_0^2}}{2}}$$

Two regimes: underdamped and overdamped


① Underdamped: $\omega_0 > \Gamma/2$

$$\Rightarrow S_{\pm} = \pm i\omega'_0 - \Gamma/2$$

$$\omega'_0 = \sqrt{\omega_0^2 - \Gamma^2/4}$$

Then, $I(t) = \text{Re} \left(\underbrace{\tilde{I}}_{\text{damping}} e^{-\Gamma/2 t} \underbrace{e^{\pm i\omega'_0 t}}_{\text{oscillations}} \right)$
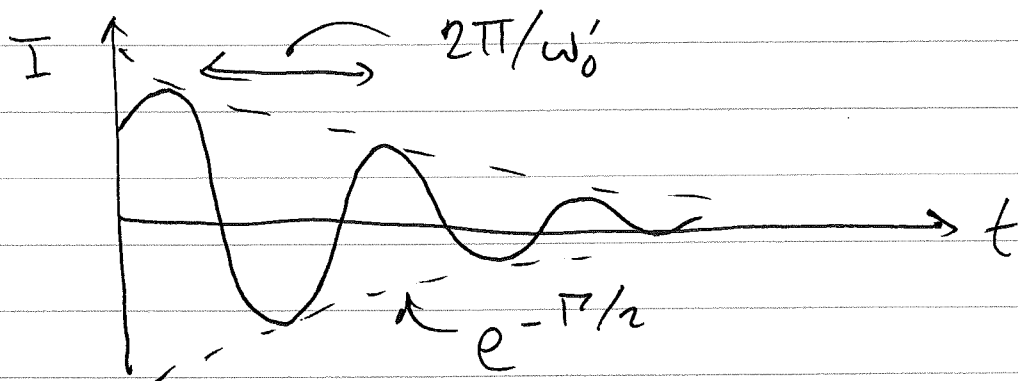
$$I(t) = A e^{-\Gamma/2 t} \cos(\omega'_0 t - \phi)$$



Next, consider steady-state solution for when $V_D(t) = \text{Re}[V_0 e^{-i\omega t}]$

$$\rightarrow I(t) = \text{Re}[\tilde{I} e^{-i\omega t}]$$

$$Z_{\text{total}} = Z_R + Z_C + Z_L = R + i \left(\frac{1}{\omega C} - \omega L \right)$$

$$\Rightarrow I(t) = \operatorname{Re} \left[\frac{V_0 e^{-i\omega t}}{Z_{\text{total}}} \right]$$

$$\text{Now, } Z_{\text{total}} = \frac{V_0}{I} = \frac{V_0}{\tilde{I}}$$

$$\text{or } I = \frac{V}{Z_{\text{total}}}, \text{ taking Real part:}$$

$$I = \operatorname{Re} \left[\frac{V_0 e^{-i\omega t}}{Z_{\text{total}}} \right]$$

$$I(t) = \operatorname{Re} \left[\frac{V_0 e^{-i\omega t}}{R + i \left(\frac{1}{\omega C} - \omega L \right)} \right] = \frac{V_0}{|Z_{\text{total}}|} \cos(\omega t - \phi)$$

$$\text{where } |Z_{\text{total}}| = \sqrt{R^2 + \frac{1}{\omega^2 C^2} \left(1 - \omega^2 / \omega_0^2 \right)^2}$$

$$\phi = \tan^{-1} \left(\frac{\frac{1}{\omega RC} - \frac{\omega L}{R}}{\quad} \right)$$

ANOTHER way to express this is in terms

of both $\sin(\omega t)$ and $\cos(\omega t)$! After all,
 $\cos(\omega t - \phi) \rightarrow$ broken into \sin & \cos terms.

$$I(t) = \operatorname{Re} \left[\frac{V_0 e^{-i\omega t}}{Z_{\text{tot}}} \right]$$

$$= \operatorname{Re} \left[\frac{V_0 z^* e^{-i\omega t}}{\underbrace{z z^*}_{\substack{\text{real} \\ = |z|^2}}} \right] = \frac{V_0}{|z|^2} \operatorname{Re} \left[z^* e^{-i\omega t} \right]$$

$$= \frac{V_0}{R^2 + \frac{1}{\omega^2 C^2} (1 - \omega^2 L^2)} \operatorname{Re} \left[(R - i(\frac{1}{\omega C} - \omega L)) (\cos \omega t - i \sin \omega t) \right]$$

$$R \cos \omega t - \left(\frac{1}{\omega C} - \omega L \right) \sin \omega t$$

$$= \frac{V_0}{R^2 + \frac{\omega_0^2 - \omega^2}{\omega_0^2 \omega^2 C^2}} \left[R \cos \omega t - \left(\frac{1}{\omega C} - \omega L \right) \sin \omega t \right]$$

Define the response function:

$$F(\omega) \equiv \frac{V_c}{V_0} \leftarrow \text{voltage across cap.}$$

$$V_c = I Z_c = \frac{V_0 \cdot Z_c}{Z_{\text{tot}}}$$

$$\rightarrow F(\omega) = \frac{i}{\omega C} \frac{1}{R + i\left(\frac{1}{\omega C} - \omega L\right)} = \frac{1}{-i\omega RC - \omega^2 LC + 1}$$

$$F(\omega) = \frac{\omega_0^2}{\omega_0^2 - \omega^2 - i\omega\Gamma}$$

Resonance when $F(\omega)$ is max., @ $\omega = \omega_0$

Here $F(\omega) \rightarrow \infty$ if no damping: $\Gamma \rightarrow 0$

If low damping $\Gamma \ll \omega_0$, $F(\omega)$ will be peaked at $\omega \approx \omega_0$. Let's see this:



$$\Delta \equiv \omega - \omega_0, \quad \Gamma, \Delta \ll \omega, \omega_0$$

$$\begin{aligned} \text{Write } \omega_0^2 - \omega^2 &= (\omega_0 - \omega)(\omega_0 + \omega) \\ &= -\Delta(\Delta + 2\omega_0) \\ &\approx -2\omega_0\Delta \end{aligned}$$

$$\text{So, } \boxed{F(\Delta) \approx \frac{\omega_0/2}{-\Delta - i\Gamma/2}}$$

$$\text{Re}(F(\Delta)) = \frac{\omega_0}{2} \left(\frac{-\Delta}{\Delta^2 + \Gamma^2/4} \right)$$
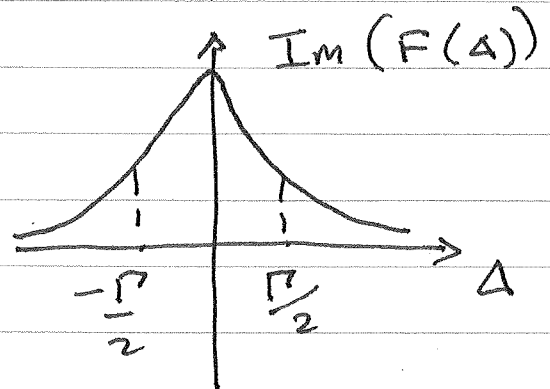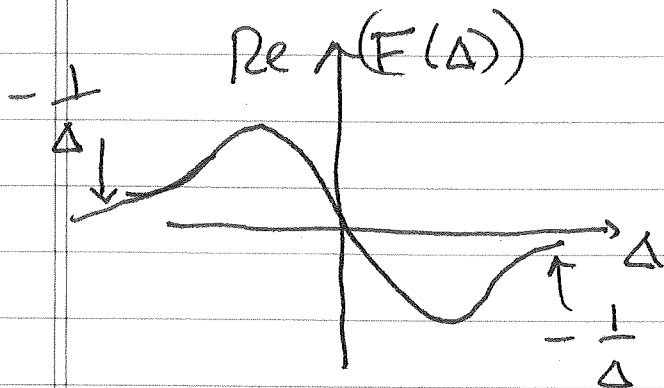
$$\text{Im}(F(\Delta)) = \frac{\omega_0}{2} \left(\frac{\Gamma/4}{\Delta^2 + \Gamma^2/4} \right)$$



$$\rightarrow V_{\text{cap}}(t) = \text{Re}[F(\omega) V_0 e^{-i\omega t}]$$

This fn is called
a "Lorentzian"
with $\Gamma \equiv$ full width
at half max.

$$V_{\text{cap}}(t) = \underbrace{\text{Re}(F(\omega)) V_0 \cos \omega t}_{\text{in phase with drive volt. } V_D(t)} + \underbrace{\text{Im}(F(\omega)) V_0 \sin \omega t}_{\text{out of phase ("in quadrature") with } V_D(t)}$$

$$= \frac{\omega_0/2}{\sqrt{\Delta^2 + \Gamma^2/4}} V_0 \cos(\omega t - \text{arg}(F(\omega)))$$

→ Amplitude of $V_{cap}(t)$ is max

When resonance, $\Delta = 0$

→ There's a phase shift:

$$\phi(\omega) = \arg(F(\omega)) = -\arg(Z_{tot})$$

$$\phi(\omega) = -\tan^{-1}\left(\frac{R}{2\Delta}\right)$$

