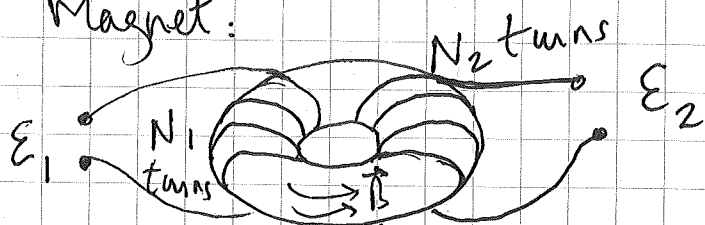


7.57) Transformer has same \vec{B} field going thru 2 separate coils that consist of independent circuits. E.g. 2 coils wrapped around a toroidal magnet:



iron torus with \vec{B} in it due to changing flux induced by one of the circuits (1 or 2)

The main point is that the same flux goes through a loop of either circuit:

$$\Phi = \text{flux} / \text{turn} = \text{same for 1 or 2}$$

$$\rightarrow \Phi_1 = N_1 \Phi \quad \text{and} \quad \Phi_2 = N_2 \Phi$$

$$\text{So, } \mathcal{E}_1 = -d\Phi_1 / dt = -N_1 d\Phi / dt$$

$$\mathcal{E}_2 = \quad \quad \quad = -N_2 d\Phi / dt$$

Ratio of these gives:

$$\boxed{\mathcal{E}_1 / \mathcal{E}_2 = N_1 / N_2}$$

This provides a mechanism for "stepping up" or "stepping down" the voltage of a circuit using a transformer.

7.58) Energy conservation in transformers.

→ stepping up or down must conserve energy

a) Show that $M^2 = L_1 L_2$ in tformer.

I_1 & I_2 are respective currents and

by definition: $\Phi_1 = I_1 L_1 + M I_2 = N_1 \Phi$

$\Phi_2 = I_2 L_2 + M I_1 = N_2 \Phi$

$$\Phi = \frac{I_1 L_1 + M I_2}{N_1} = \frac{I_2 L_2 + M I_1}{N_2}$$

this eqn holds for all I_1, I_2 .

Specifically, if $I_1 = 0$, then


$$\frac{M I_2}{N_1} = \frac{I_2 L_2}{N_2}$$

and if $I_2 = 0$: $\frac{L_1}{N_1} = \frac{M}{N_2}$ } divide these eqns: $\frac{M}{L_1} = \frac{L_2}{M}$

↓


$M^2 = L_1 L_2$

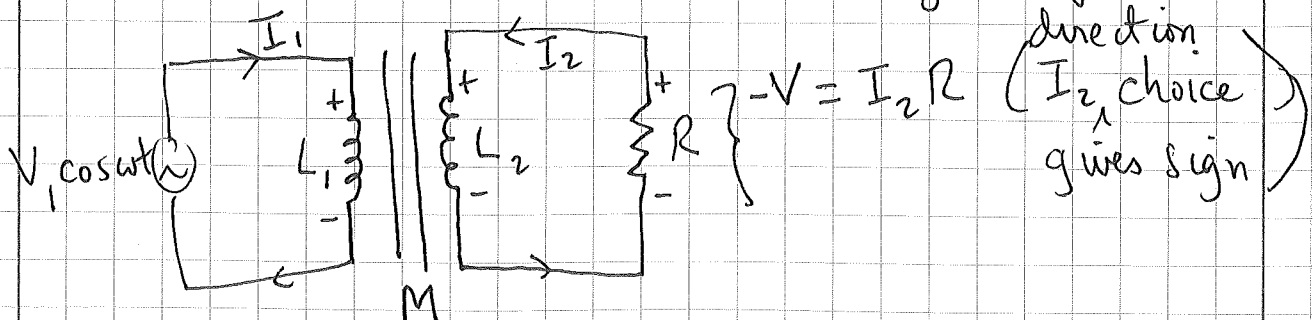b) Can show this using circuit diagram of 2 coils =



Kirchoff: $V_1 \cos \omega t = V_{L_1}$ and $V_{L_2} = -I_2 R$

Also from convention

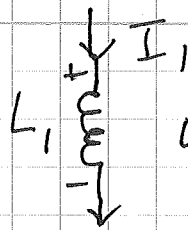

we have:

$$V_{L_1} = L \frac{dI_1}{dt}$$

Finally we add

Contribution from mutual

induction:

$$\textcircled{1} \quad V_{L_1} = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} = V_1 \cos \omega t$$

$$\textcircled{2} \quad V_{L_2} = L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = -I_2 R$$

Can also use part a) results and note that voltages in 2 cw circuits will be different signs (right hand rule) due to Lenz's Law.

c) Solve equations in part b) for I_1 & I_2

Multiply $\textcircled{1}$ above by L_2 and sub $\textcircled{2}$ in form

$$L_2 \frac{dI_2}{dt} = -I_2 R - M \frac{dI_1}{dt} \text{ into it.}$$

$$L_2 V_1 \cos \omega t = \underbrace{L_1 L_2}_{M^2} \frac{dI_1}{dt} + M \left(-I_2 R - M \frac{dI_1}{dt} \right)$$

from a)


$$L_2 V_1 \cos \omega t = M^2 \frac{dI_1}{dt} - M I_2 R - M^2 \frac{dI_1}{dt}$$
$$= -M I_2 R$$

$$\rightarrow \boxed{I_2 = -\frac{L_2 V_1 \cos \omega t}{M R}}$$

sub back into $\textcircled{1}$ above

sub back

Also from convention

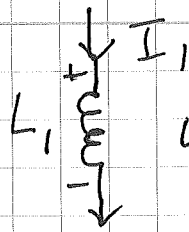

we have:

$$V_{L_1} = L \frac{dI_1}{dt}$$

Finally we add

Contribution from mutual

induction:

$$\textcircled{1} \quad V_{L_1} = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} = V_1 \cos \omega t$$

$$\textcircled{2} \quad V_{L_2} = L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt} = -I_2 R$$

Can also use part a) results and note that voltages in 2 cw circuits will be different signs (right hand rule) due to Lenz's Law.

c) Solve equations in part b) for I_1 & I_2

Multiply $\textcircled{1}$ above by L_2 and sub $\textcircled{2}$ in form

$$L_2 \frac{dI_2}{dt} = -I_2 R - M \frac{dI_1}{dt} \text{ into it.}$$

$$L_2 V_1 \cos \omega t = \underbrace{L_1 L_2}_{M^2} \frac{dI_1}{dt} + M \left(-I_2 R - M \frac{dI_1}{dt} \right)$$

(from a)

$$L_2 V_1 \cos \omega t = M^2 \frac{dI_1}{dt} - M I_2 R - M^2 \frac{dI_1}{dt}$$

$$= -M I_2 R$$

$$\rightarrow \left(I_2 = -\frac{L_2 V_1 \cos \omega t}{M R} \right) \text{ sub back into } \textcircled{1} \text{ above}$$

$$V_1 \cos \omega t = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$

$$\frac{dI_1}{dt} = \frac{V_1}{L_1} \left(\cos \omega t - \frac{L_2 \omega \sin \omega t}{R} \right) \left[\frac{L_2 V_1 \omega \sin \omega t}{M R} \right]$$

$$I_1 = \frac{V_1}{L_1} \left[\frac{\sin \omega t}{\omega} + \frac{L_2 \cos \omega t}{R} \right]$$

d) Ratio of voltages $V_{out}/V_{in} = ? = \frac{I_2 R}{V_1 \cos \omega t}$

$$= \left(\frac{-L_2 V_1 \cos \omega t}{M R} \right) \frac{R}{V_1 \cos \omega t}$$

$$= -\frac{L_2}{M} = -\frac{N_2}{N_1}$$

from work done in part a)

e) Calc. input/output powers & show (energy conservation) that their averages are equal:

$$P_{in} = V_{in} I_1 = (V_1 \cos \omega t) \frac{V_1}{L_1} \left[\frac{\sin \omega t}{\omega} + \frac{L_2 \cos \omega t}{R} \right]$$

$$P_{in} = \frac{V_1^2}{L_1} \left(\frac{\sin \omega t \cos \omega t}{\omega} + \frac{L_2 \cos^2 \omega t}{R} \right)$$

Time avg over a full cycle will give 0 for 1st term and $\frac{1}{2}$ for $\cos^2 \omega t$ term, so

$$\langle P_{in} \rangle = \frac{1}{2} \frac{V_1^2 L_2}{R L_1}$$

$$P_{out} = V_{out} I_2 = I_2^2 R = \left(\frac{L_2 V_1}{M} \right)^2 \frac{1}{R} \cos^2 \omega t$$

$$\langle P_{out} \rangle = \frac{1}{2} \frac{V_1^2}{R} \frac{L_2}{L_1}$$
$$= \langle P_{in} \rangle$$



$$(M^2 = L_1 L_2)$$

Physics 406

Problem Set #3 Solutions

Problem 1:

Parallel R-L-C circuit

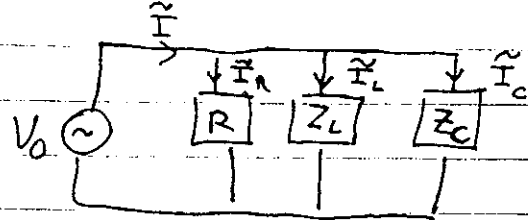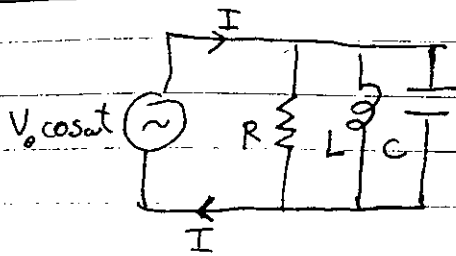

$$Z_R = R \quad Z_L = -i\omega L \quad Z_C = \frac{i}{\omega C}$$

Since the elements are in parallel

$$V_R = V_L = V_C = V_0$$

The total current divides between the elements

$$\tilde{I} = \tilde{I}_R + \tilde{I}_L + \tilde{I}_C = \tilde{V}/Z_R + \tilde{V}/Z_C + \tilde{V}/Z_L$$

$$\Rightarrow \tilde{I} = \left(\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} \right) V_0 = \frac{V_0}{Z_{\text{total}}}$$

Parallel addition of impedances

$$\frac{1}{Z_{\text{total}}} = \frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} = \frac{1}{R} - i\omega C + \frac{i}{\omega L}$$

(a) On resonance $\omega = \frac{1}{\sqrt{LC}}$

$$\Rightarrow \frac{1}{Z_{\text{total}}} = \frac{1}{R} - i\sqrt{\frac{C}{L}} + i\sqrt{\frac{C}{L}} = \frac{1}{R}$$

$$\Rightarrow \tilde{I} = \frac{V_0}{R} \Rightarrow \boxed{I(t) = \text{Re}(\tilde{I} e^{-i\omega t}) = \frac{V_0}{R} \cos \omega t}$$

On resonance the magnitude of $|Z_L| = |Z_C| = \sqrt{\frac{L}{C}}$

but they are 180° out of phase so they cancel

On resonance a parallel L-C is like an open circuit.

(b) In general

$$I(t) = \operatorname{Re}(\tilde{I} e^{-i\omega t}) = \operatorname{Re}\left(\frac{V_0}{Z_{\text{total}}} e^{-i\omega t}\right)$$
$$= \frac{V_0}{|Z_{\text{total}}|} \cos(\omega t + \operatorname{Arg}(Z_{\text{total}}))$$

$$\frac{1}{|Z_{\text{total}}|} = \left| \frac{1}{Z_{\text{total}}} \right| = \left| \frac{1}{R} - i\left(\omega C - \frac{1}{\omega L}\right) \right|$$
$$= \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2} = \frac{1}{\omega L} \sqrt{\frac{\omega^2 L^2}{R^2} + (\omega^2 LC - 1)^2}$$
$$= \frac{1}{R} \frac{\Gamma}{\omega} \sqrt{\frac{\omega^2}{\Gamma^2} + \left(\frac{\omega^2}{\omega_0^2} - 1\right)}, \quad \Gamma = \frac{R}{L}$$
$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\operatorname{Arg}(Z_{\text{total}}) = -\operatorname{Arg}\left(\frac{1}{Z}\right) = \tan^{-1}\left(\frac{\omega C - \frac{1}{\omega L}}{\frac{1}{R}}\right)$$
$$= \tan^{-1}\left(\frac{\Gamma}{\omega} \left(\frac{\omega^2}{\omega_0^2} - 1\right)\right)$$

$$\therefore I(t) = \frac{V_0}{R} \frac{\Gamma}{\omega} \sqrt{\frac{\omega^2}{\Gamma^2} + \left(\frac{\omega^2}{\omega_0^2} - 1\right)} \cos(\omega t + \operatorname{Arg}(Z_{\text{total}}))$$
$$\operatorname{Arg}(Z_T) = \tan^{-1}\left(\frac{\Gamma}{\omega} \left(\frac{\omega^2}{\omega_0^2} - 1\right)\right)$$

Note: On resonance, $I(t) = \frac{V_0}{R} \cos \omega t$
 $\operatorname{Arg}(Z_{\text{total}}) = 0$

Problem 2 Quality factor

(a) Math Lemma: Given $A(t) = A_0 \cos(\omega t - \phi_A)$
 $B(t) = B_0 \sin(\omega t - \phi_B)$

$$\text{Show } \langle A(t) B(t) \rangle = \frac{1}{T} \int_0^T dt A(t) B(t) = \frac{1}{2} \operatorname{Re}(\tilde{A}^* \tilde{B}) \\ = \frac{1}{2} \operatorname{Re}(\tilde{A} \tilde{B}^*)$$

$$\text{where } \tilde{A} = A_0 e^{i\phi_A} \quad A(t) = \operatorname{Re}(\tilde{A} e^{-i\omega t}) \\ \tilde{B} = B_0 e^{i\phi_B} \quad B(t) = \operatorname{Re}(\tilde{B} e^{-i\omega t})$$

Proof: There are lots of ways to do this, here's one of them

$$A(t) = \operatorname{Re}(\tilde{A} e^{-i\omega t}) = \tilde{A}' \cos \omega t + \tilde{A}'' \sin \omega t \quad \left(\begin{array}{l} \text{where} \\ \tilde{A} = \tilde{A}' + i\tilde{A}'' \\ \tilde{B} = \tilde{B}' + i\tilde{B}'' \end{array} \right) \\ B(t) = \operatorname{Re}(\tilde{B} e^{-i\omega t}) = \tilde{B}' \cos \omega t + \tilde{B}'' \sin \omega t$$

$$\therefore \langle A(t) B(t) \rangle = \tilde{A}' \tilde{B}' \langle \cos^2 \omega t \rangle + \tilde{A}'' \tilde{B}'' \langle \sin^2 \omega t \rangle \\ + (\tilde{A}' \tilde{B}'' + \tilde{A}'' \tilde{B}') \langle \cos \omega t \sin \omega t \rangle$$


$$\text{Now } \langle \cos^2 \omega t \rangle = \langle \sin^2 \omega t \rangle = \frac{1}{2} \quad \left. \begin{array}{l} \text{check} \\ \text{these} \end{array} \right\} \\ \langle \cos \omega t \sin \omega t \rangle = \frac{1}{2} \langle \sin 2\omega t \rangle = 0$$

$$\Rightarrow \langle A(t) B(t) \rangle = \frac{1}{2} (\tilde{A}' \tilde{B}' + \tilde{A}'' \tilde{B}'')$$

$$= \frac{1}{2} \operatorname{Re}(\tilde{A} \tilde{B}^*) = \frac{1}{2} \operatorname{Re}(\tilde{A}^* \tilde{B})$$

QED

(b) Power dissipated in an RLC circuit

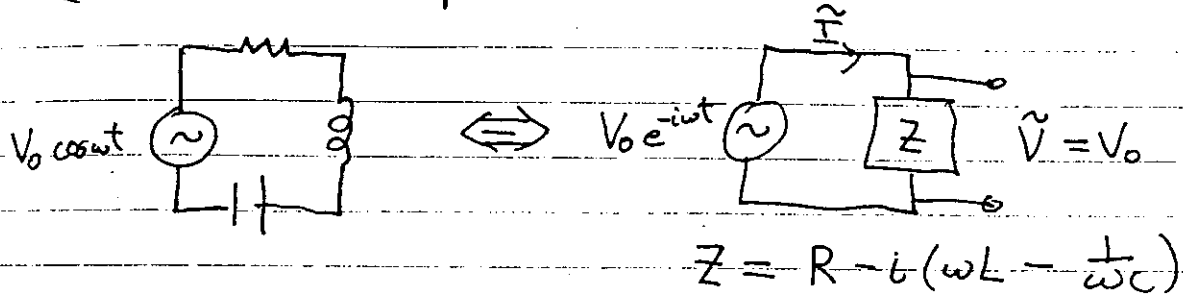

From part (a)

$$\langle P(t) \rangle = \langle V(t) I(t) \rangle = \frac{1}{2} \operatorname{Re}(\tilde{V} \tilde{I}^*)$$

Here \tilde{V} and \tilde{I} are the complex amplitudes of the voltage and current across the load

$$\tilde{V} = V_0 \quad \tilde{I} = \frac{\tilde{V}}{Z} = \frac{V_0}{Z}$$

$$\begin{aligned} \therefore \langle P \rangle &= \frac{1}{2} \operatorname{Re} \left(\frac{V_0^2}{Z} \right) = \frac{V_0^2}{2} \operatorname{Re} \left(\frac{1}{R - i(\omega L - \frac{1}{\omega C})} \right) \\ &= \frac{V_0^2}{2} \operatorname{Re} \left(\frac{R + i(\omega L - \frac{1}{\omega C})}{R^2 + (\omega L - \frac{1}{\omega C})^2} \right) \end{aligned}$$

Multiplying top and bottom by $R + i(\omega L - \frac{1}{\omega C})$

$$= \frac{V_0^2}{2} \frac{R}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \frac{V_0^2}{2R} \frac{\frac{R^2}{L^2} \omega^2}{\omega^2 \frac{R^2}{L^2} + (\omega^2 - \frac{1}{LC})^2}$$

(multiplying top and bottom by $\frac{\omega^2}{L^2}$)

$$= \frac{V_0^2}{2R} \frac{\Gamma^2 \omega^2}{\omega^2 \Gamma^2 + (\omega^2 - \omega_0^2)^2}$$

where $\Gamma \equiv \frac{R}{L} \quad \omega_0 = \frac{1}{LC}$


Now in the near resonance approximation

$$\omega^2 - \omega_0^2 = (\omega - \omega_0)(\omega + \omega_0) \approx 2\omega(\omega - \omega_0)$$

$$\Rightarrow \langle P \rangle = \frac{V_0^2}{2R} \frac{\Gamma^2 \omega^2}{\omega^2 \Gamma^2 + 4\omega^2(\omega - \omega_0)^2}$$

$$\langle P \rangle = \frac{V_0^2}{2R} \frac{\Gamma^2/4}{(\omega - \omega_0)^2 + \frac{\Gamma^2}{4}}$$

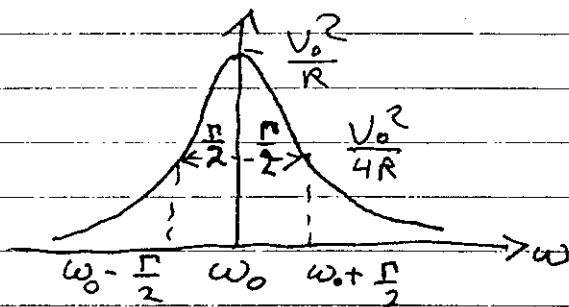Near the resonance, the $\langle \text{Power} \rangle$ dissipated looks like a Lorentzian



$$\text{FWHM} = \Gamma$$

(c) The average stored energy is the sum of energies in C +

$$\langle E \rangle = \langle E_C \rangle + \langle E_L \rangle = \frac{1}{2} \langle V_C^2 \rangle + \frac{1}{2} L \langle I_L^2 \rangle$$

But $\langle E_C \rangle = \langle E_L \rangle$ (capacitor + inductor store equal energies)

$$\Rightarrow \langle E \rangle = 2 \langle E_L \rangle = L \langle I_L^2 \rangle$$

$$= L \left(\frac{\text{Re} \langle \tilde{I} \tilde{I}^* \rangle}{2} \right) = \frac{L}{2} \text{Re} \left(\frac{\tilde{V}}{Z} \frac{\tilde{V}^*}{Z^*} \right)$$

$$= \frac{L}{2} \frac{V_0^2}{|Z|^2}$$

On resonance $Z = R \Rightarrow \langle E(\omega = \omega_0) \rangle = \frac{L V_0^2}{2 R^2}$

On resonance, the average power dissipated is


$$\langle P \rangle |_{\omega=\omega_0} = \frac{V_0^2}{2R}$$

$$\therefore Q \equiv \omega_0 \frac{\langle E \rangle}{\langle P \rangle} = \omega_0 \frac{\frac{L V_0^2}{2R^2}}{\frac{V_0^2}{2R}}$$


$$\Rightarrow \boxed{Q = \omega_0 \frac{L}{R} = \frac{\omega_0}{\Gamma}}$$

This is the general form of Q : ratio of oscillation frequency to the damping rate.

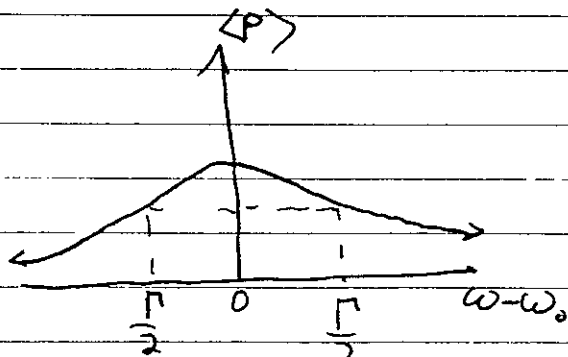It measures the number of periods oscillated before the stored energy decays to $1/e$ of its value. For a good oscillator Q is very large ($\sim 10^4$). The resonance is then very narrow (i.e. if we want to deliver power to the load we must be almost exactly on resonance);



Low Q
(R big)

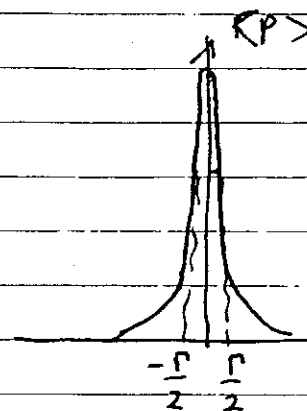

High Q
(R small)