

Lecture 38


PHYC 161 Fall 2016

- PLEASE FILL OUT YOUR COURSE EVALUATIONS ONLINE — available up to 12/9

Inductors as circuit elements


- In the circuit shown, the box enables us to control the current i in the circuit.
- The potential difference between the terminals of the inductor L is:

$$V_{ab} = V_a - V_b = L \frac{di}{dt}$$

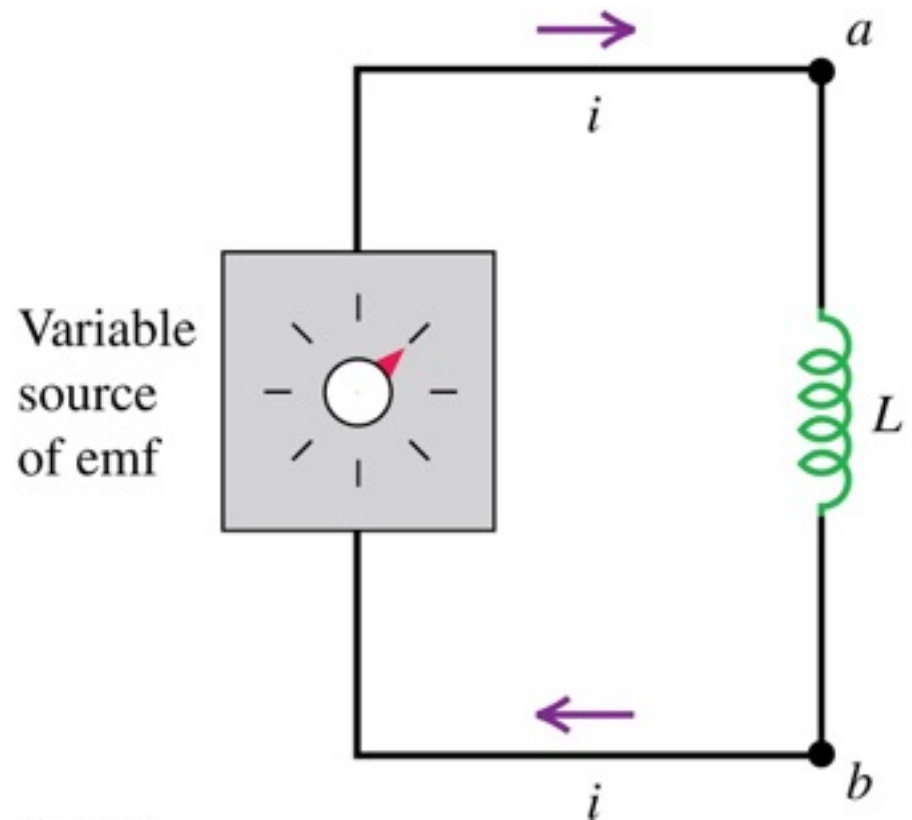

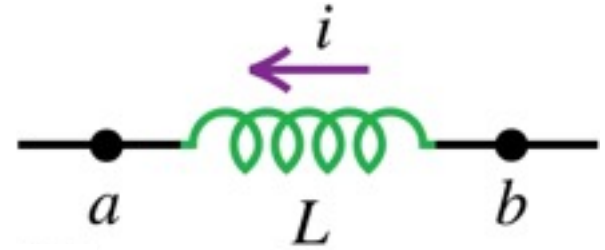Q30.2


A current i flows through an inductor L in the direction from point b toward point a . There is zero resistance in the wires of the inductor. If the current is *decreasing*,



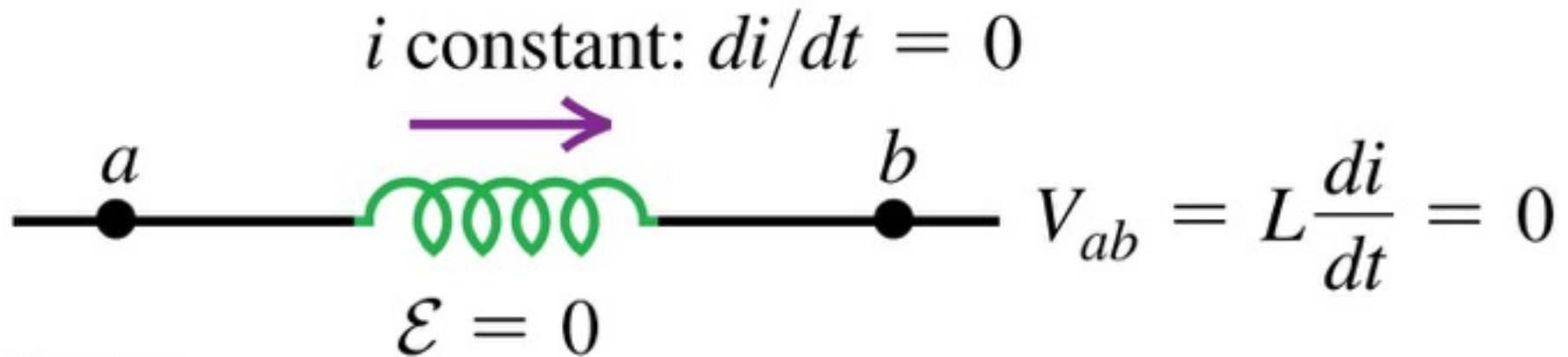- A. the potential is greater at point a than at point b .
- B. the potential is less at point a than at point b .
- C. the answer depends on the magnitude of di/dt compared to the magnitude of i .
- D. the answer depends on the value of the inductance L .
- E. both C and D are correct.


Potential across an inductor with constant current

- The potential difference across an inductor depends on the rate of change of the current.
- When you have an inductor with *constant* current i flowing from a to b , there is *no* potential difference.




Potential across an inductor with increasing current

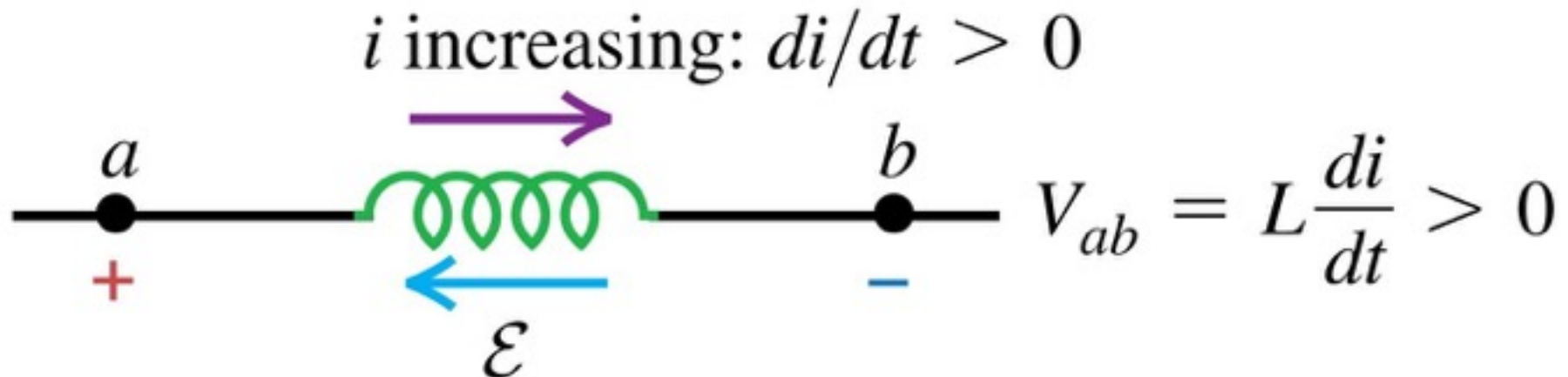- The potential difference across an inductor depends on the rate of change of the current.
- When you have an inductor with *increasing* current i flowing from a to b , the potential *drops* from a to b .



Potential across an inductor with decreasing current

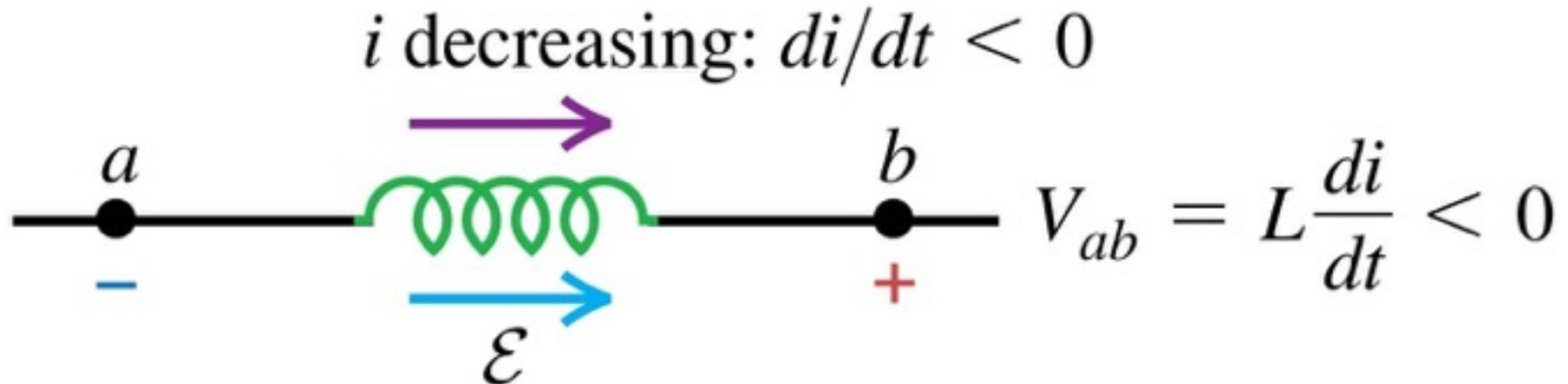
- The potential difference across an inductor depends on the rate of change of the current.
- When you have an inductor with *decreasing* current i flowing from a to b , the potential *increases* from a to b .




Magnetic field energy

- A resistor is a device in which energy is irrecoverably *dissipated*.
- By contrast, energy stored in a current-carrying inductor can be recovered when the current decreases to zero.

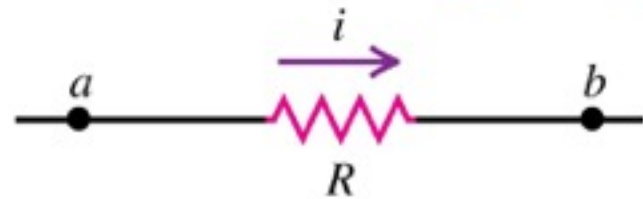Resistor with current i : energy is *dissipated*.



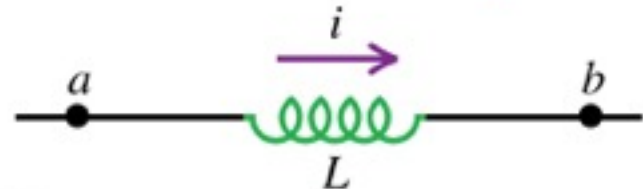Inductor with current i : energy is *stored*.



Energy stored in an inductor $\rightarrow U = L \int_0^I i \, di = \frac{1}{2} LI^2$

Inductance L and Final current I are indicated by dashed arrows pointing to the corresponding terms in the equation.

Integral from initial (zero) value of instantaneous current to final value

Magnetic energy density

- The energy in an inductor is actually stored in the magnetic field of the coil, just as the energy of a capacitor is stored in the electric field between its plates.
- In a vacuum, the energy per unit volume, or **magnetic energy density**, is:

$$\text{Magnetic energy density in vacuum} \dots \rightarrow u = \frac{B^2 \dots \text{Magnetic-field magnitude}}{2\mu_0 \dots \text{Magnetic constant}}$$

- When the magnetic field is located within a material with (constant) magnetic permeability $\mu = K_m \mu_0$, we replace μ_0 by μ in the above equation:


$$\text{Magnetic energy density in a material} \dots \rightarrow u = \frac{B^2 \dots \text{Magnetic-field magnitude}}{2\mu \dots \text{Permeability of material}}$$

The R - L circuit

- An R - L circuit contains a resistor and inductor and possibly an emf source.
- Shown is a typical R - L circuit.

Start with S_1 , S_2 both open
At $t=0$, close S_1

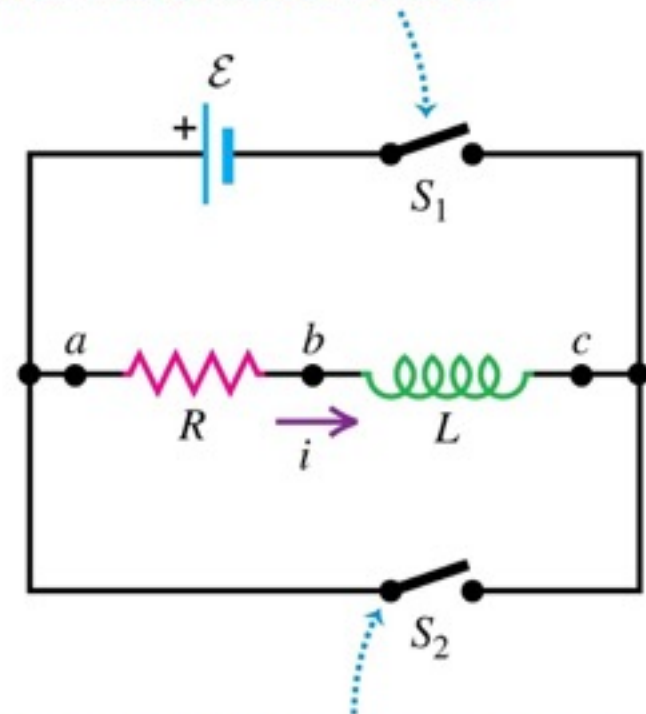Closing switch S_1 connects the R - L combination in series with a source of emf \mathcal{E} .





Closing switch S_2 while opening switch S_1 disconnects the combination from the source.

Current growth in an R - L circuit

- Suppose that at some initial time $t = 0$ we close switch S_1 .
- The current cannot change suddenly from zero to some final value.
- As the current increases, the rate of increase of current given becomes smaller and smaller.
- This means that the current approaches a final, steady-state value I .
- The **time constant** for the circuit is $\tau = L/R$.

Switch S_1 is closed at $t = 0$.

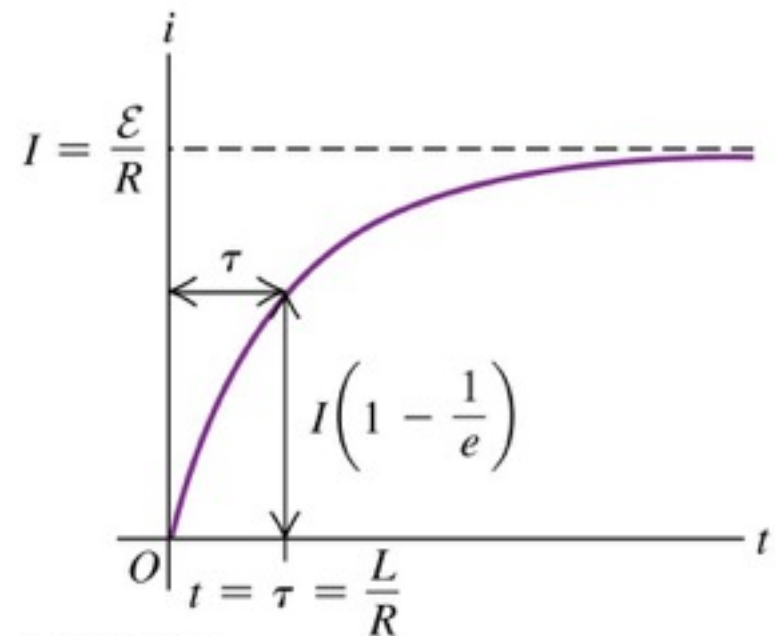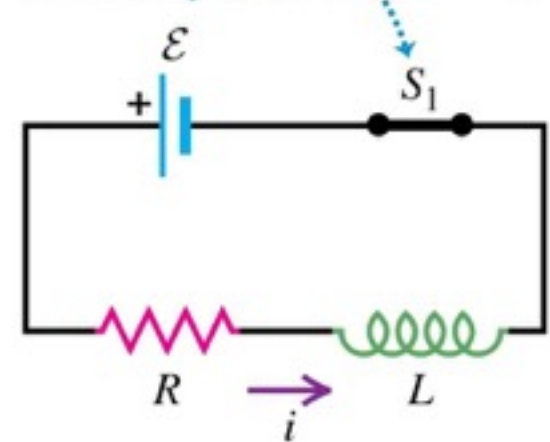


The R - L circuit

- An R - L circuit contains a resistor and inductor and possibly an emf source.
- Shown is a typical R - L circuit.

Start with S_1 closed for a long time, S_2 open
At $t=0$, close S_2 , open S_1

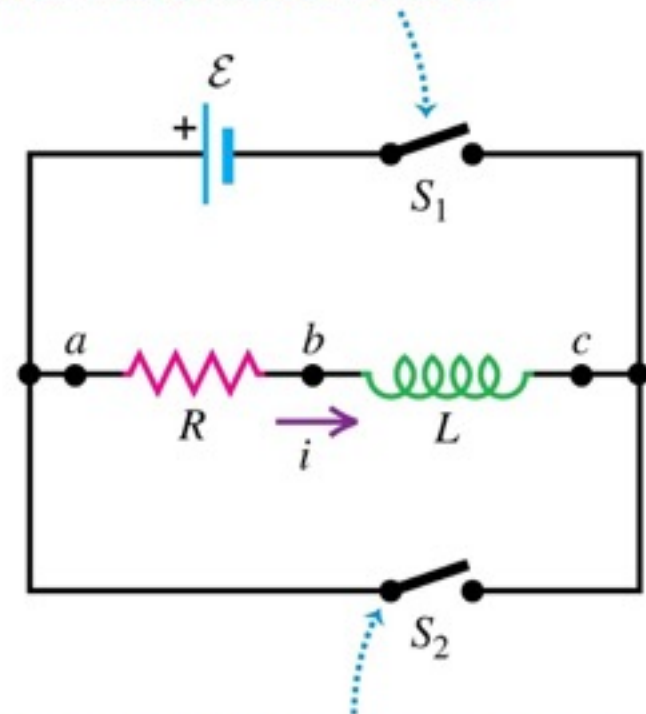
Closing switch S_1 connects the R - L combination in series with a source of emf \mathcal{E} .



Closing switch S_2 while opening switch S_1 disconnects the combination from the source.

Current decay in an R - L circuit

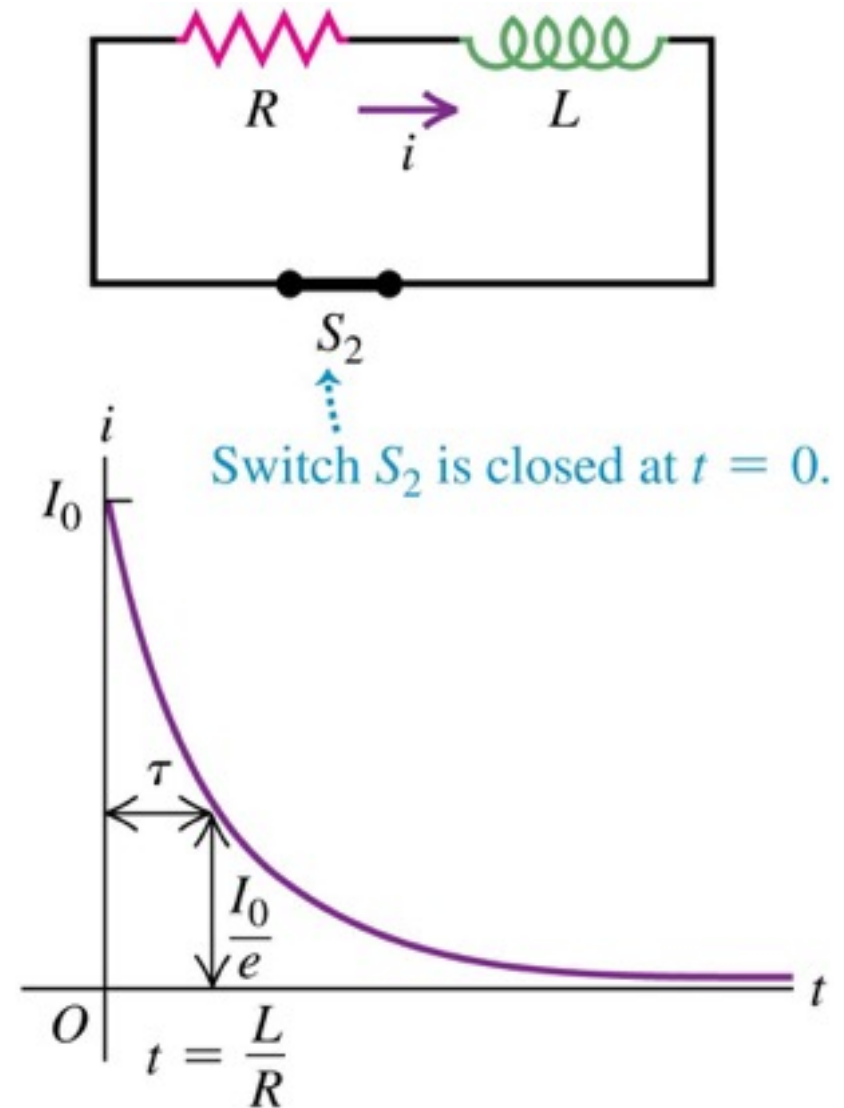- Suppose there is an initial current I_0 running through the resistor and inductor shown.
- At time $t = 0$ we close the switch S_2 , bypassing the battery (not shown).
- The energy stored in the magnetic field of the inductor provides the energy needed to maintain a decaying current.
- The **time constant** for the exponential decay of the current is $\tau = L/R$.




- We start with a charged capacitor in series with a switch and an inductor. $Q_{\text{init}} = CV_{\text{init}}$
- Let's apply Kirchhoff's loop rule:

$$\sum \Delta V = -\frac{q}{C} - L \frac{di}{dt} = 0 \Rightarrow$$

$$\frac{q}{C} + L \frac{di}{dt} = 0 \Rightarrow$$

$$L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0 \Rightarrow$$
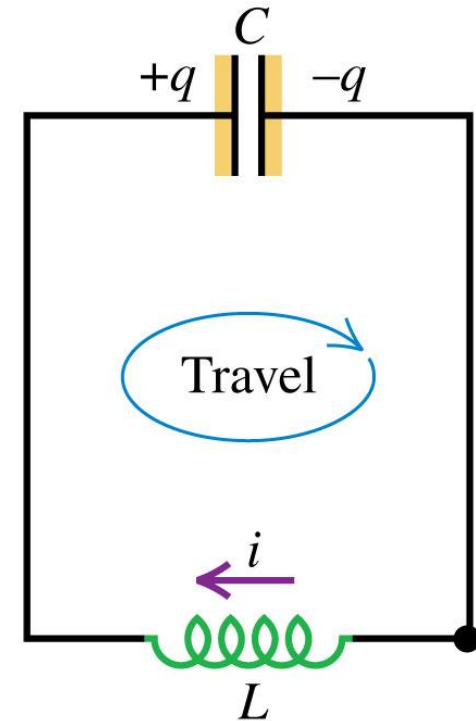
$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0$$



© 2012 Pearson Education, Inc.

Capacitor discharges
through inductor

LC Circuits

- Do you recognize this equation?

$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0$$

- What if I just changed q to x and renamed the constant?


$$\frac{d^2 x}{dt^2} + \omega^2 x = 0$$

- So the equation just describes oscillations with a frequency:


$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0 \Rightarrow$$

$$q = Q_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

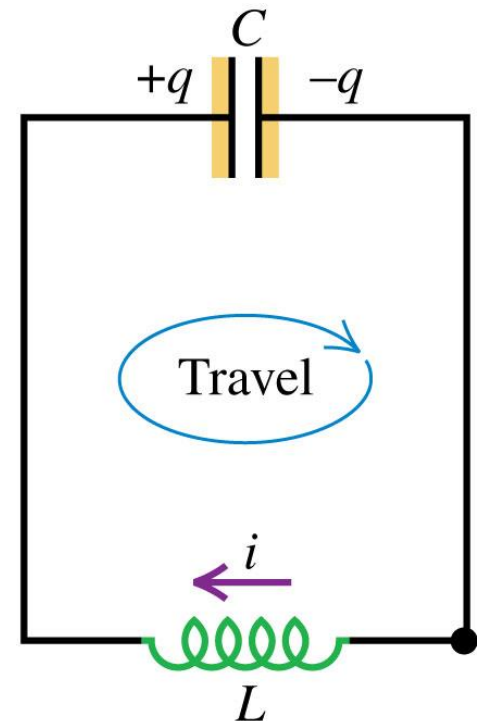


Capacitor fully charged;
zero current

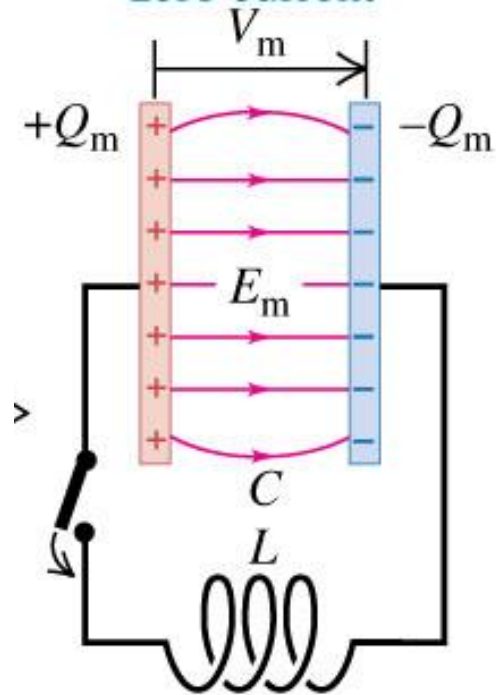

$$E = U_B + U_E$$

Circuit's energy all
stored in electric field

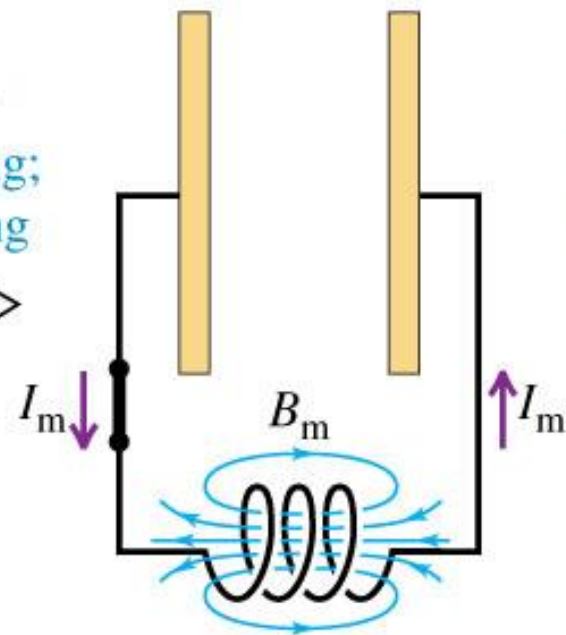
Capacitor fully
discharged;
current maximal





$$E = U_B + U_E$$

Circuit's energy all
stored in magnetic field

Capacitor
discharging;
 I increasing

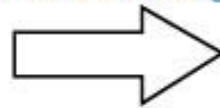

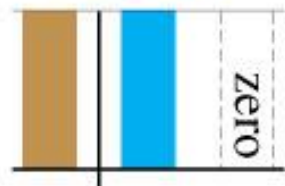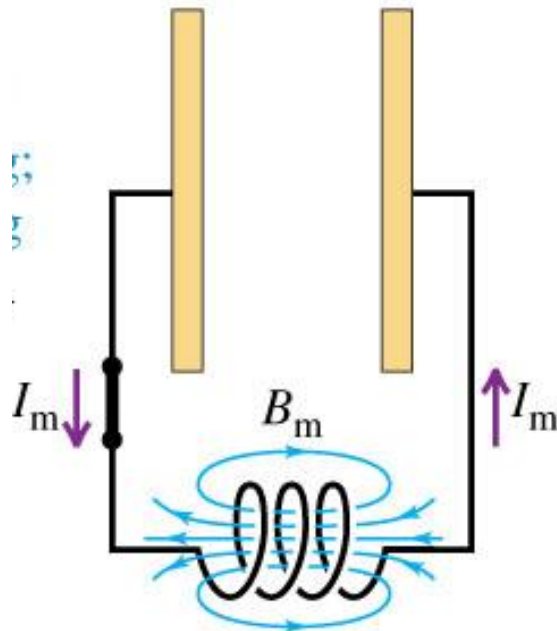
Capacitor fully discharged;
current maximal



$$E = U_B + U_E$$

Circuit's energy all stored in magnetic field


Capacitor fully charged;
zero current

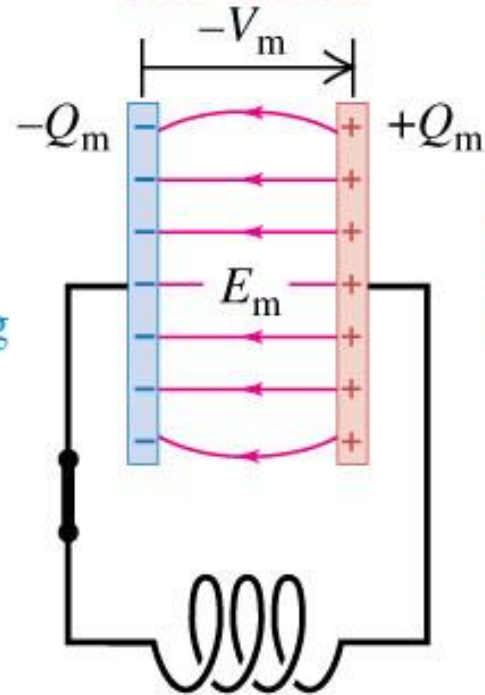

$$E = U_B + U_E$$


Circuit's energy all stored in electric field

Capacitor charging;
 I decreasing

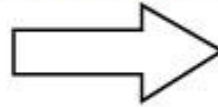

Energy/Current/Charge Oscillations
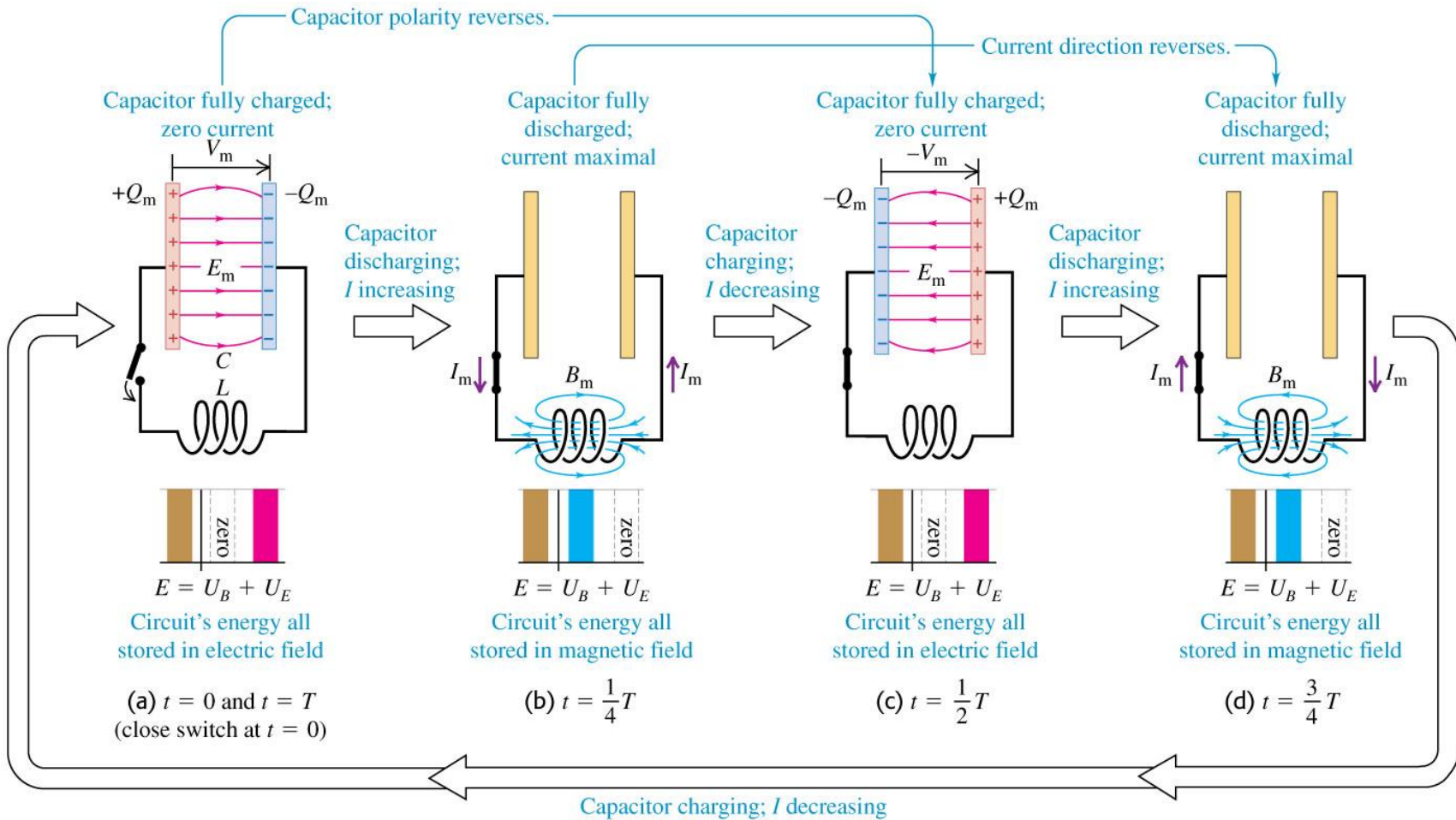
$$E_{\text{Total}} = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} Li^2 = \text{Constant} = \frac{1}{2} \frac{Q_{\text{max}}^2}{C} = \frac{1}{2} LI_{\text{max}}^2$$



Analogy to Spring-Mass Oscillations

$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0 \Rightarrow$$
$$x = X_0 \cos(\omega t + \phi)$$
$$\omega = \sqrt{\frac{k}{m}}$$

$$\frac{d^2q}{dt^2} + \frac{1}{LC}q = 0 \Rightarrow$$
$$q = Q_0 \cos(\omega t + \phi)$$
$$\omega = \sqrt{\frac{1}{LC}}$$

Table 30.1 Oscillation of a Mass-Spring System Compared with Electrical Oscillation in an *L-C* Circuit

Mass-Spring System

$$\text{Kinetic energy} = \frac{1}{2}mv_x^2$$

$$\text{Potential energy} = \frac{1}{2}kx^2$$

$$\frac{1}{2}mv_x^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2$$

$$v_x = \pm \sqrt{k/m} \sqrt{A^2 - x^2}$$

$$v_x = dx/dt$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$x = A \cos(\omega t + \phi)$$

Inductor-Capacitor Circuit

$$\text{Magnetic energy} = \frac{1}{2}Li^2$$

$$\text{Electric energy} = q^2/2C$$

$$\frac{1}{2}Li^2 + q^2/2C = Q^2/2C$$

$$i = \pm \sqrt{1/LC} \sqrt{Q^2 - q^2}$$

$$i = dq/dt$$


$$\omega = \sqrt{\frac{1}{LC}}$$

$$q = Q \cos(\omega t + \phi)$$

CPS 37-1

An inductor (inductance L) and a capacitor (capacitance C) are connected as shown.

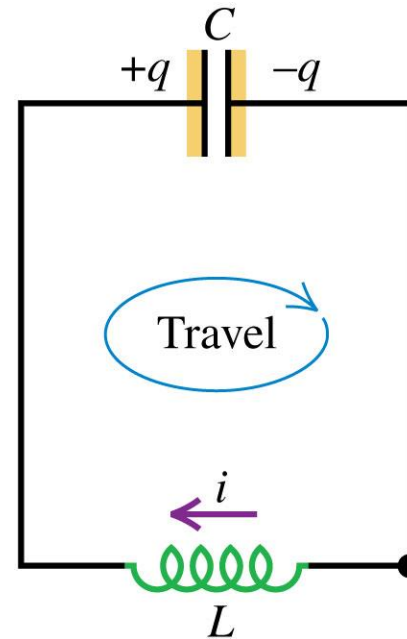If the values of both L and C are doubled, what happens to the *time* required for the capacitor charge to oscillate through a complete cycle?



© 2012 Pearson Education, Inc.

- A. It becomes 4 times longer.
- B. It becomes twice as long.
- C. It is unchanged.
- D. It becomes $1/2$ as long.
- E. It becomes $1/4$ as long.

Energy/Current/Charge Oscillations

- Now that you have the spring-mass system in your head as an analogy, what do you think happens if we put a resistor in series with the capacitor and inductor?
- Remember that with the resistor, the total energy will decrease due to the power dissipated in the resistor.

