

Lecture 39

PHYC 161 Fall 2016

Announcements


DO THE ONLINE COURSE EVALUATIONS

- response so far is < 28 %


Magnetic field energy

- A resistor is a device in which energy is irrecoverably *dissipated*.
- By contrast, energy stored in a current-carrying inductor can be recovered when the current decreases to zero.

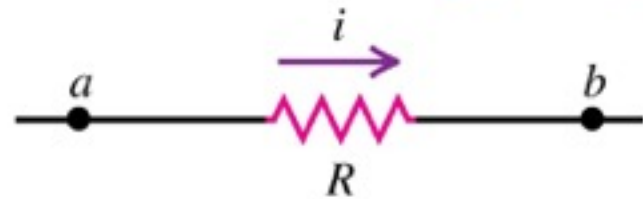Resistor with current i : energy is *dissipated*.



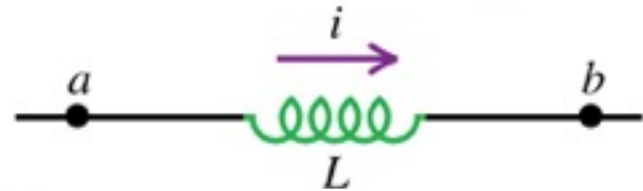Inductor with current i : energy is *stored*.



Energy stored in an inductor $\rightarrow U = L \int_0^I i \, di = \frac{1}{2} LI^2$

Inductance L (indicated by a dashed arrow pointing to the L in the equation)

Final current I (indicated by a dashed arrow pointing to the I in the equation)

Integral from initial (zero) value of instantaneous current to final value


Q30.3

A steady current flows through an inductor. If the current is doubled while the inductance remains constant, the amount of energy stored in the inductor

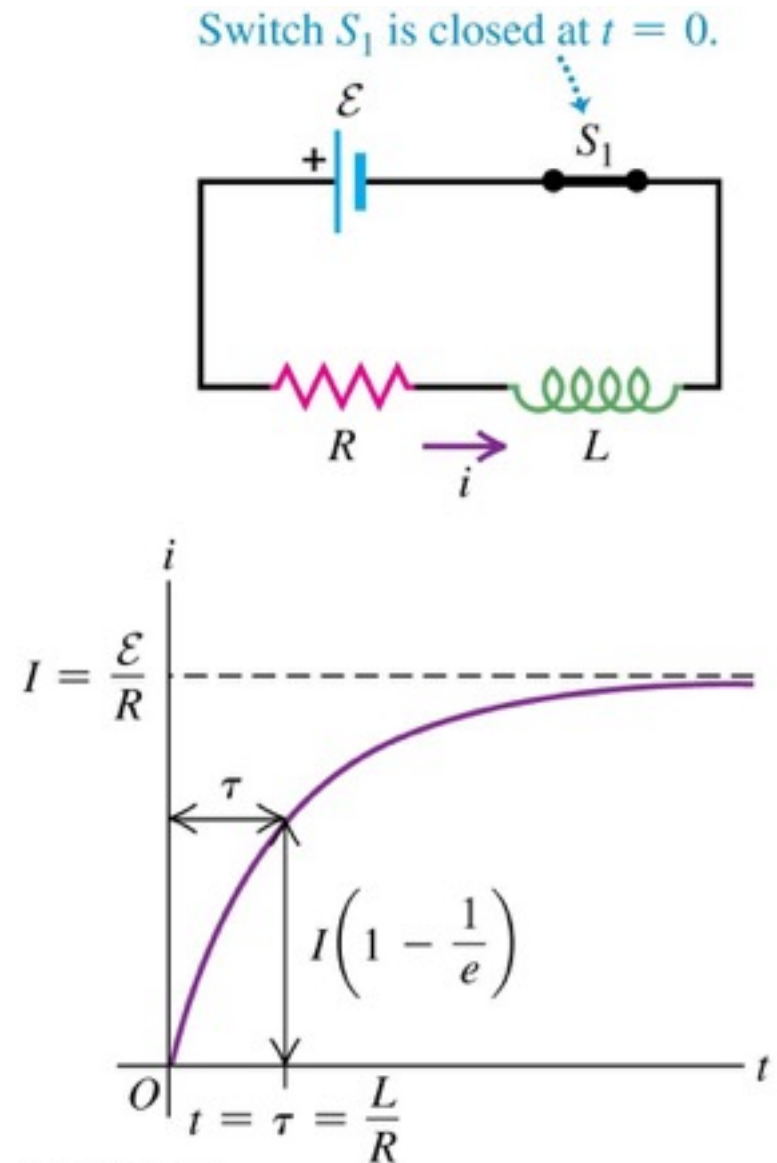- A. increases by a factor of $\sqrt{2}$.
- B. increases by a factor of 2.
- C. increases by a factor of 4.
- D. increases by a factor that depends on the geometry of the inductor.
- E. none of the above

Current growth in an R - L circuit

- Suppose that at some initial time $t = 0$ we close switch S_1 .
- The current cannot change suddenly from zero to some final value.
- As the current increases, the rate of increase of current given becomes smaller and smaller.
- This means that the current approaches a final, steady-state value I .
- The **time constant** for the circuit is $\tau = L/R$.




Q30.4

An inductance L and a resistance R are connected to a source of emf as shown. When switch S_1 is closed, a current begins to flow. The *final* value of the current is

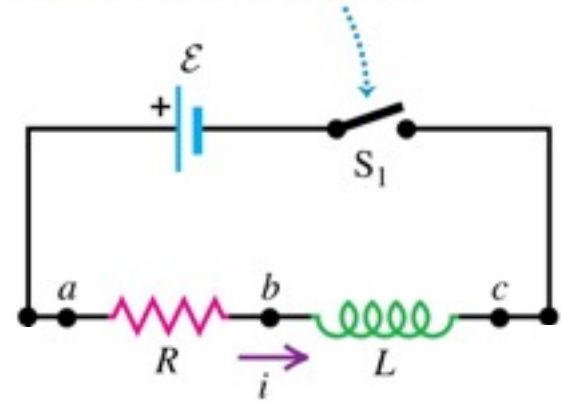- A. directly proportional to RL .
- B. directly proportional to R/L .
- C. directly proportional to L/R .
- D. directly proportional to $1/(RL)$.
- E. independent of L .

Closing switch S_1 connects the R - L combination in series with a source of emf \mathcal{E} .




Q30.5

An inductance L and a resistance R are connected to a source of emf as shown. When switch S_1 is closed, a current begins to flow. The *time* required for the current to reach one-half its final value is

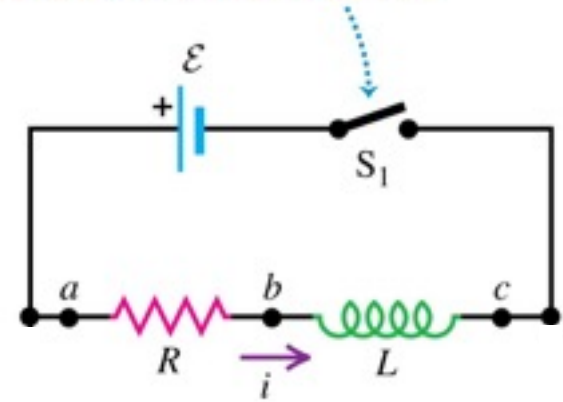
- A. directly proportional to RL .
- B. directly proportional to R/L .
- C. directly proportional to L/R .
- D. directly proportional to $1/(RL)$.
- E. independent of L .

Closing switch S_1 connects the R - L combination in series with a source of emf \mathcal{E} .



Current decay in an R - L circuit

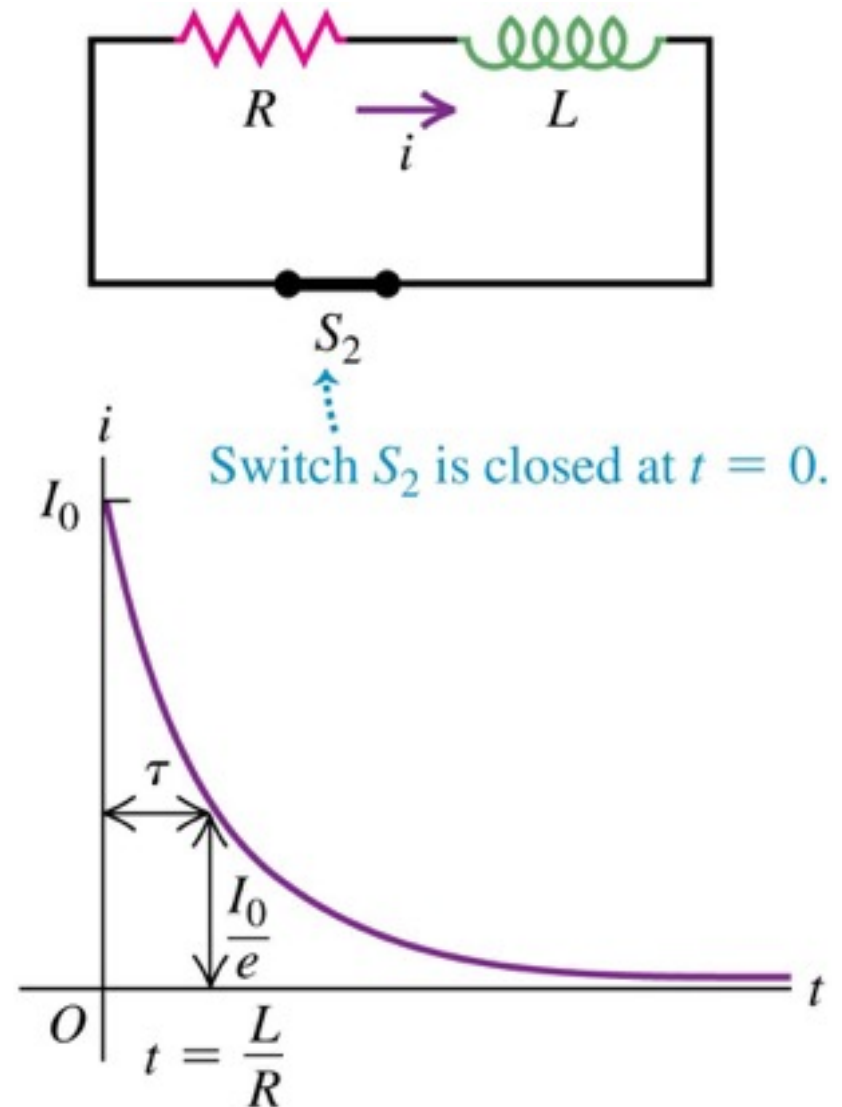- Suppose there is an initial current I_0 running through the resistor and inductor shown.
- At time $t = 0$ we close the switch S_2 , bypassing the battery (not shown).
- The energy stored in the magnetic field of the inductor provides the energy needed to maintain a decaying current.
- The **time constant** for the exponential decay of the current is $\tau = L/R$.




Q30.6

An inductance L and a resistance R are connected to a source of emf as shown. Initially, switch S_1 is closed, switch S_2 is open, and current flows through L and R . When S_1 is opened and S_2 is simultaneously closed, the *rate* at which this current decreases

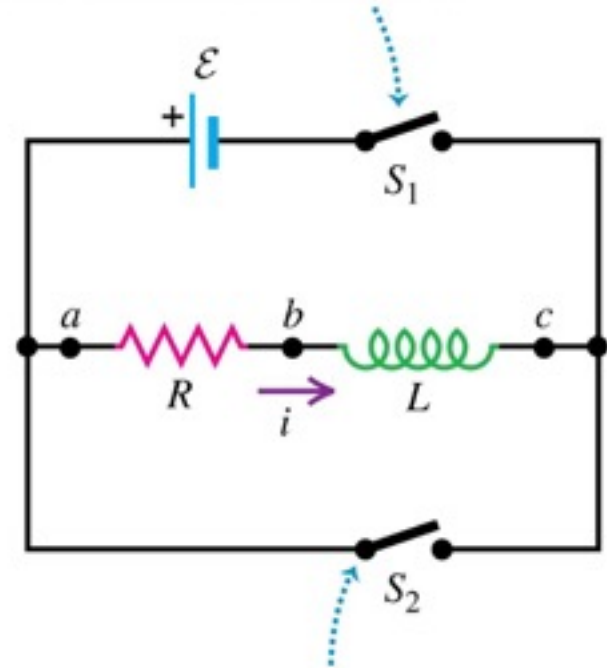- A. remains constant.
- B. increases with time.
- C. decreases with time.
- D. Any of A, B, or C is possible.
- E. Misleading question — the current does not decrease.

Closing switch S_1 connects the R - L combination in series with a source of emf \mathcal{E} .



Closing switch S_2 while opening switch S_1 disconnects the combination from the source.


- We start with a charged capacitor in series with a switch and an inductor. $Q_{\text{init}} = CV_{\text{init}}$
- Let's apply Kirchhoff's loop rule:

$$\sum \Delta V = -\frac{q}{C} - L \frac{di}{dt} = 0 \Rightarrow$$

$$\frac{q}{C} + L \frac{di}{dt} = 0 \Rightarrow$$

$$L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0 \Rightarrow$$
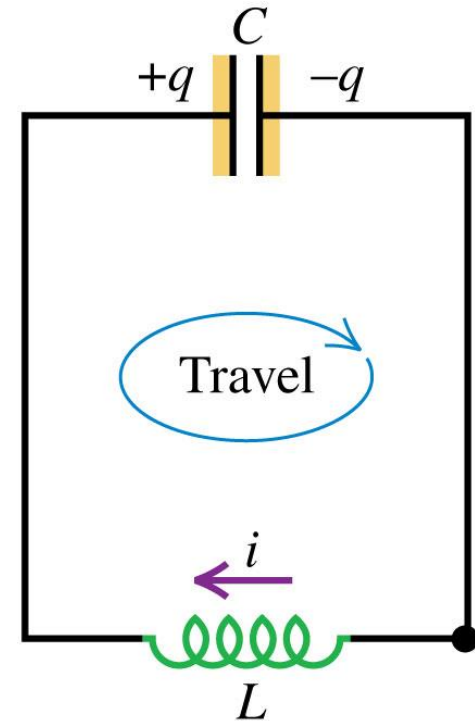
$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0$$



© 2012 Pearson Education, Inc.

Capacitor discharges
through inductor

LC Circuits

- Do you recognize this equation?

$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0$$

- What if I just changed q to x and renamed the constant?


$$\frac{d^2 x}{dt^2} + \omega^2 x = 0$$

- So the equation just describes oscillations with a frequency:

$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0 \Rightarrow$$

$$q = Q_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

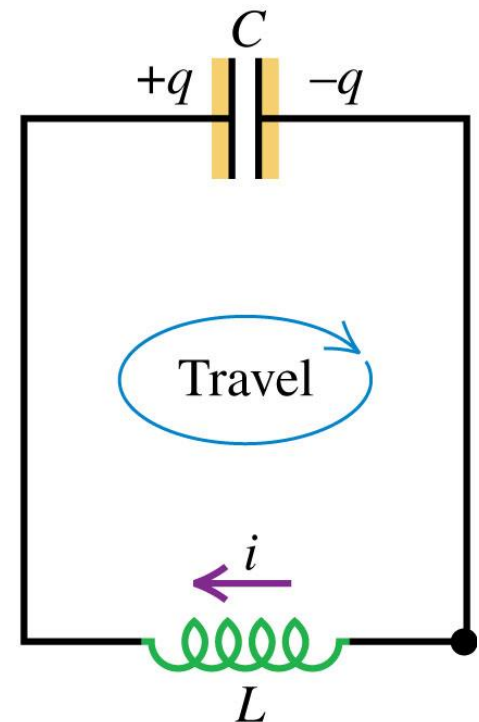

Analogy to Spring-Mass Oscillations

$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0 \Rightarrow$$

$$x = X_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$\frac{d^2q}{dt^2} + \frac{1}{LC}q = 0 \Rightarrow$$

$$q = Q_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

Table 30.1 Oscillation of a Mass-Spring System Compared with Electrical Oscillation in an **L-C** Circuit

Mass-Spring System

$$\text{Kinetic energy} = \frac{1}{2}mv_x^2$$

$$\text{Potential energy} = \frac{1}{2}kx^2$$

$$\frac{1}{2}mv_x^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2$$

$$v_x = \pm \sqrt{k/m} \sqrt{A^2 - x^2}$$

$$v_x = dx/dt$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$x = A \cos(\omega t + \phi)$$

Inductor-Capacitor Circuit

$$\text{Magnetic energy} = \frac{1}{2}Li^2$$

$$\text{Electric energy} = q^2/2C$$

$$\frac{1}{2}Li^2 + q^2/2C = Q^2/2C$$


$$i = \pm \sqrt{1/LC} \sqrt{Q^2 - q^2}$$

$$i = dq/dt$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$q = Q \cos(\omega t + \phi)$$



Capacitor fully charged;
zero current

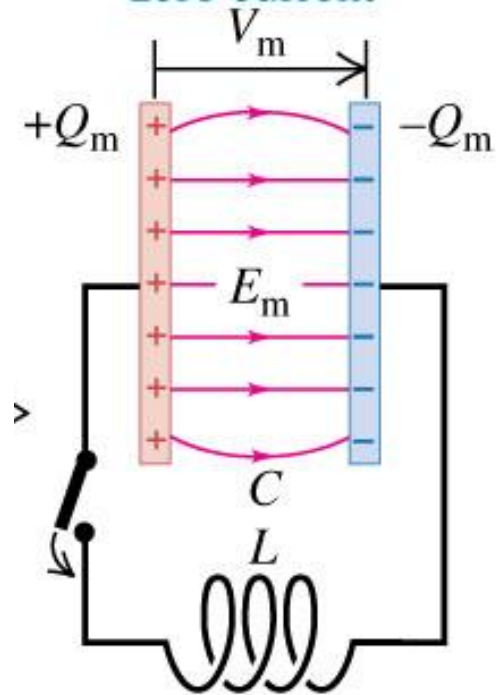

$$E = U_B + U_E$$

Circuit's energy all
stored in electric field

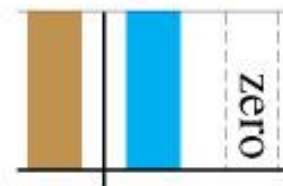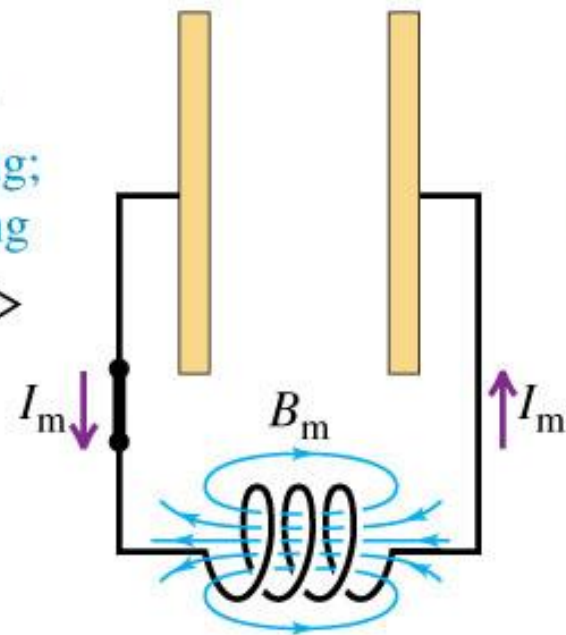
Capacitor fully
discharged;
current maximal





$$E = U_B + U_E$$

Circuit's energy all
stored in magnetic field

Capacitor
discharging;
 I increasing

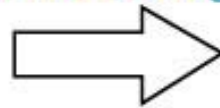

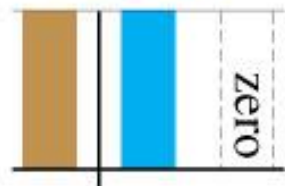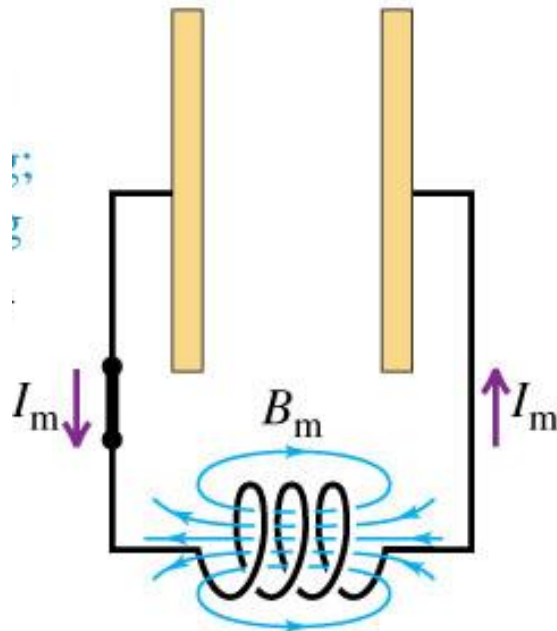
Capacitor fully discharged;
current maximal



$$E = U_B + U_E$$

Circuit's energy all stored in magnetic field


Capacitor fully charged;
zero current

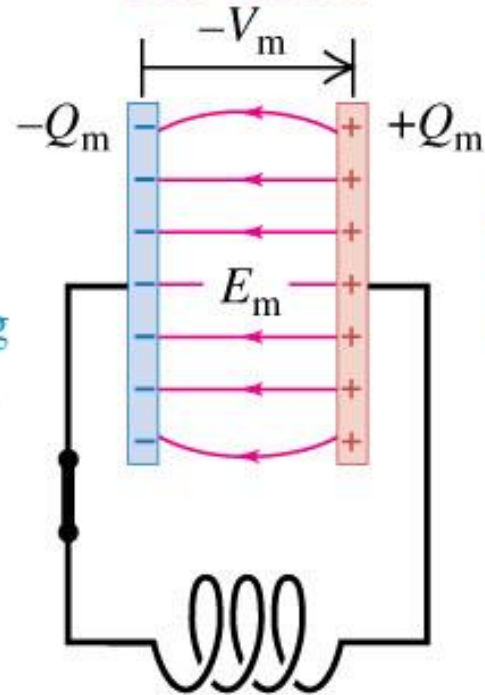


$$E = U_B + U_E$$

Circuit's energy all stored in electric field

Capacitor charging;
 I decreasing

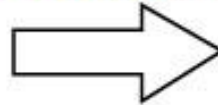

Capacitor fully charged;
zero current


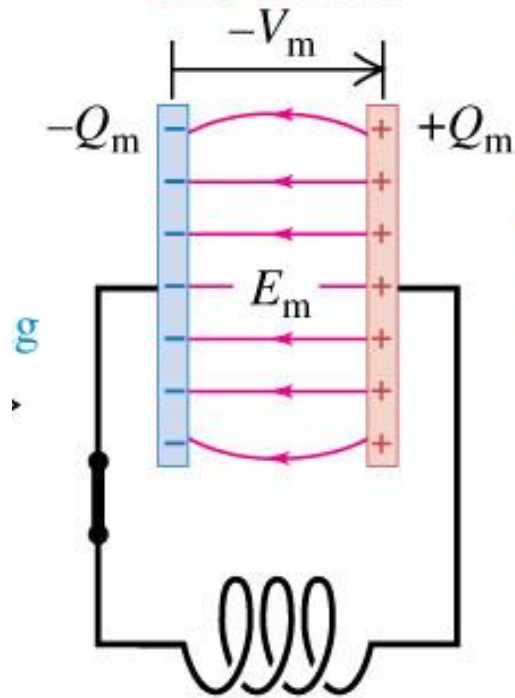


$$E = U_B + U_E$$

Circuit's energy all
stored in electric field

Capacitor fully
discharged;
current maximal

Capacitor
discharging;
 I increasing

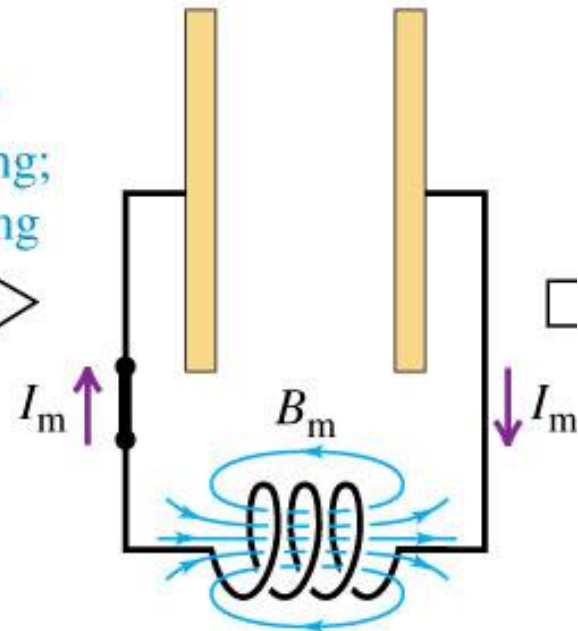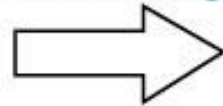


$$E = U_B + U_E$$

Circuit's energy all
stored in magnetic field

Energy/Current/Charge Oscillations


$$E_{\text{Total}} = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} Li^2 = \text{Constant} = \frac{1}{2} \frac{Q_{\text{max}}^2}{C} = \frac{1}{2} LI_{\text{max}}^2$$

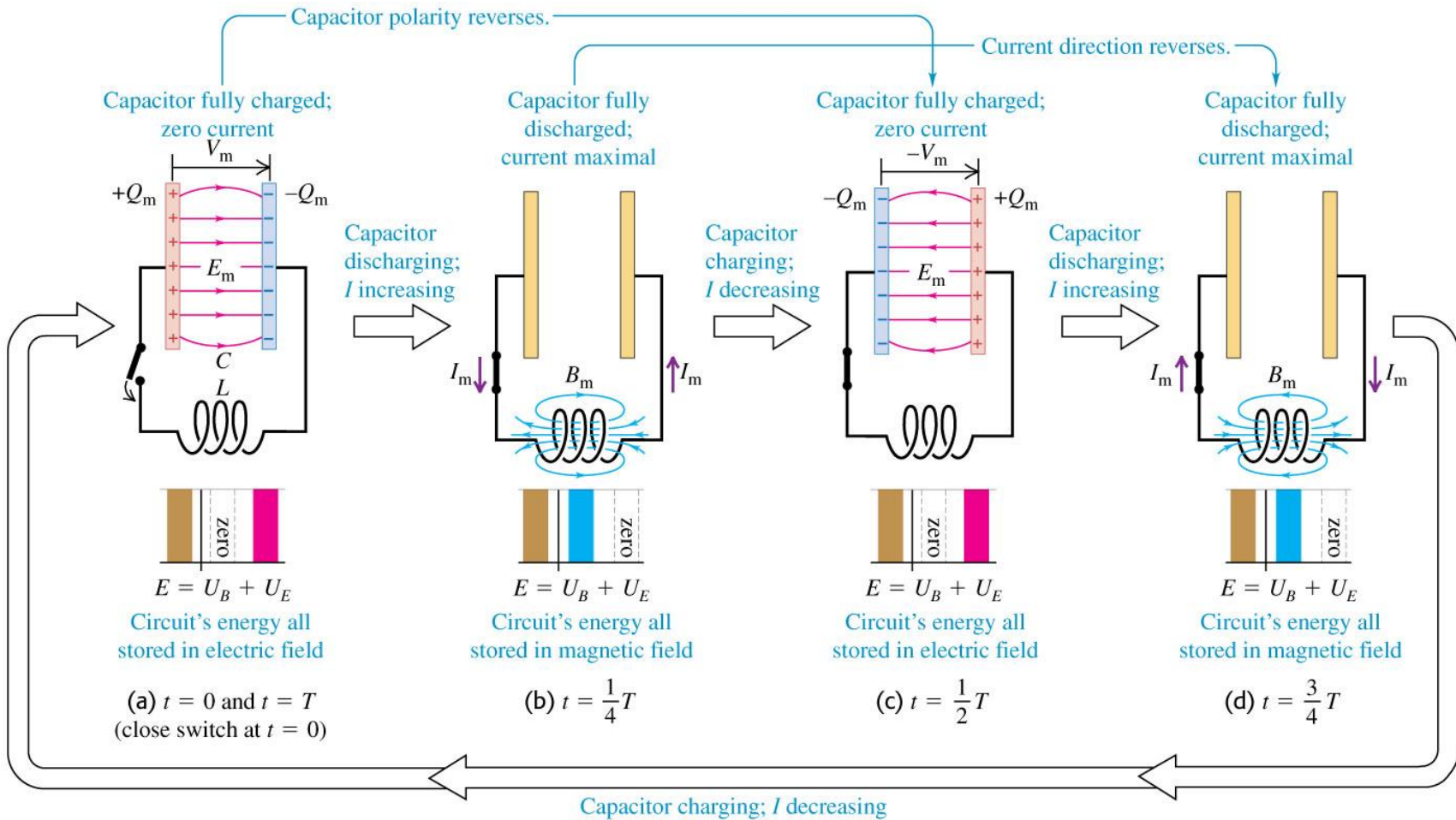

CPS 37-1

An inductor (inductance L) and a capacitor (capacitance C) are connected as shown.

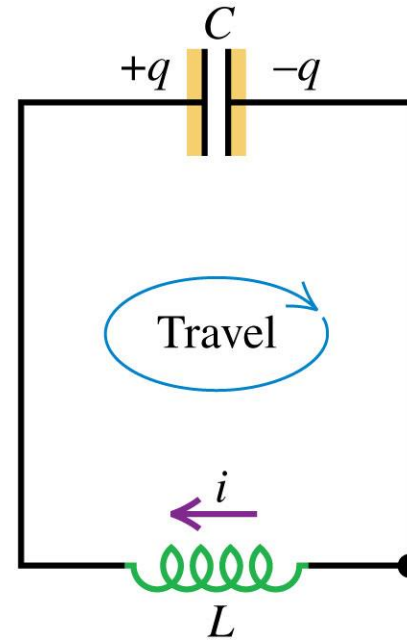If the values of both L and C are doubled, what happens to the *time* required for the capacitor charge to oscillate through a complete cycle?




© 2012 Pearson Education, Inc.

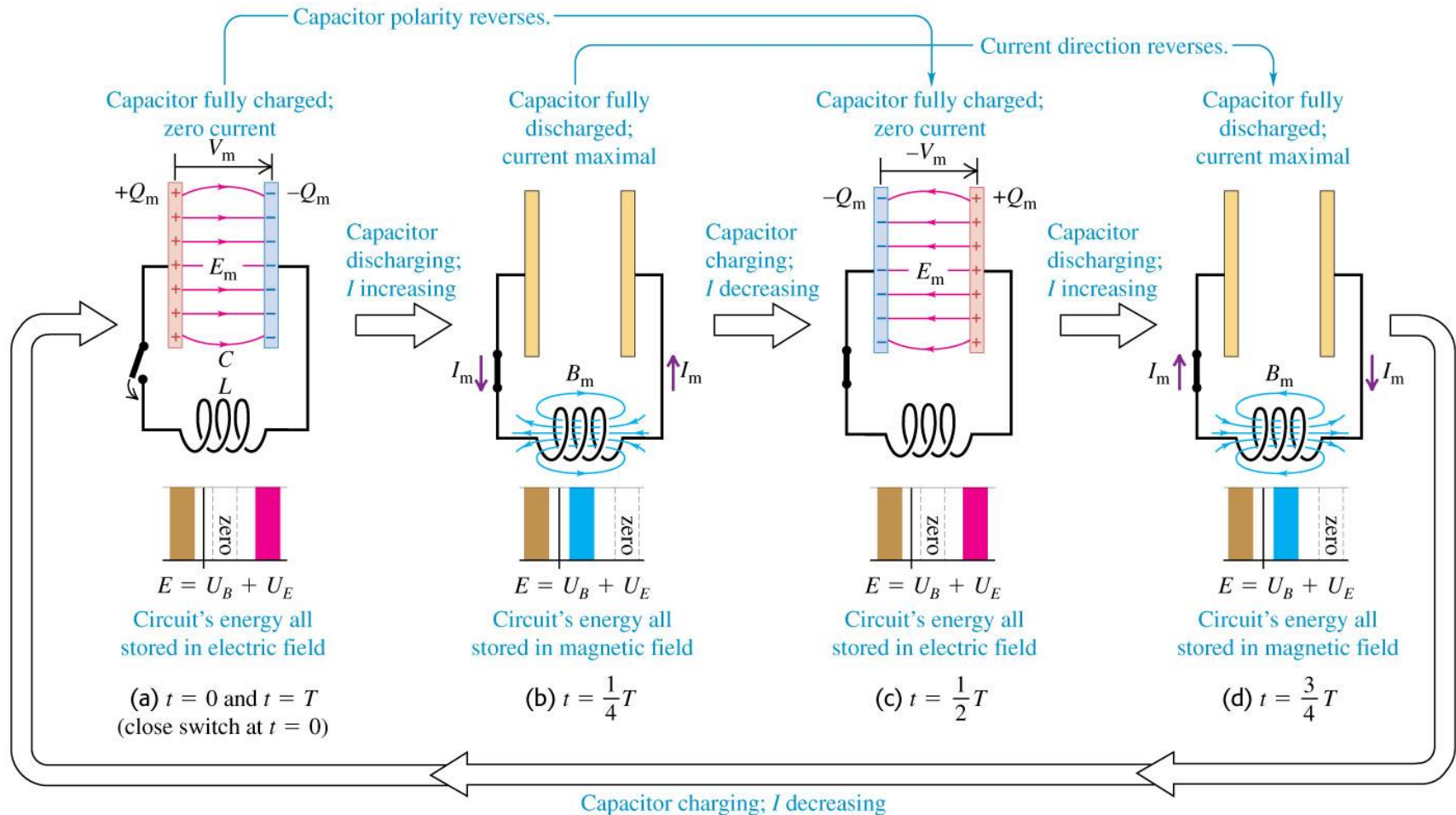- A. It becomes 4 times longer.
- B. It becomes twice as long.
- C. It is unchanged.
- D. It becomes 1/2 as long.
- E. It becomes 1/4 as long.

Energy/Current/Charge Oscillations

$$E_{\text{Total}} = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} Li^2 = \text{Constant} = \frac{1}{2} \frac{Q_{\text{max}}^2}{C} = \frac{1}{2} LI_{\text{max}}^2$$



Electrical and mechanical oscillations: analogies

Mass-Spring System

$$\text{Kinetic energy} = \frac{1}{2}mv_x^2$$

$$\text{Potential energy} = \frac{1}{2}kx^2$$

$$\frac{1}{2}mv_x^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2$$

$$v_x = \pm \sqrt{k/m} \sqrt{A^2 - x^2}$$

$$v_x = dx/dt$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$x = A \cos(\omega t + \phi)$$

Inductor-Capacitor Circuit

$$\text{Magnetic energy} = \frac{1}{2}Li^2$$

$$\text{Electrical energy} = q^2/2C$$

$$\frac{1}{2}Li^2 + q^2/2C = Q^2/2C$$

$$i = \pm \sqrt{1/LC} \sqrt{Q^2 - q^2}$$

$$i = dq/dt$$

$$\omega = \sqrt{\frac{1}{LC}}$$


$$q = Q \cos(\omega t + \phi)$$

Electrical oscillations in an L - C circuit

- We can apply Kirchoff's loop rule to the circuit shown.
- This leads to an equation with the same form as that for simple harmonic motion studied in Chapter 14.
- The charge on the capacitor and current through the circuit are functions of time:

$$q = Q \cos(\omega t + \phi)$$


$$i = -\omega Q \sin(\omega t + \phi)$$

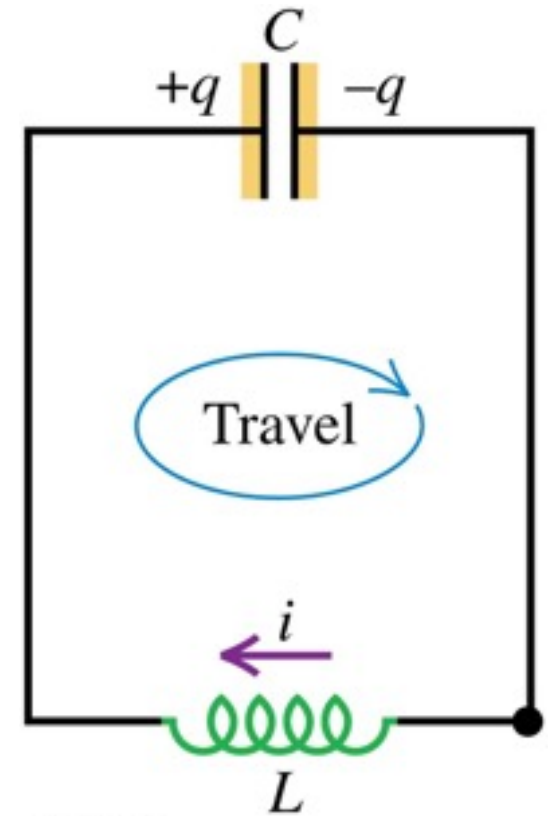

Angular frequency of oscillation in an L - C circuit $\omega = \sqrt{\frac{1}{LC}}$ Capacitance Inductance


Energy/Current/Charge Oscillations

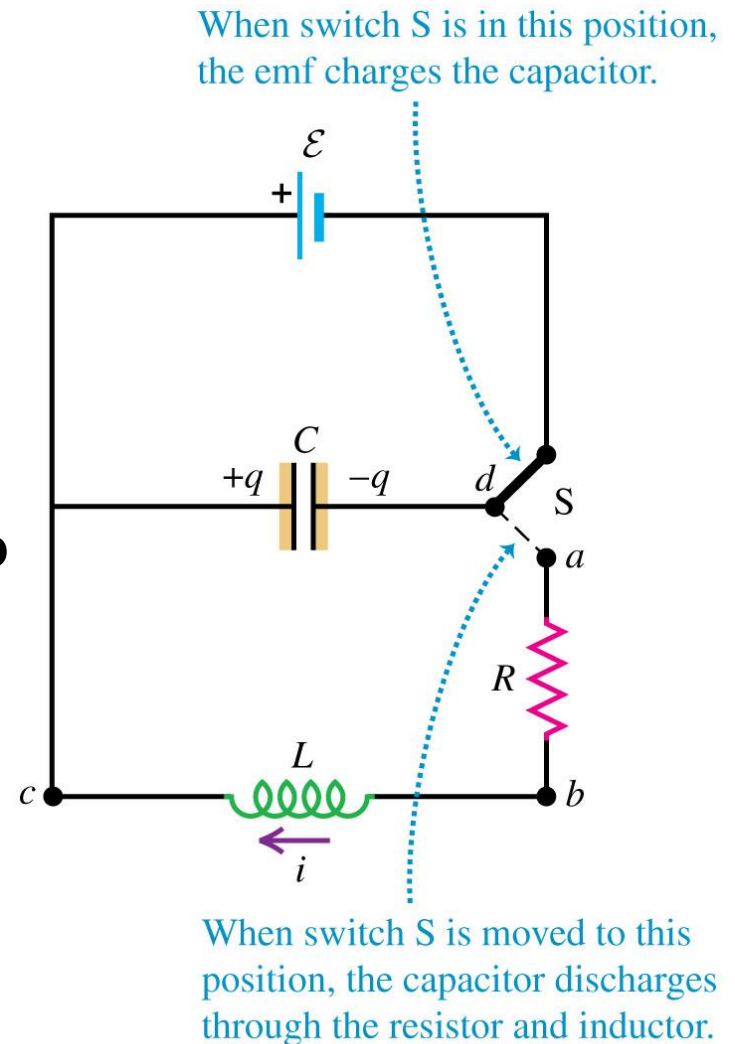- Now that you have the spring-mass system in your head as an analogy, what do you think happens if we put a resistor in series with the capacitor and inductor?
- Remember that with the resistor, the total energy will decrease due to the power dissipated in the resistor.



The L - R - C series circuit

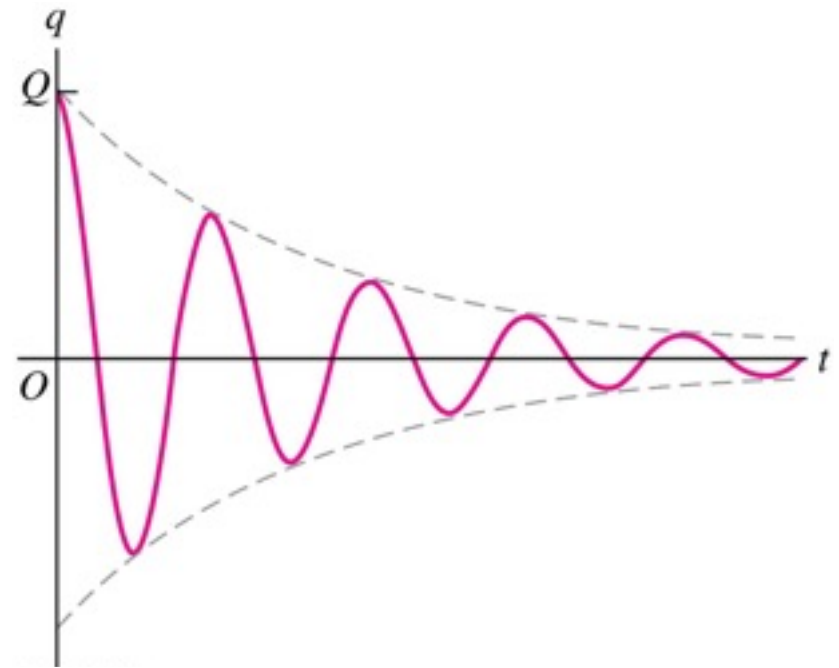- An L - R - C circuit exhibits **damped harmonic motion** if the resistance is not too large.
- The charge as a function of time is sinusoidal oscillation with an exponentially decaying amplitude, and angular frequency:



Angular frequency of underdamped oscillations in an L - R - C series circuit

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

Inductance Capacitance Resistance Inductance