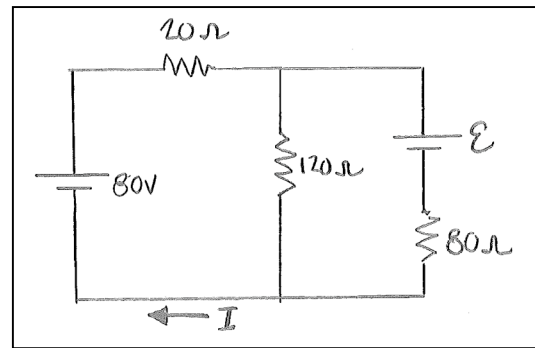


Physics 161 Fall 2010 Exam 5

Numbers and possibly circuit details will be changed on the real exam. Closed book closed notes calculators OK.

1&2. The current  $I$  is 1 A. What is the unknown EMF?

3&4. What is the power (in watts) dissipated in the 20 ohm resistor?



5&6. In the circuit shown below, what is the current through the battery immediately after closing the switch?  $EMF = 100V$ ,  $R_2=R_3=10$  ohms,  $R_1=20$  ohms.

7&8. What is the current through the battery a long time after the switch is closed?

9. To measure the current through the battery, an ammeter should be connected:

- A] touching points a and b
- B] touching points a and g
- C] touching points c and d
- D] the circuit must be broken at point a and the meter inserted
- E] the circuit must be broken at point c and the meter inserted
- F] the circuit must be broken at point e and the meter inserted
- G] none of these will work

10. To measure the voltage across resistor  $R_1$ , a voltmeter must be connected: (choose from the answers to Q9).

11&12. The capacitor is a parallel plate air-gap capacitor with area =  $0.1 \text{ m}^2$  and a plate separation of  $0.1 \text{ mm}$ . A long time after the switch is closed, what is the electric field in the capacitor?

13&14. What is the charge on the capacitor, in microcoulombs?

15&16. How much energy (in microJoules) is stored in the capacitor?

