

SOLUTIONS


Physics 161 Fall 2010 Exam 5

Numbers and possibly circuit details will be changed on the real exam. Closed book closed notes calculators OK.

1&2. The current I is 1 A. What is the unknown EMF?

3&4. What is the power (in watts) dissipated in the 20 ohm resistor?

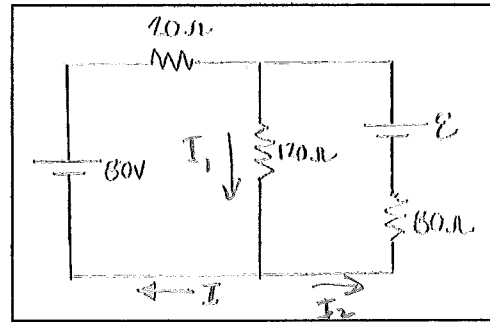ON REAL EXAM, THE 2-LOOP CIRCUIT MAY DIFFER.



5&6. In the circuit shown below, what is the current through the battery immediately after closing the switch? EMF = 100V, $R_2=R_3=10$ ohms, $R_1=20$ ohms.

7&8. What is the current through the battery a long time after the switch is closed?

9. To measure the current through the battery, an ammeter should be connected:

- A] touching points a and b
- B] touching points a and g
- C] touching points c and d
- D] the circuit must be broken at point a and the meter inserted**
- E] the circuit must be broken at point c and the meter inserted
- F] the circuit must be broken at point e and the meter inserted
- G] none of these will work

10. To measure the voltage across resistor R_1 , a voltmeter must be connected: (choose from the answers to Q9).

11&12. The capacitor is a parallel plate air-gap capacitor with area = 0.1 m^2 and a plate separation of 0.1 mm. A long time after the switch is closed, what is the electric field in the capacitor?

13&14. What is the charge on the capacitor, in microcoulombs?

15&16. How much energy (in microJoules) is stored in the capacitor?

$$E = V/d \quad V = IR_1 = 4 \cdot 20 = 80V$$

$$E = 80 \times 10^4 \text{ V/m}$$

$$C = \frac{\epsilon_0 A}{d} = \frac{8.85 \times 10^{-12} \cdot 0.1}{0.1 \times 10^{-3}}$$


$$= 8.85 \times 10^{-9}$$

$$CV = Q$$

$$= 8.85 \times 10^{-9} \cdot 80V$$

$$= 708 \times 10^{-9}$$

$$= 0.7 \mu C$$

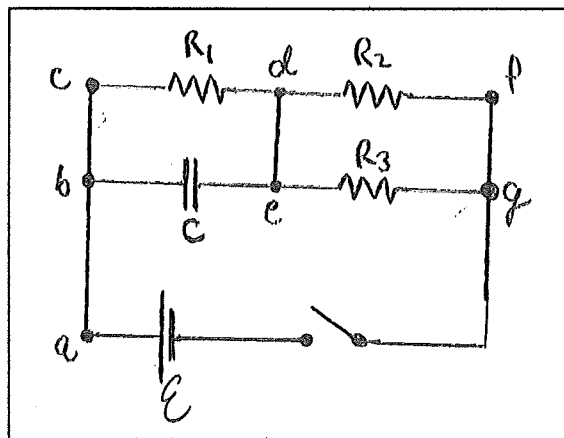

15&16] $U = \frac{1}{2} CV^2 = 28 \times 10^{-5} \text{ J} \approx 30 \mu J$

SEE FOLLOWING PAGE

182) Kirchoff Loop Laws

$$80 - 20I - 120I_1 = 0$$

$$\Sigma - 120I_1 - 80I_2 = 0$$

$$I_1 = I + I_2$$

unknowns I, I_2, Σ . $I = 1A$.

$$\begin{cases} 80 - 20 - 120I_1 = 0 & \rightarrow I_1 = \frac{1}{2}A \\ \Sigma - 120I_1 - 80(I_1 - I) = 0 \end{cases}$$

$$\Sigma - 200I_1 + 80 = 0$$


$$\Sigma - 100 + 80 = 0$$

$$\Sigma = 20V$$

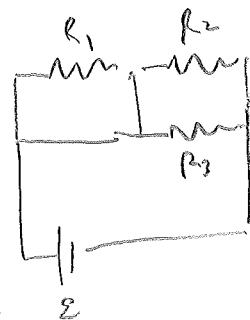324) $P = I^2 R = 1^2 \cdot 20 = 20W$

5 & 6) $\frac{1}{\text{Cap}} = \text{Short circuit}$

$\frac{1}{\text{Cap}} = \text{at long times}$



At short times, R_1 doesn't matter, R_2 & $R_3 \Rightarrow \frac{1}{R_{\text{eff}}} = \frac{1}{R_2} + \frac{1}{R_3}$ $R_{\text{eff}} = 5\Omega$.

$$I = 100V / 5\Omega = 20 \text{ Amps}$$

728] Cap = open circuit. so $R_{\text{eff}} = R_1 + R_{\text{eff}} = 20\Omega + 5\Omega = 25\Omega$

$$I = 100V / 25\Omega = 4 \text{ Amps}$$